 




Digital Microelectronic Circuits

(361-1-3021)

Presented by: Adam Teman

Lecture 7: Logical Effort

Last Lectures

- ❑ The CMOS Inverter
 - » Delay Calculation
 - » Driving a Load
- ❑ CMOS Digital Logic
 - » Dealing with High Fan-In

This Lecture



- ❑ So we learned how to drive a large load with a chain of inverters.
- ❑ But what if there is logic to be calculated along the way?
- ❑ How should we distribute the logic in order to optimally drive the load?
- ❑ Can we develop a methodology for designing a logical network?



Design Technique Question

- We need to implement an 8-input decoder:


$$F = ABCDEFGH$$

  

- Which implementation is best?

Design Technique Question 2

 - Is it better to drive a big capacitive load directly with the NAND gate or after some buffering?



- Method to answer both of these questions:


» Logical Effort

- This is an extension of the buffer sizing problem

Reminder: Inverter with Load

- We saw that the delay increases with ratio of load to inverter size:
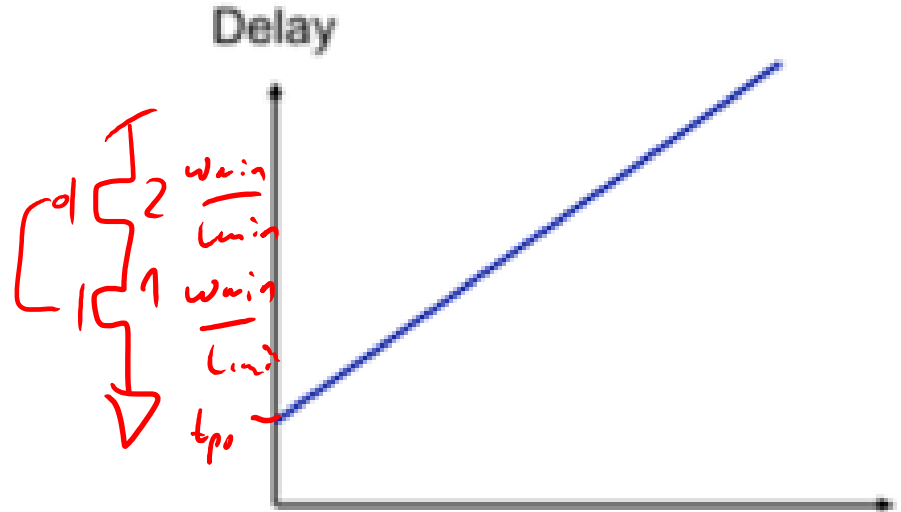
$$t_p = t_{p0} \left(1 + \frac{f}{\gamma} \right)$$




- t_{p0} is the intrinsic delay of an unloaded inverter.
- γ is a technology dependent ratio.
- f is the **Effective Fanout** – ratio of load to inverter size

Reminder: Inverter with Load

- For easier equations, we will rewrite this a bit...


$$\underline{t_{pINV}} \triangleq t_{p0} / \gamma = 0.69 R_{out} C_{in} \Rightarrow \underline{t_p} = \underline{t_{pINV}} (\underline{\gamma} + \underline{f})$$

- For a chain of inverters, we get:

 

$$Delay = t_{inv} \sum_{i=1}^N (\gamma + f_i)$$

An Optimal (reference) Inverter

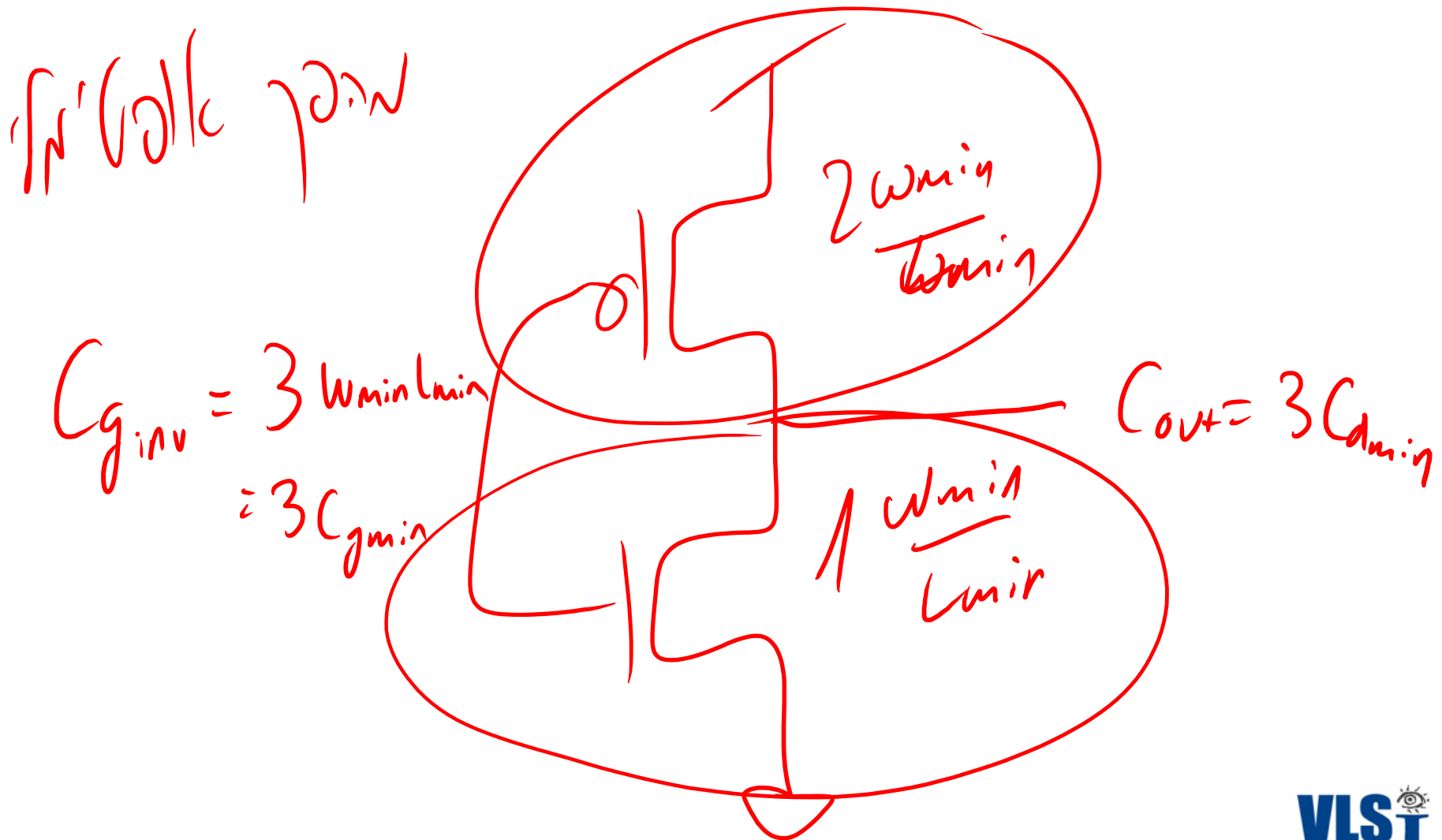


Now, lets look at a NAND Gate

- We will take a NAND gate sized for equal resistance to an optimal inverter.
- We notice that:

$$C_{g,A} = C_{g,B} = 4C_{g,min} = \frac{4}{3}C_{g,INV}$$

 
$$C_{out,NAND} \approx 6C_{d,min} \quad C_{out,INV} \approx 3C_{d,min}$$



- Let us write the delay of the NAND:

$$t_{p,NAND} = 0.69R_{NAND}C_{out} = 0.69R_{INV} (C_{out,NAND} + C_{Load})$$

Now, lets look at a NAND Gate

 

$$\frac{C_{out,NAND}}{C_{out,INV}} \approx \frac{6C_{d,min}}{3C_{d,min}} = 2$$

$$C_{g,INV} = \frac{3}{4} C_{g,NAND}$$

$$t_{p0} = 0.69R_{INV}C_{out,INV}, \quad t_{p,INV} = \frac{t_{p0}}{\gamma}$$

$$\gamma = \frac{C_{d,min}}{C_{g,min}} \Rightarrow C_{out,INV} = \gamma C_{g,INV}$$


$$\begin{aligned} t_{p,NAND} &= 0.69R_{INV} (C_{out,NAND} + C_L) = 0.69R_{INV} \frac{C_{out,INV}}{\gamma} \left(\frac{\gamma C_{out,NAND}}{C_{out,INV}} + \frac{\gamma C_L}{C_{out,INV}} \right) \\ &= \frac{t_{p0}}{\gamma} \left(\frac{6C_{d,min}}{3C_{d,min}} \gamma + \frac{\cancel{\gamma} C_L}{\cancel{\gamma} C_{g,INV}} \right) = t_{p,INV} \left(\frac{2\gamma + \frac{C_L}{\frac{3}{4}C_{g,NAND}}}{1} \right) \\ &= t_{p,INV} \left(2\gamma + \frac{4}{3} f \right) \end{aligned}$$

$$t_{p(NAND)} = t_{p,INV}(\gamma + f)$$

Now, lets look at a NAND Gate

- We arrived at:
 
$$t_{p,NAND} = t_{p,INV} \left(2\gamma + \frac{4}{3} f \right)$$



$2 t_{pinv}$

- Two Conclusions:

- » The intrinsic (unloaded) delay is twice that of an inverter.
- » The fanout increases the delay at a faster pace than an inverter.


- It is better to drive a load with an inverter than a NAND!

How about a NOR Gate?

- We take an optimal NOR:

$$\frac{C_{out,NOR}}{C_{out,INV}} \approx \frac{(4+1+1)C_{d,min}}{3C_{d,min}} = 2$$
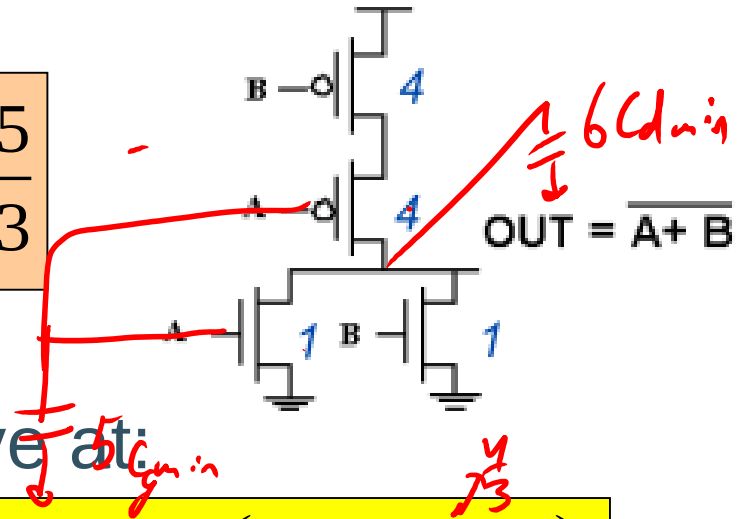
$$\frac{C_{g,NOR}}{C_{g,INV}} = \frac{5}{3}$$



- Using the same steps, we arrive at:

$$\underline{t_{p,NOR}} = t_{p,INV} \left(\frac{C_{out,NOR}}{C_{out,INV}} \gamma + \frac{C_{g,NOR}}{C_{g,INV}} f \right) = t_{p,INV} \left(\underline{2\gamma} + \frac{5}{3} f \right)$$

- A NOR gate is less efficient than a NAND at driving a load!

Logical Effort

- We can generalize the delay to be:

$$t_p = t_{p,INV} (p \cdot \gamma + LE \cdot f)$$

- » p – intrinsic delay (~proportional to Fan In)
- » LE – Logical Effort
- » f – Electrical Effort
- » $EF = LE \times f \rightarrow$ Effective Fanout

$$t_p = t_{p,INV} (\gamma + f)$$

- » $LE(INV)=1$ $p(INV)=1$

Logical Effort

□ To summarize:

- » The logical effort of a gate describes how much “effort” we need to perform a logic calculation.
- » An Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates.
- » Logical Effort increases with gate complexity.

Generalization of LE

$$t_{pd} = 0.69R_{gate} (C_{d,gate} + C_{Load}) = \underline{0.69R_{gate}} \frac{\cancel{R_{inv}}}{R_{inv}} \frac{\cancel{C_{d,inv}}}{C_{d,inv}} \frac{\gamma}{\cancel{\gamma}} (C_{d,gate} + C_{Load})$$

$$t_{p,inv} \triangleq \frac{0.69R_{inv}C_{d,inv}}{\gamma}$$

$$= t_{p,inv} \left(\frac{\cancel{R_{gate}}}{\cancel{R_{inv}}} \frac{\gamma}{\cancel{C_{d,inv}}} C_{d,gate} + \frac{R_{gate}}{R_{inv}} \frac{\cancel{\gamma}}{\cancel{C_{d,inv}}} C_{Load} \right)$$

$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}}, \frac{C_{d,inv}}{\gamma} = C_{g,inv}$$

$$= t_{p,inv} \left(p\gamma + \frac{R_{gate}}{R_{inv}} \frac{1}{C_{g,inv}} \cdot \frac{C_{g,gate}}{C_{g,gate}} C_{Load} \right)$$

$$LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}, f \triangleq \frac{C_{Load}}{C_{g,gate}}$$

$$= t_{p,inv} (p \cdot \gamma + LE \cdot f)$$

Generalization of LE

$$t_{pd} = t_{p,inv} (p \cdot \gamma + LE \cdot f)$$

$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}} \quad LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$

Logical Effort Methodology


$$t_{pd} = t_{p,inv} (p \cdot \gamma + LE \cdot f)$$

$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}} \quad LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$

- ❑ We “don’t like” the resistance factor in the expressions for p and LE .
- ❑ Therefore, first size the gate so the resistance is equivalent to an optimal inverter.
- ❑ Now just find the ratio of capacitances to an optimal inverter!

LE of a NAND Gate
 
$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}} \quad LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$



$$\rightarrow C_{d,gate} = 6C_{dmin}$$

$$C_{g,A} = C_{g,B} = 4C_{gmin}$$


$$p = \frac{R_{gate}}{R_{inv}} \cdot \frac{C_{d,gate}}{C_{d,inv}} = \frac{6C_{dmin}}{3C_{dmin}} = 2$$

$$LE = \frac{C_{g,A}}{C_{g,inv}} = \frac{4}{3}$$

$$t_{p(NAND)} = t_{p,inv} \left(2 + \frac{4}{3} \right)$$

LE of a NOR Gate
 
$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}} \quad LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$




$$p = \frac{C_{d,gate}}{C_{d,inv}} = \frac{6}{3} = 2$$

$$LE = \frac{5}{3}$$

$$t_p(NOR) = t_{p,inv} \left(2 + \frac{5}{3} \right)$$

Logical Effort of Gates
 
$$t_p = t_{p,INV} (p \cdot \gamma + LE \cdot f)$$



$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}} \quad LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$

What happens with higher Fan-In?


- A three-input NAND gate:

$$C_{gA,B,C} = 5C_{gm'n}$$

$$LE = \frac{5}{3}$$

- A three-input NOR gate:

$$P = \frac{9}{3} = 3$$

 

$$LE_{NAND} = \frac{(n+2)}{3}$$

$$t_{p\ NAND_3} = t_{pinv} \left(38 + \frac{5}{3} \right)$$

$$LE_{NOR} = \frac{(2n+1)}{3}$$




Last Lecture

- The method of Logical Effort:

$$t_p = t_{p,INV} (p \cdot \gamma + LE \cdot f)$$

$$p \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{d,gate}}{C_{d,inv}}$$

   
$$LE \triangleq \frac{R_{gate}}{R_{inv}} \frac{C_{g,gate}}{C_{g,inv}}$$



$$\frac{4}{3} \cdot f$$

Add Branching Effort

- What happens if a node branches off?

 

$$b = \frac{C_{L,\text{on-path}} + C_{L,\text{off-path}}}{C_{L,\text{on-path}}} = \frac{C_{L,\text{total}}}{C_{L,\text{on-path}}}$$

Cascading gates into a Path

$$t_p = t_{p,INV} \sum_{i=1}^N (p_i \cdot \gamma + \underbrace{LE_i \cdot f_i \cdot b_i})$$

□ Let's give a few things names...

» Stage Electrical Effort $EF_i \equiv \underbrace{LE_i \cdot f_i \cdot b_i}_{\text{Stage Electrical Effort}} = LE_i \cdot \frac{C_{out,i} \cdot b_i}{C_{in,i}}$

» Path Electrical Fanout $F \equiv \frac{C_{out}}{C_{in}}$

» Path Logical Effort $\Pi LE = LE_1 \cdot LE_2 \cdot \dots \cdot LE_N$

» Path Branching Effort $\Pi B = b_1 \cdot b_2 \cdot \dots \cdot b_N$

» Path Effort

$$PE = F \cdot \Pi LE \cdot \Pi B$$

Cascading gates into a Path

$$t_p = t_{p,INV} \sum_{i=1}^N (p_i \cdot \gamma + LE_i \cdot f_i \cdot b_i)$$

- ❑ Using the same approach as before, we can find the minimal delay.
- ❑ The solution, again, is that the electrical effort should be equal between stages, so we get:

$$EF_i = \sqrt[N]{PE} = \sqrt[N]{F \cdot \Pi LE \cdot \Pi B}$$


Optimal Number of Stages

- We now have a delay equation:

$$t_p = N \cdot \sqrt[N]{PE} + \gamma \sum p_i$$

- We can find the optimal number of stages.

 - Again we get $EF_{opt}=4$ (3.6 with $\gamma=1$)



Summary – Method of Logical Effort

- Compute the *Path Effort*:

$$PE = F \cdot \prod LE \cdot \prod B$$

- Find the optimal number of stages:

$$N = \left\lfloor \log_{3.6} PE \right\rfloor$$

- Compute the *Effective Fanout*:
(identical for all stages)

$$EF = \sqrt[N]{PE}$$

$\sim f_{charge}$

- Find sizes of each stage:

$$EF_i \equiv LE_i \cdot f_i = LE_i \cdot \frac{C_{out,i} \cdot b_i}{C_{in,i}}$$


$$C_{in,i} = LE_i \cdot \frac{C_{out,i} \cdot b_i}{EF}$$

Example

Given the following network with

- » $C_{in,1} = C$
- » Size of Y and Z equal for all gates at the same stage.

 Size the gates optimally for the red path.



$$F = \frac{9}{1} = 9, \quad \Pi LE = \frac{4}{3} \cdot \frac{4}{3} \cdot \frac{4}{3} = \frac{64}{27}$$

$$b_C = \frac{2}{1}, \quad b_Y = \frac{3}{1}, \quad b_Z = \frac{1}{1} \Rightarrow \Pi B = 6$$

$$PE = 9 \cdot \frac{64}{27} \cdot 6 = 128 \Rightarrow EF = \sqrt[3]{128} = 5.04$$

$$C_Z = LE_Z \cdot \frac{C_L \cdot b_Z}{EF} = \frac{4}{3} \cdot \frac{9C \cdot 1}{5.04} = 2.38C$$

$$C_Y = LE_Y \cdot \frac{C_Z \cdot b_Y}{EF} = \frac{4}{3} \cdot \frac{2.38C \cdot 3}{5.04} = 1.89C$$

SANITY CHECK!!!

$$C_C = LE_C \cdot \frac{C_Y \cdot b_C}{EF} = \frac{4}{3} \cdot \frac{1.89C \cdot 2}{5.04} = 0.998C$$



$$C_{in,i} = LE_i \cdot \frac{C_{out,i} \cdot b_i}{EF}$$