

# Digital Microelectronic Circuits (361-1-3021 )

Presented by: Mr. Adam Teman

## Lecture 8: Ratioed Logic

# Motivation

- ❑ In the previous lecture, we learned about *Standard CMOS Digital Logic* design.
- ❑ *CMOS* is unquestionably the leading design family in use today, due to its many advantages and relative simplicity. However, it has a number of drawbacks that have led to the development of alternative solutions.
- ❑ The main drawback of *Standard CMOS* is its relatively large area ( *$2N$  transistors* to implement an  *$N$ -input gate*).
- ❑ In this lecture, we will start to overview a number of **alternative logic families** that try to *reduce the number of transistors* needed to implement a logic function.

# *What will we learn today?*

---

**8.1 Ratioed Logic**

**8.2 Pseudo NMOS**

**8.3 LE of Pseudo NMOS**

# 8.1


## 8.1 Ratioed Logic

## 8.2 Pseudo NMOS

## 8.3 LE of Pseudo NMOS

Let's start with an important concept that has driven a number of logic families:

# ***RATIOED LOGIC***

 

# Ratioed Logic Concept


- ❑ When we discussed *Standard CMOS* during the previous two lectures, we spent quite a while analyzing the *sizes of the transistors*.
- ❑ It is important to note that these sizing considerations improved the *performance* (=speed) of the logic gates, but not their *functionality*.
- ❑ In other words, even if we implemented the gates *without size considerations*, we would arrive at the *requested logic function* (though it might take a while...).

# Ratioed Logic Concept


- ❑ **Ratioed Logic** is an attempt to *reduce the number of transistors* required to implement a given logic function, *waiving the assurance of functionality*.
- ❑ As its name implies, *in order to ensure functionality*, a certain *ratio of sizes* has to be kept *between various devices* that make up the gate.
- ❑ **Ratioed Logic** has another great disadvantage – high *static power dissipation* – which makes it vary scarcely used. But the concept is implemented in quite a few complex circuits (such as *memory circuits*), and so it is important to understand.
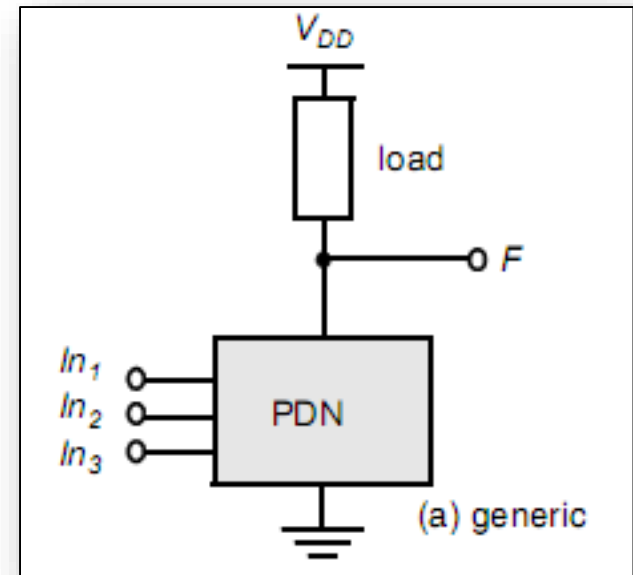
# Ratioed Logic Concept

- ❑ The concept of *Ratioed Logic* uses the same *Pull Down Network* as *CMOS*, but uses a simple *Load* as its *Pull Up Network*.
- ❑ This *Load* constantly *leaks current* from the supply to the output capacitance. In this way, the output is charged when the *PDN* is *closed*, providing a '1'.
- ❑ On the other hand, the *Load's resistance* is much larger than that of an *open PDN*, so when the *PDN* is open, *the output is pulled down to  $V_{OL}$* .
- ❑ The ratio between the resistance of the *Load* and the *PDN* is crucial in designing such a gate, hence it is called "*Ratioed*" Logic.




# VTC of Generic Ratioed Logic Gate

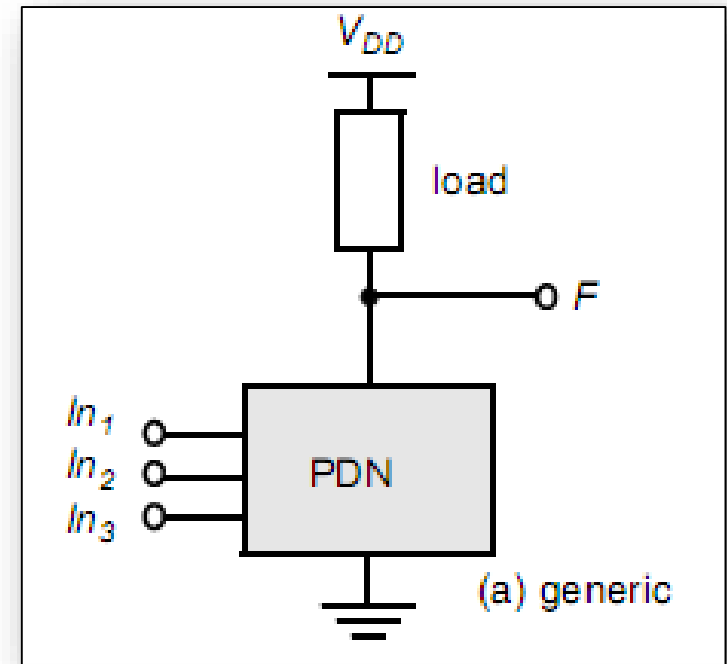



 
# Ratioed Logic Characteristics

- N transistors + Load
- $V_{OH} = V_{DD}$
- $V_{OL} = \frac{R_{PDN}}{R_{PDN} + R_L}$
- Asymmetrical Response
- Static Power Consumption
- Slow pull up:  $t_{pLH} = 0.69C_{out}R_L$



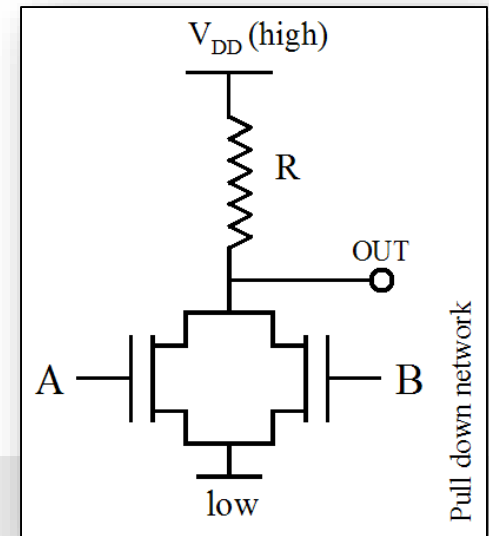
# Load Implementation

- ❑ Early *Ratioed Logic* designs used a simple **resistor** as the *Load*.
- ❑ This approach had several drawbacks, especially with the difficulty in **resistor implementation** in *VLSI*.



 
# Load Implementation

- Accordingly, the *Load* was replaced with a *Diode-connected nMOS* ( $V_{GD}=0$ ) a.k.a. *Saturated Load Inverter*.
- This circuit stopped conducting at  $V_{GS}=V_{DD}-V_{Tn}$  (*weak '1'*) providing a largely reduced *swing*.


 
# Load Implementation

- ❑ To *improve the swing*, the *nMOS* (also known as an “*enhancement mode*” *nMOS*) was replaced with a “*Depletion Mode*” *nMOS*.
- ❑ This is a special, *highly doped nMOS* with a *negative threshold voltage* ( $V_{Tn} < 0$ ).
- ❑ This was used for some time until the *Pseudo nMOS inverter* was invented, replacing the *nMOS load* with a *pMOS* connected to *ground*.



# 8.2

**8.1 Ratioed Logic**

**8.2 Pseudo NMOS**

**8.3 LE of Pseudo NMOS**




The only really surviving ratioed logic family is:

***PSEUDO NMOS***
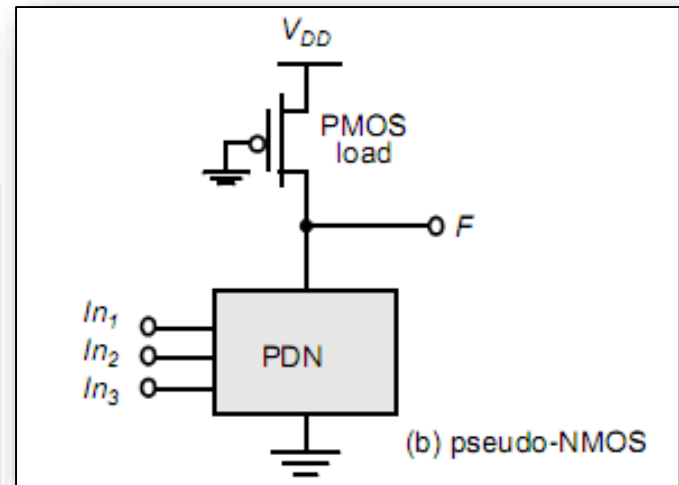
# Pseudo nMOS


- The topology of a *Pseudo nMOS* gate is shown in the following figure:



- The clear advantage of this gate over *Standard CMOS* is the **reduced number of transistors**:
  - »  *$N+1$  transistors* to implement an  *$N$ -input gate*.
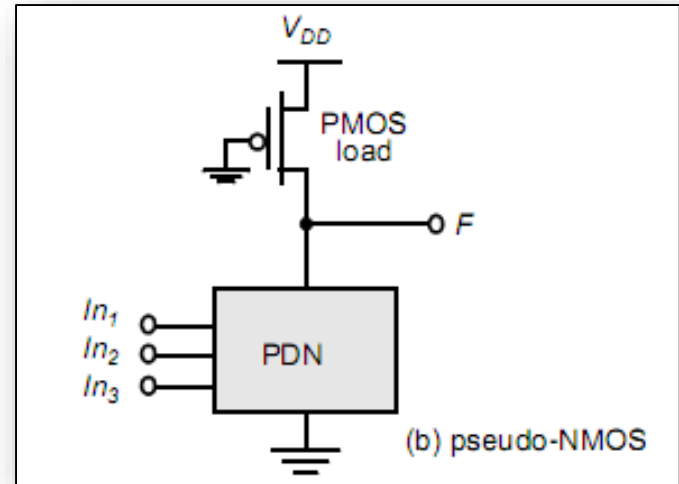
# Pseudo nMOS

- ❑ Using a *pMOS* in the *PUN*, we get a **Strong '1'** when the *PDN* is closed, so  $V_{OHmax} = V_{DD}$ .
- ❑ On the other hand, when the *PDN* is open, there is a “**fight**” between the *PDN* and the *pMOS load*.



# Pseudo nMOS

- ❑ To calculate  $V_{OLmin}$ , we will equate the *pMOS saturation current* with the *PDN current*, assuming that it consists of *nMOS* devices in *Linear Mode*.
- ❑ We will mark the drive strength of the *PDN* as  $k_{neq}$  and assume *short channel devices*\*:

$$I_{Dp} = k_p \left( (V_{DD} - |V_{Tp}|) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right) = I_{Dn} = k_{neq} \left[ (V_{DD} - V_{Tn}) V_{OL} - \frac{1}{2} V_{OL}^2 \right]$$

\*Calculate for long channel devices at home!



# Pseudo nMOS

- Making a few minor assumptions, we arrive at:

$$V_{OL} \approx \frac{k_p (V_{DD} - |V_{Tp}|) V_{DSAT}}{k_{neq} (V_{DD} - V_{Tn})} \approx \frac{\mu_p \cdot W_p}{\mu_n \cdot W_{neq}} \cdot V_{DSAT}$$

- So to get a **Low  $V_{OLmin}$** , we need the **pMOS** to be *much smaller* than the **equivalent width** of the **nMOS** network.
- Making the **pMOS** small means a *small charge current*, resulting in a large  **$t_{pLH}$** !

 


Figure 6.28 Voltage-transfer curves of the pseudo-NMOS inverter as a function of the PMOS size.

# Pseudo nMOS



- In addition, we get *static power dissipation* from the direct path between  $V_{DD}$  and  $GND$  when outputting a '0':

$$P_{low} = V_{DD} I_{low} \approx V_{DD} k_p \left( (V_{DD} - |V_{Tp}|) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

- Accordingly, *Pseudo nMOS* won't usually be used in *low power* or *high frequency* applications.
  
# Pseudo nMOS

- However, when *large fan-in gates* are needed, the reduced transistor count can be attractive.



# *VTC of Pseudo NMOS*

---

# Pseudo NMOS Characteristics Summary

## ❑ Small $\beta$ ratio (small pMOS, big PDN):


- » Lower VOL
- » Better Gain
- » Less static power
- » Fast  $t_{pHL}$

## ❑ But...

- » Slow  $t_{pLH}$
- » Bigger capacitive load
 
## ❑ In general:

- » N+1 Transistors
- » Only 1 NMOS load to previous stage
- » Make sure  $R_{PMOS}$  resistance at least  $4 \times R_{PDN}$



# 8.3

## 8.1 Ratioed Logic

## 8.2 Pseudo NMOS

## 8.3 LE of Pseudo NMOS




Now we can compare this logic family using our previously developed design methodology:

# LOGICAL EFFORT OF PSEUDO NMOS
 
# Pseudo-NMOS – Rising Edge

- $t_{pLH}$  is simply through the pMOS:  $t_{pLH} = 0.69 \cdot C_L \cdot R_{p,\min}$
- Let's look at the Logical Effort parameters of this transition:



$$R_{eq} = R_{p,\min}$$

$$C_G = \beta_n C_{g\min}$$

$$C_d = (\beta_n + 1) C_{d\min}$$

# Rising Edge Logical Effort

- Now it is straightforward to calculate the LE parameters.

$$p = \frac{R_{gate}}{R_{inv}} \cdot \frac{C_{d,gate}}{C_{d,min}}$$

$$LE = \frac{R_{gate}}{R_{inv}} \cdot \frac{C_{g,gate}}{C_{g,min}}$$

$$R_{eq} = R_{p,min}$$

$$C_G = \beta_n C_{g,min}$$


$$C_d = (\beta_n + 1) C_{d,min}$$

$$\longrightarrow p = \frac{R_{p,min}}{R_{p,min}/2} \cdot \frac{(\beta_n + 1) C_{d,min}}{3 C_{d,min}} = \frac{2}{3} (\beta_n + 1)$$

$$LE = \frac{R_{p,min}}{R_{p,min}/2} \cdot \frac{\beta_n C_{d,min}}{3 C_{d,min}} = \frac{2}{3} \beta_n$$

$$\text{for } \underline{\beta_n = 1}: \quad p = 4/3 \quad LE = 2/3$$
 
$$\text{for } \underline{\beta_n = 4}: \quad p = 10/3 \quad LE = 8/3$$





# Pseudo-NMOS – Falling Edge

□ But what about  $t_{pHL}$ ?

» Let's find the *Thevenin Equivalent*:

$$V_{Thevenin} = V_{DD} \frac{R_N}{R_N + R_P} \quad R_{Thevenin} = \frac{R_N \cdot R_P}{R_N + R_P}$$



» So we would expect:

$$t_{pHL} = 0.69 \cdot C_L \cdot R_{Thevenin}$$

» But the swing is  $V_{DD}/2$ , not  $V_{Thevenin}/2$

» So it actually takes a bit longer to discharge.

# Response on Falling edge

  


$$\frac{v_o(t)}{V_{DD}} = \frac{R_n}{R_n + R_p} + \left(1 - \frac{R_n}{R_n + R_p}\right) e^{-t/\tau}$$

□ The smaller  $R_{PUN}$ :

- » The smaller the swing, so it takes less time to reach  $0.5(V_{OH} - V_{OL})$
- » But the longer it takes to reach  $0.5V_{DD}$  !
 
# Falling Edge Logical Effort

- $t_{pHL}$  presents a new problem:
  - » Both the PUN and PDN are conducting.



$$R_{thevenin} = R_n \parallel R_p$$

*So Req is smaller than Rn?*


How could this be – the pmos is “fighting” the discharge...

It's because of the swing...

# Pseudo nMOS Logical Effort
 
## □ What is the actual R?

- » Available Current is the difference between PDN and PUN.
- » The current is approximately proportional to the resistance.



$$\frac{V_{DD}}{R_{eq}} \approx \frac{V_{DD}}{R_{PDN}} - \frac{V_{DD}}{R_{PUN}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_{n,min}/\beta_n} - \frac{1}{R_{p,min}} \Rightarrow R_{eq} \approx \frac{R_{n,min}}{\beta_n - 1/2}$$

for  $\beta_n=1$ :  $R_{eq} = 2R_{n,min}$

for  $\beta_n=4$ :

$$R_{eq} = R_{n,min}/3.5 > R_{n,min}/\beta_n$$

*So Req is bigger than Rn?*  
That makes more sense...

# Pseudo nMOS Logical Effort

□ So the parameters for pull down:

$$p = \frac{R_{gate}}{R_{inv}} \cdot \frac{C_{d,gate}}{C_{d,min}}$$

$$LE = \frac{R_{gate}}{R_{inv}} \cdot \frac{C_{g,gate}}{C_{g,min}}$$

$$R_{eq} = \frac{R_{nmin}}{\beta_n - 1/2} \longrightarrow p = \frac{R_{nmin}}{(\beta_n - 0.5)/R_{nmin}} \cdot \frac{(\beta_n + 1)C_{d,min}}{3C_{d,min}} = \frac{1}{3} \left( \frac{\beta_n + 1}{\beta_n - 0.5} \right)$$


$$C_G = \beta_n C_{g,min}$$

$$C_d = (\beta_n + 1)C_{d,min}$$

$$LE = \frac{R_{nmin}}{(\beta_n - 0.5)/R_{nmin}} \cdot \frac{\beta_n C_{g,min}}{3C_{g,min}} = \frac{\beta_n}{3(\beta_n - 0.5)}$$

$$\text{for } \beta_n = 1: \quad p = 4/3 \quad LE = 2/3$$
 
$$\text{for } \beta_n = 4: \quad p = 10/21 \quad LE = 8/21$$



# Pseudo nMOS Logical Effort - Summary

## □ So to summarize:

- » With  $\beta=1$  (high  $V_{OL}$ ), we got:

$$t_{pLH} : p = \frac{4}{3} \quad LE = \frac{2}{3} \quad t_{pHL} : p = \frac{4}{3} \quad LE = \frac{2}{3}$$

- » Our LE is **LOWER** than an inverter!
- » But don't forget we have depleted noise margins and we have static power...
- » With  $\beta=4$  (more realistic), we got:  
$$t_{pLH} : p = \frac{10}{3} \quad LE = \frac{8}{3} \quad t_{pHL} : p = \frac{10}{21} \quad LE = \frac{8}{21}$$
- » Our HL transition has much better performance than CMOS!
- » But the LH transition is much worse.

# *Last Lecture*

---

□ Pseudo NMOS

# *Last Lecture*

---

□ Rising Edge (easy):



# *Last Lecture*

---

- ❑ Falling Edge (“complicated”):

# Another Example

□ What if we were to give the pMOS a long L?

» Say we want  $\beta=4$ , so we would choose  $W_p/L_p = W_{min}/4L_{min}$

$$C_g = C_{g\min}$$

$$C_d = 2C_{d\min}$$

$$R_{eqLH} = 4R_p = 8R_{eq}$$

$$I_{HL} = I_n - I_p/4 = 7/8 I_{eq}$$

$$R_{eqHL} \propto 1/I_{eq} \Rightarrow 8/7 R_{eq}$$

$$LH : p_{LH} = 8 \cdot \frac{2}{3} = 16/3 \quad LE_{LH} = 8 \cdot \frac{1}{3} = 8/3$$

$$HL : p_{HL} = \frac{8}{7} \cdot \frac{2}{3} = 16/21 \quad LE_{HL} = \frac{8}{7} \cdot \frac{1}{3} = 8/21$$

