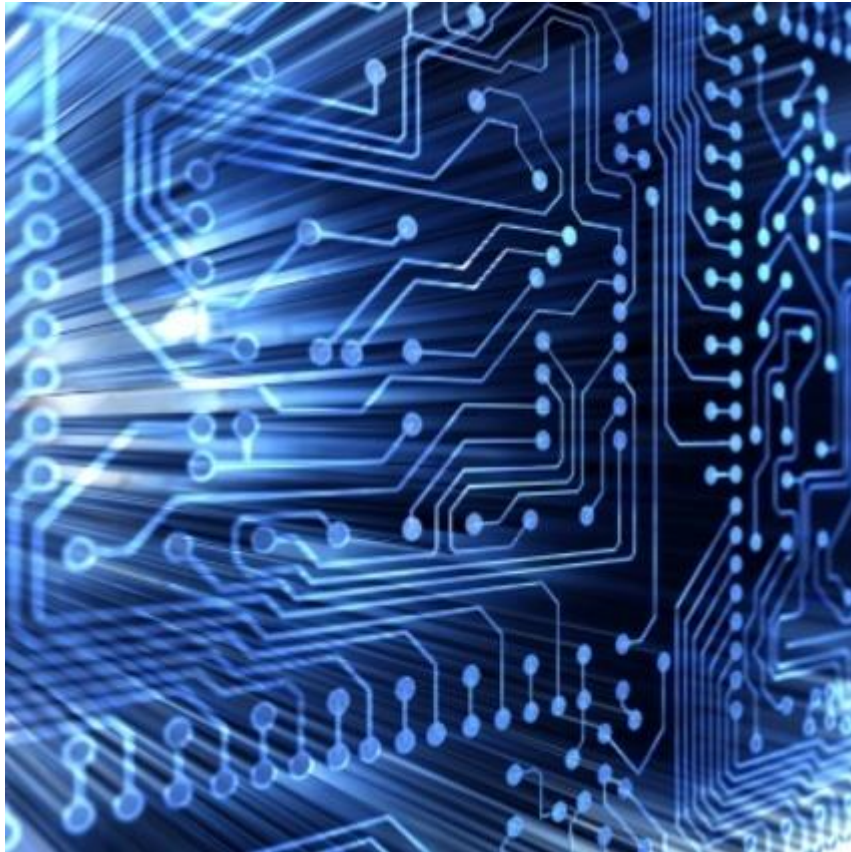




Digital Microelectronic Circuits

(361-1-3021)

Presented by: Adam Teman


Lecture 12:

Sequential Logic Circuits and Memories

Last Lecture

□ Dynamic Logic

 - » Features and Problems
- » Domino Logic



This Lecture

- ❑ An introduction to sequential circuits and semiconductor memory, focusing on the circuit level implementation of basic gates and cells.
- ❑ A much more in-depth study of these circuits will be given in Introduction to VLSI.

What will we learn today?

1 1.1 The Latch



1 1.2 The Flip Flop

1 1.3 Read Only Memory

1 1.4 SRAM


1 1.5 DRAM

Sequential Logic

  

Memory Hierarchy

Volatility

 

11.1

11.1 The Latch

11.2 The Flip Flop

11.3 Read Only Memory

11.4 SRAM


11.5 DRAM

The basic sequential timing element is the

LATCH

Transparent Latch

 
- ◆ Latch: level-sensitive
clock is low - hold mode
clock is high - transparent



Clk	D	Q
0	0	Hold
0	1	Hold
1	0	0
1	1	1



Basic Static Latch

Clk	D	Q
0	0	Hold
0	1	Hold
1	0	0
1	1	1


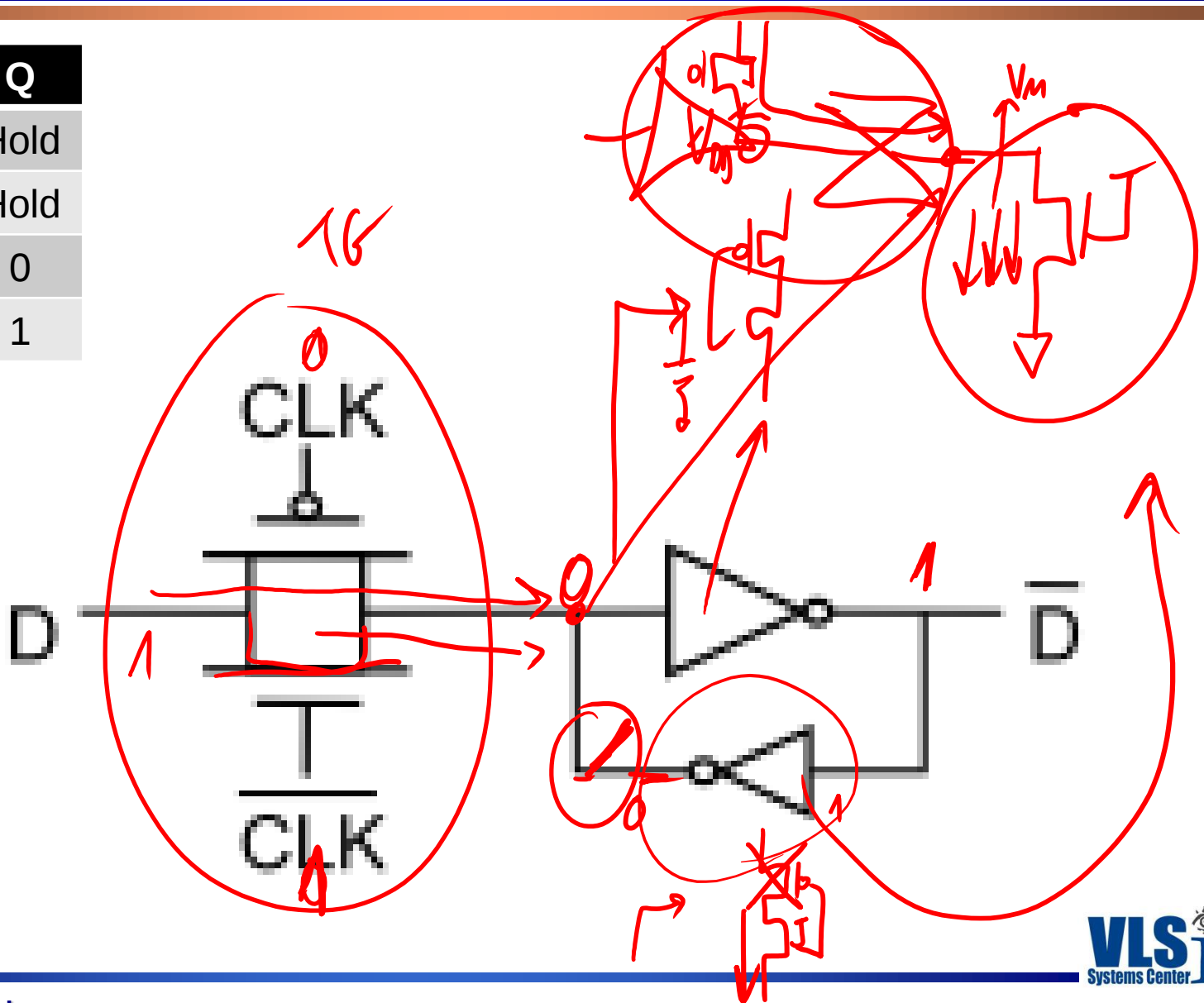


Feedback Mux Latch


Clk	D	Q
0	0	Hold
0	1	Hold
1	0	0
1	1	1

  

Simple Dynamic Latch

  

C²MOS

 



11.2

11.1 The Latch

11.2 The Flip Flop

11.3 Read Only Memory

11.4 SRAM

11.5 DRAM


The most important timing element in synchronous systems is the

FLIP FLOP

Flip Flop = Register


- Register: edge-triggered stores data when clock rises

Latch

 

Clk	D	Q
0 → 1	0	0
0 → 1	1	1
0	X	Hold
1	X	Hold


Master-Slave (Edge-Triggered) Register

 

Two opposite latches trigger on edge
Also called master-slave latch pair


Master-Slave Register

Multiplexer-based latch pair

 


Clock load – 8 transistors

C2MOS Register

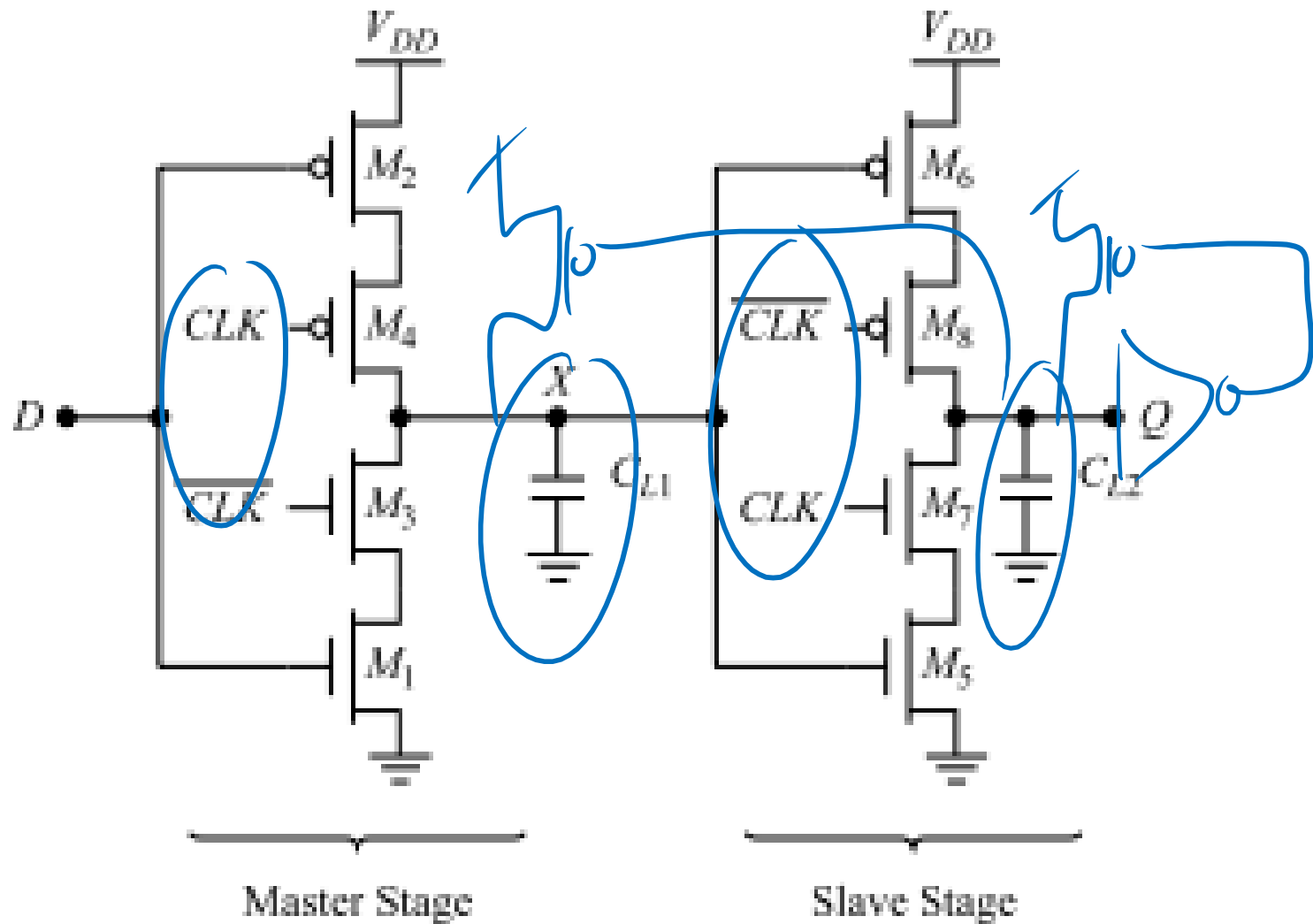

Pulse Triggered Register

Pulse-Triggered Latch

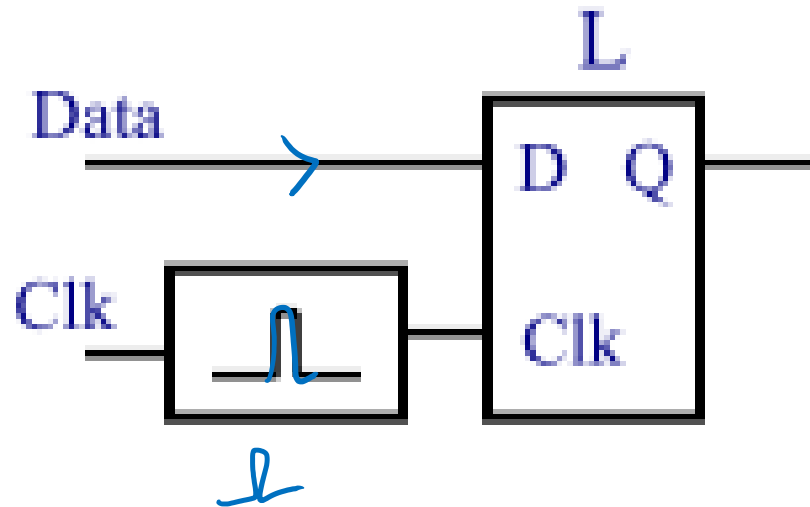

11.3


11.1 The Latch

11.2 The Flip Flop

11.3 Read Only Memory

11.4 SRAM


11.5 DRAM

 



Now we are ready to look at the basic memory array:

READ ONLY MEMORY


Memory Architecture

 


Read-Only Memory Cells

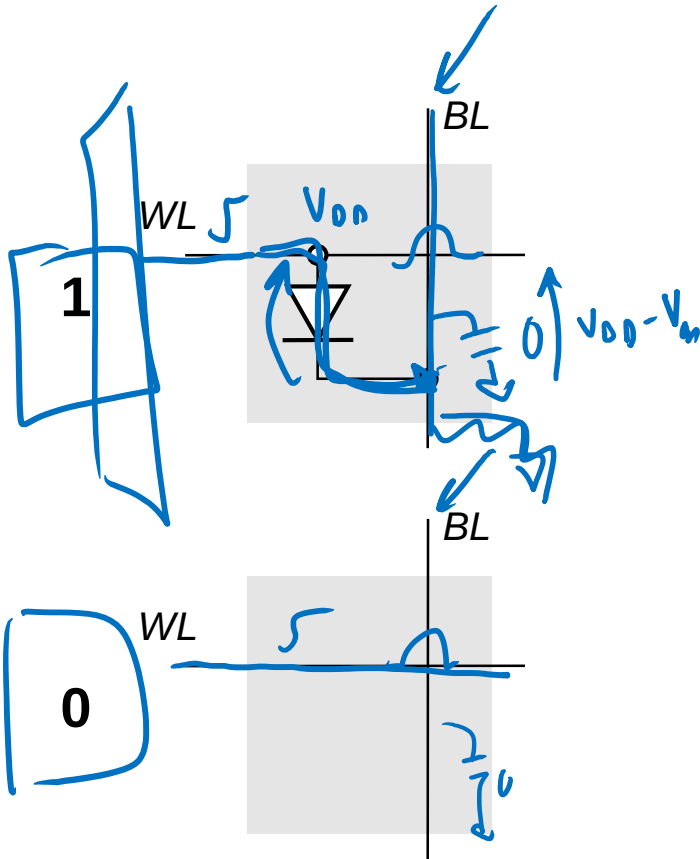 

Diode ROM

 


MOS ROM 1

 


MOS ROM 2


MOS NOR ROM

 

Precharged MOS NOR ROM

 

MOS NAND ROM

 

All word lines high by default with exception of selected row

11.4


11.1 The Latch

11.2 The Flip Flop

11.3 Read Only Memory

11.4 SRAM

11.5 DRAM

 

Most embedded memories are implemented with

STATIC RANDOM ACCESS MEMORY

Random Access Memories

❑ STATIC (SRAM)

Data stored as long as supply is applied

Larger (6 transistors/cell)

Fast

Differential (usually)




❑ DYNAMIC (DRAM)

Periodic refresh required


Smaller (1-3 transistors/cell)

Slower

Single Ended


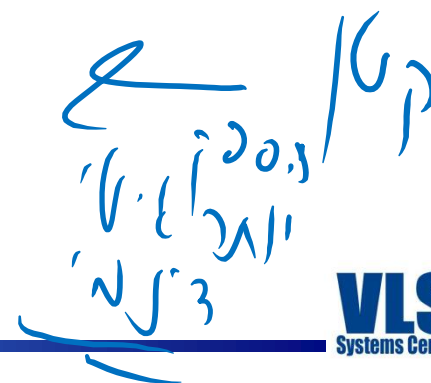


Basic Static Memory Element

 


- If D is high, $\overline{D}$ will be driven low
 - Which makes D stay high
- Positive feedback

Positive Feedback: Bi-Stability

  


Memory Cell

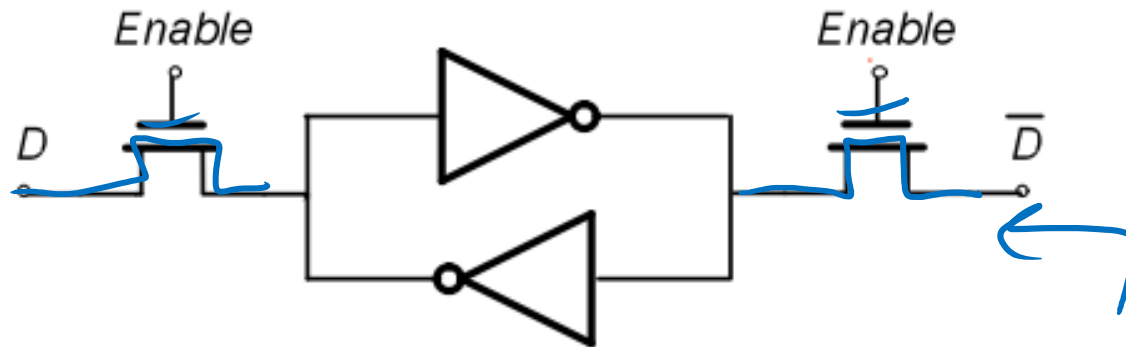


Complementary data values are written (read) from two sides


6-transistor CMOS SRAM Cell

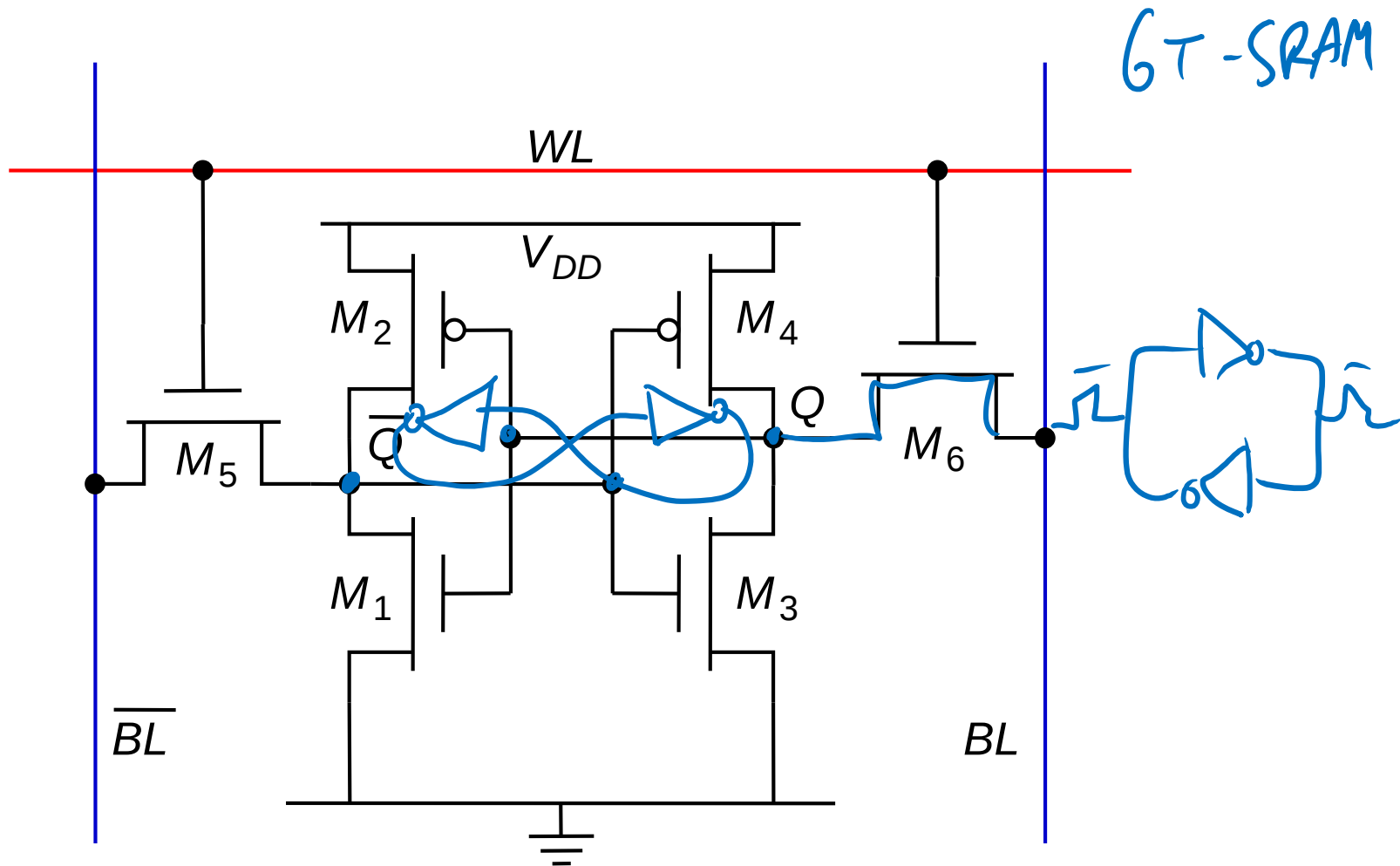

SRAM Operation - Read

 

SRAM Operation - Write

 

11.5

11.1 The Latch

11.2 The Flip Flop

11.3 Read Only Memory


11.4 SRAM

11.5 DRAM

How about reducing the number of transistors to achieve high density...


DYNAMIC RANDOM ACCESS MEMORY

3-Transistor DRAM Cell

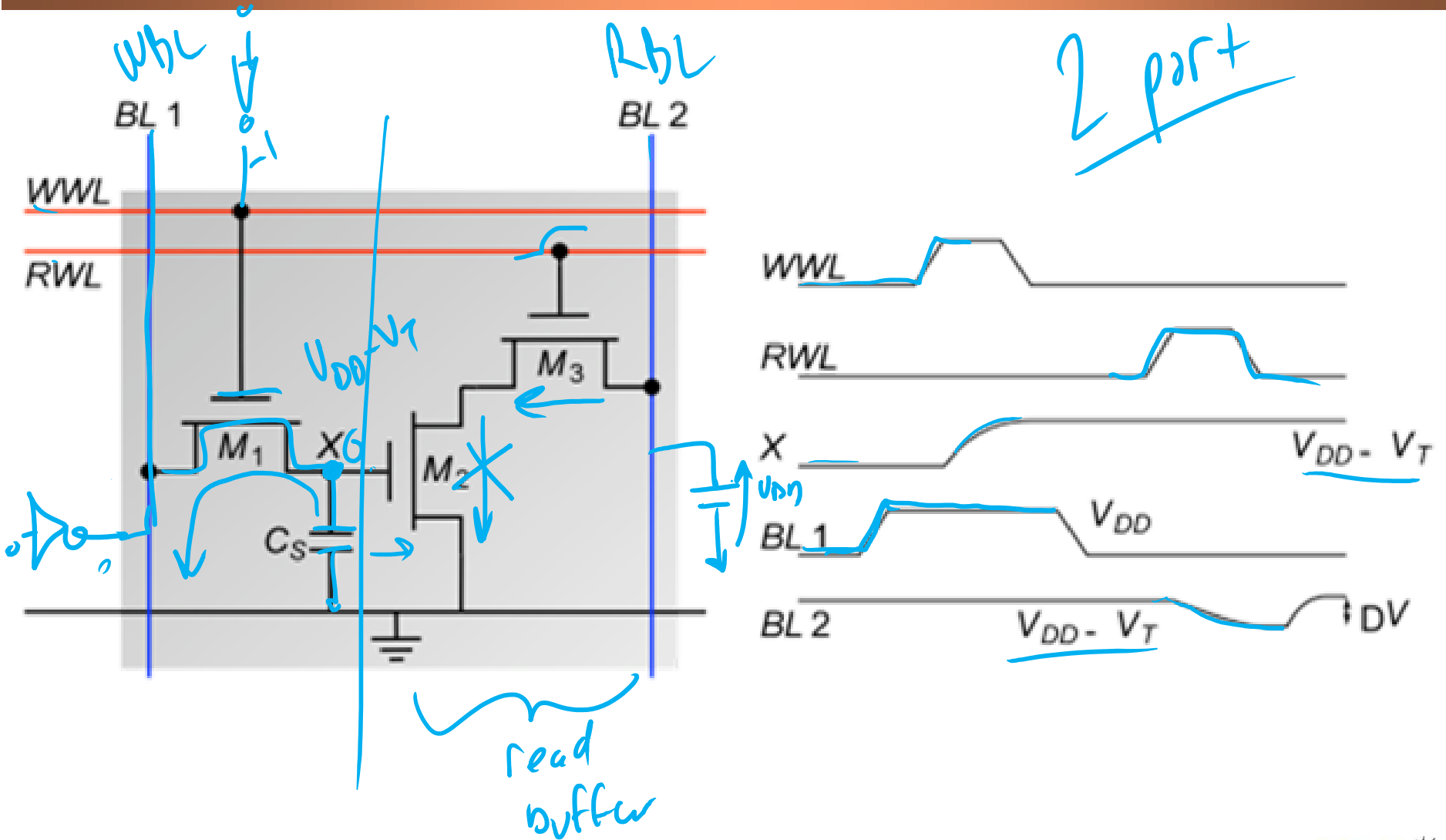


1-Transistor DRAM Cell

65ms

 

1-Transistor DRAM Cell

 

$$Q_{initial} = V_{\text{precharge}} C_{BL} + V_S C_S$$

$$Q_{final} = V_{final} (C_{BL} + C_S)$$

for $V_{\text{precharge}} = V_{DD}/2$:

$$V_{final}('0') = \frac{V_{DD}}{2} \frac{C_{BL}}{(C_{BL} + C_S)}$$

$$V_{final}('1') = \frac{(V_{DD} - V_T) C_S + 0.5 V_{DD} C_{BL}}{(C_{BL} + C_S)}$$