

Digital Integrated Circuits

(83-313)

Lecture 7:

Designing Sequential Logic Circuits



Emerging Nanoscaled
Integrated Circuits and Systems Labs

Prof. Adam Teman
27 April 2021


The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



Disclaimer: This course was prepared, in its entirety, by Adam Teman. Many materials were copied from sources freely available on the internet. When possible, these sources have been cited; however, some references may have been cited incorrectly or overlooked. If you feel that a picture, graph, or code example has been copied from you and either needs to be cited or removed, please feel free to email adam.teman@biu.ac.il and I will address this as soon as possible.

Sequential Logic

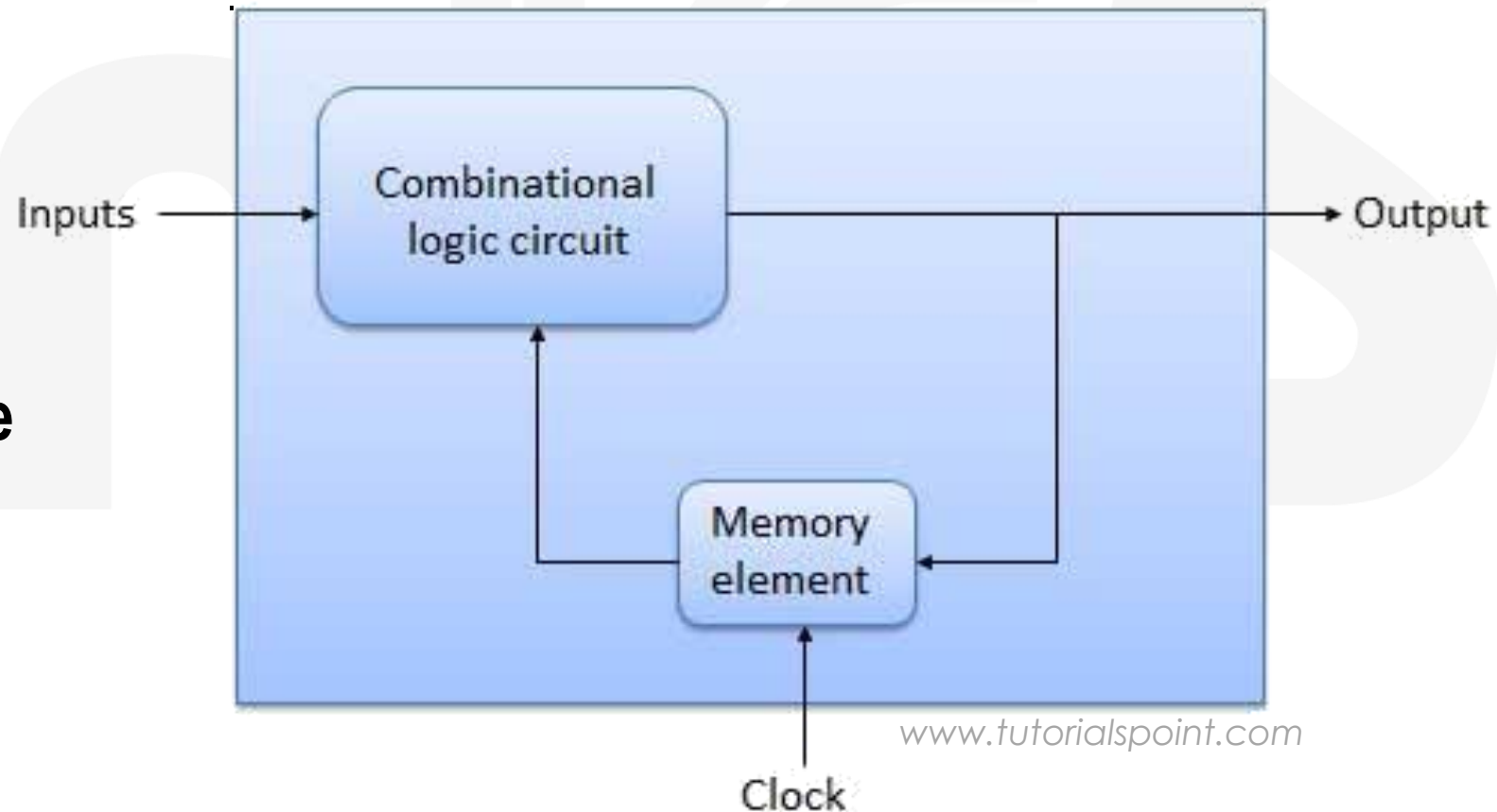- Sequential circuits are a function of both the **current** state and the **previous** state.
- In other words, they have **memory**.
- The majority of sequential circuits are **Synchronous**, using a clock to synchronize the logic paths.



Lecture Content

Why use Sequential Logic?

Sequential Logic Elements

Timing Parameters of
Sequential Elements

Other Flip Flop
Implementations

Basic Timing Constraints

Static Timing Analysis
Example

Why use Sequential Logic?

Explanation through example


- We will look at two examples:
 - An **accumulator circuit**, where sequential methods are essential to **eliminate races**.
 - A **pipelined system**, where sequential methods **improve throughput**.

What would happen if there were no traffic lights?



Accumulator Example

 - An accumulator is a register that sums a list of numbers. Therefore, it feeds back the output back to the input.
- Without a register, there would be the possibility that races would occur, causing erroneous outputs.
- We need to delay the output until the original calculation is finished.






Accumulator Example

- It is essential to use sequential logic when paths have **different delays** but **need to converge** together.
- We always have to **slow** our **fast paths** down so they arrive along with our **slowest path**.
- If we could make all paths have **equal delays**, we wouldn't need sequential logic, but this is really hard (almost impossible) to do.


Laundry Example

   - Small laundry has one washer, one dryer and one operator, it takes **90 minutes** to finish one load:
- Washer takes **30 minutes**
- Dryer takes **40 minutes**
- “Operator folding” takes **20 minutes**



Sequential Laundry

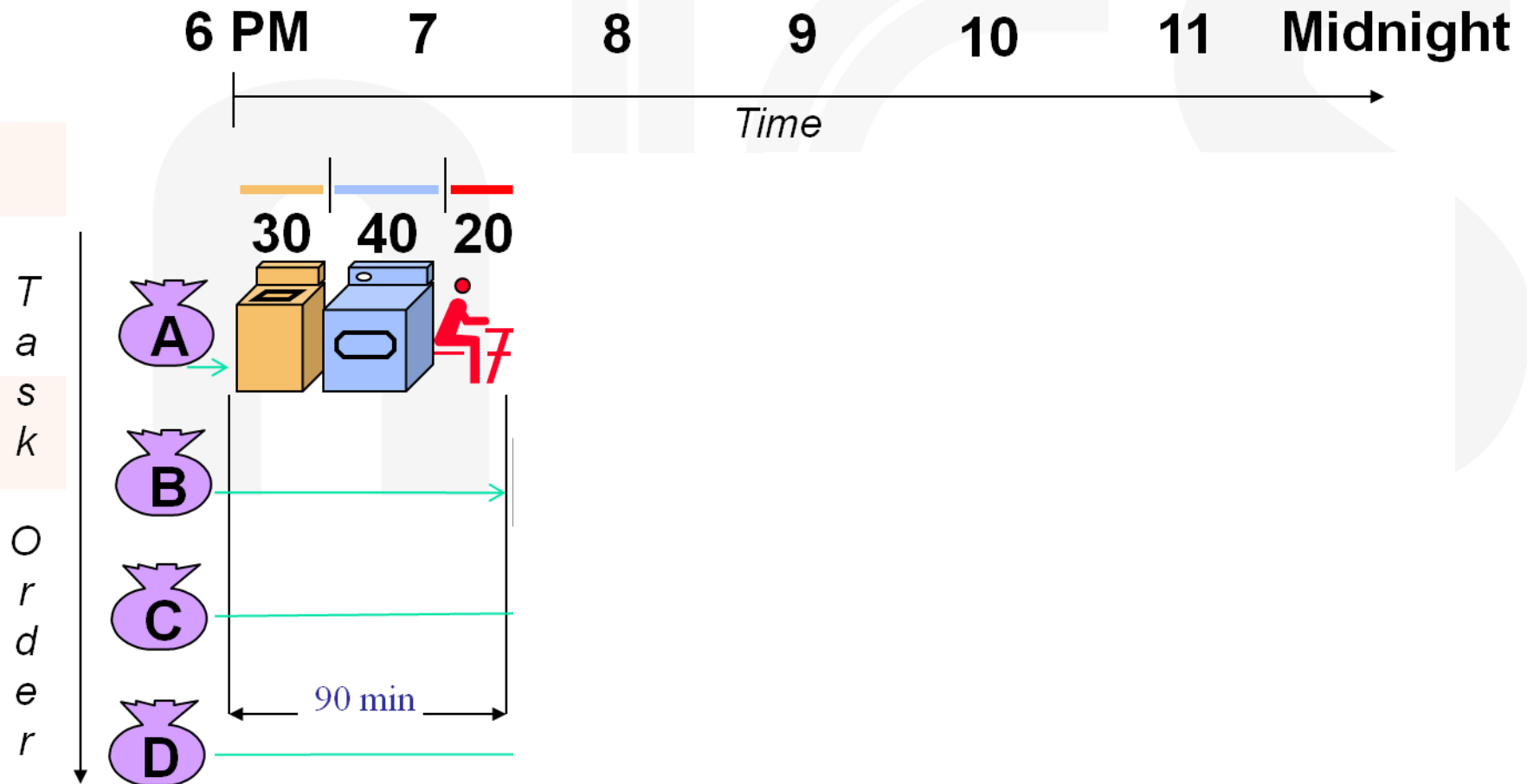- It takes **90 minutes** to finish one load.
- The process is sequential.




- Sequential laundry takes **6 hours** for 4 loads.

Pipelined Laundry


- Every 40 minutes a new load starts and a new load ends.

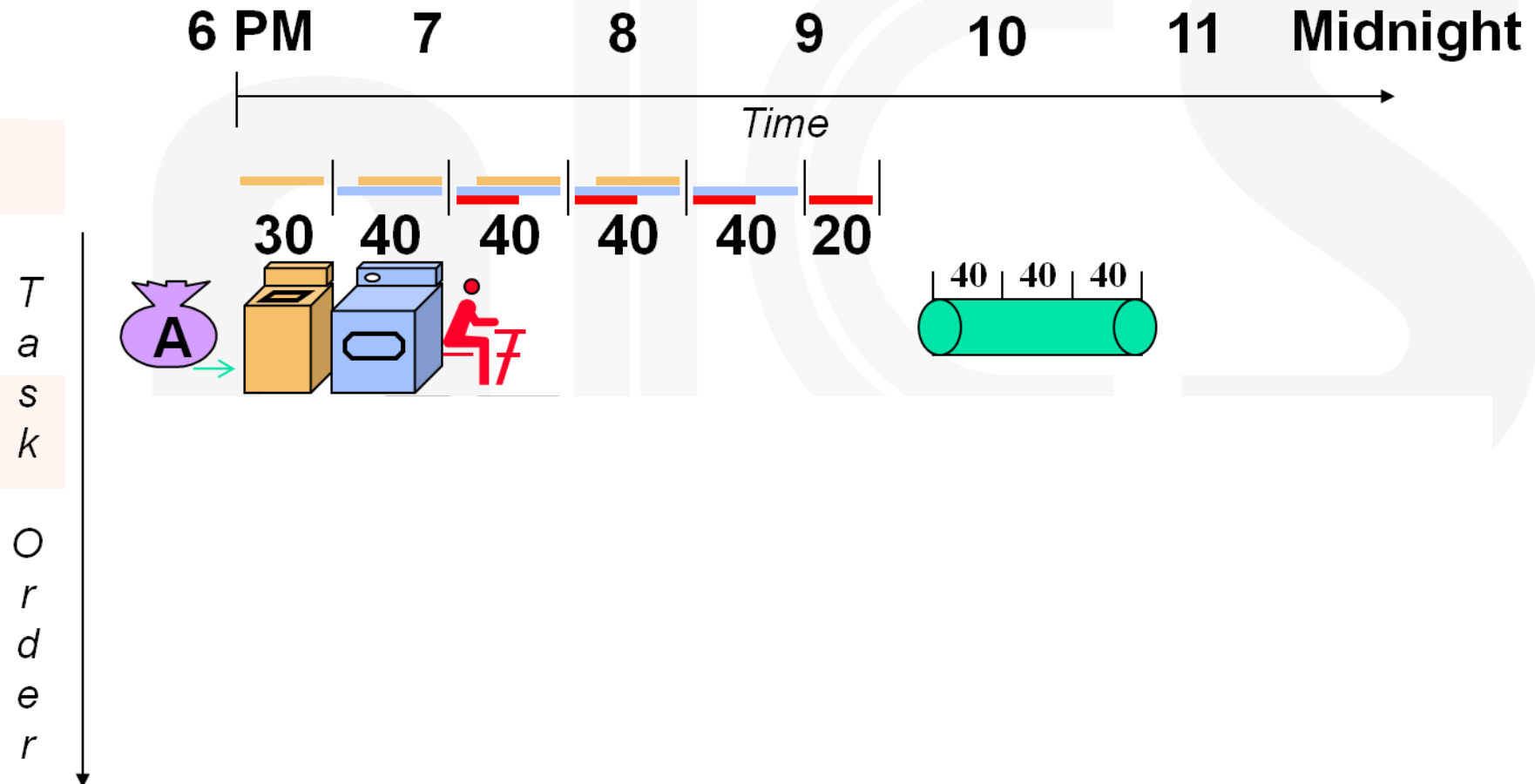- Pipelined laundry takes 3.5 hours for 4 loads




Pipelining Data

 - If it takes **10 time units** to process an instruction, we could perform **one instruction every 10 time units**:



 
- But if we divide the process into **5 tasks** that take **2 time units** each:



- We can start a **new instruction** every **2 time units**.
- And after filling the pipe, we **finish an instruction** every **2 units**.


Pipelining Data

 - But some stages may be **faster** than others, so we need to hold the input to each stage constant until the **previous stage is done**.
- We achieve this by adding a **register** in between the stages.



- So by using a pipeline, we can make our **slowest** path shorter and therefore **reduce the delay** between actions.
- All data paths are built using a pipeline of some sort, either to **eliminate races** or to **increase throughput**.

Classic 5-Stage RISC Pipeline

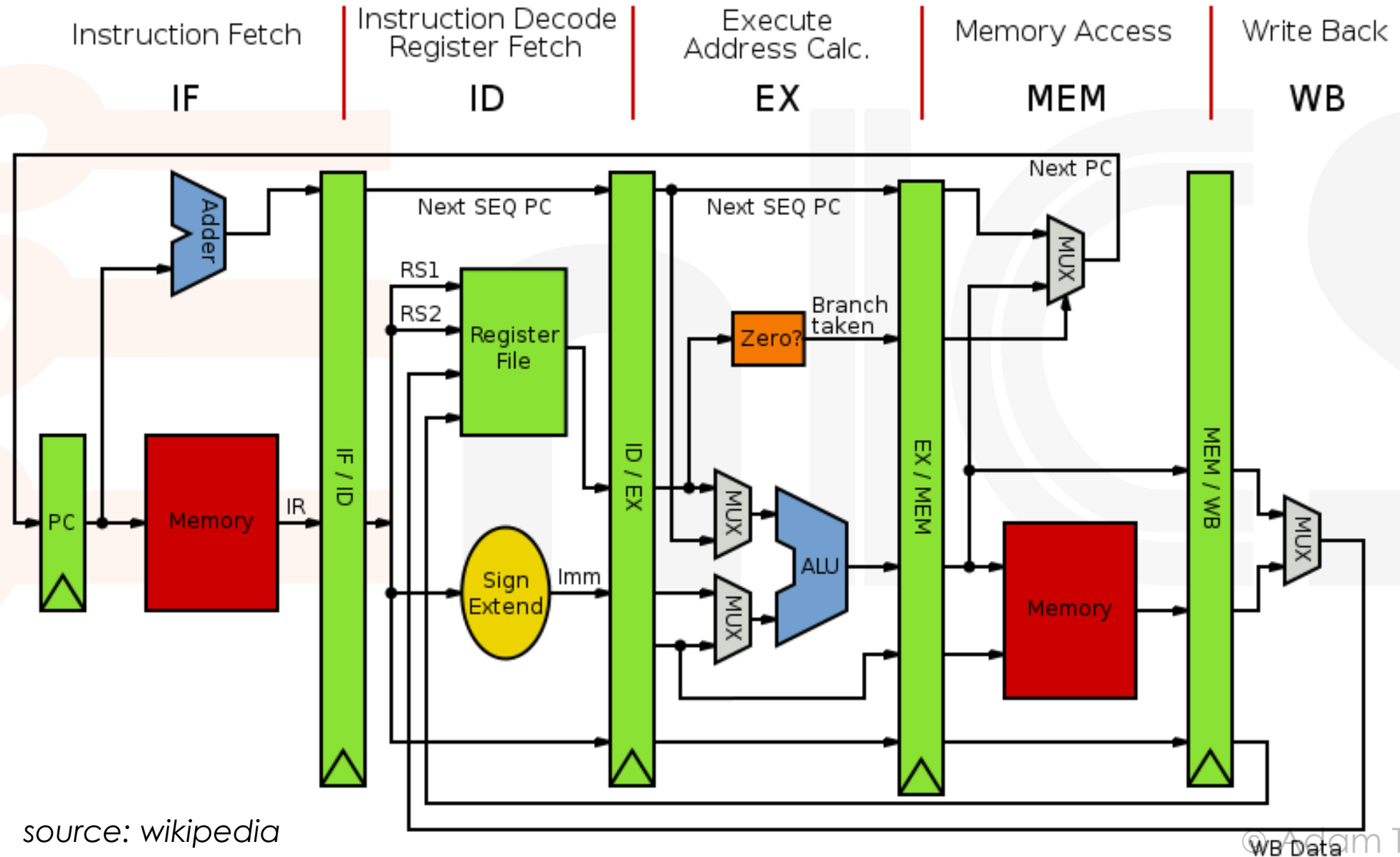

source: wikipedia

Sequential Logic Elements

Naming Conventions


- In our course we relate to **registers** as follows:

- a **latch** is level sensitive

- a **flip-flop** is edge-triggered


- There are many different naming conventions

- For instance, many books call any bi-stable element a **flip-flop** (such as an SR Latch)
- However, this leads to confusion, so we will use the convention above (as used in industry).

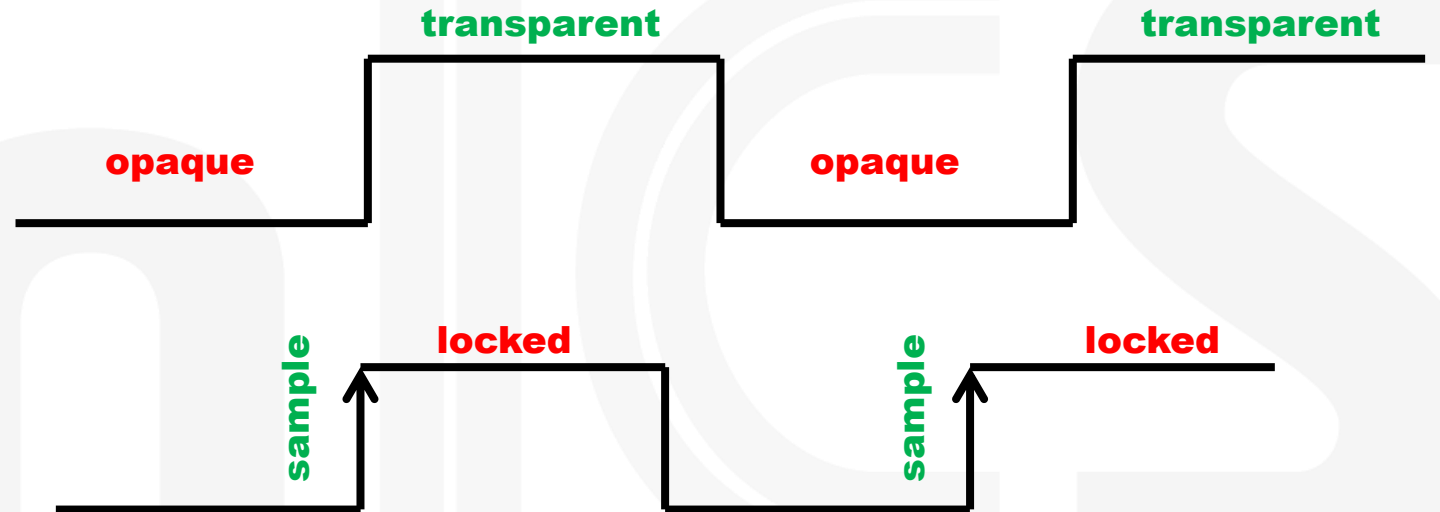

Latch Vs. Register


- During high clock phases, a **latch** is transparent, *latching* the input on the **falling edge**.
- However, a **Flip Flop** only *samples* the input on the **rising edge**.

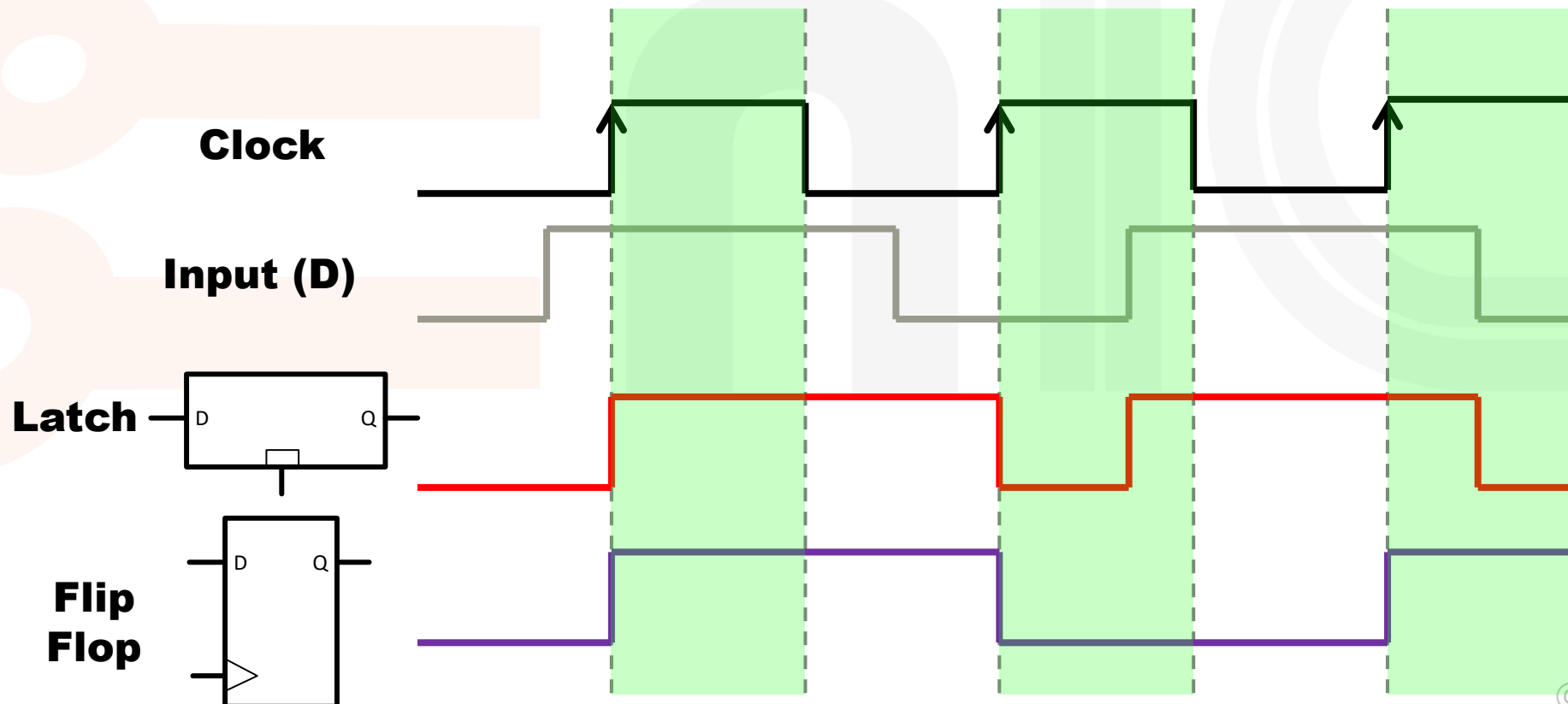

Latch Vs. Register


- 3 main options for sequential timing:

- Using Flip-Flops
- Using Transparent Latches
- Using Pulsed Latches

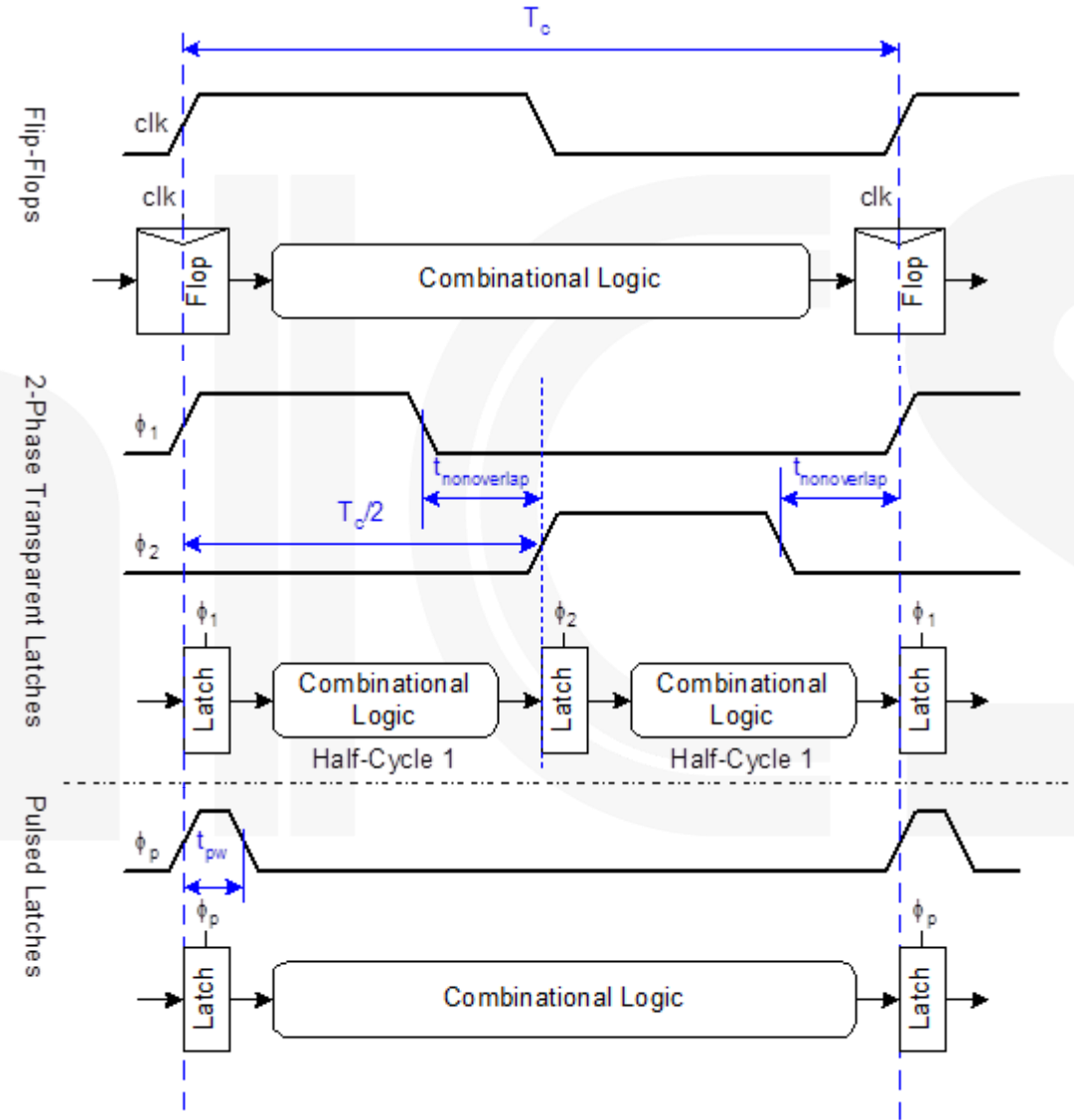


Static Vs. Dynamic Latch

 - A *static latch* stores its output in a static state
- A *dynamic latch* uses temporary capacitance to store its state.
- As with logic, this provides a trade-off between area, speed and reliability.



Static Latch

 


Dynamic Latch


Static Vs. Dynamic Latch

- Some basic implementations of static and dynamic latches.

Static

 


Dynamic

 



Ratioed vs. Non-Ratioed Latch

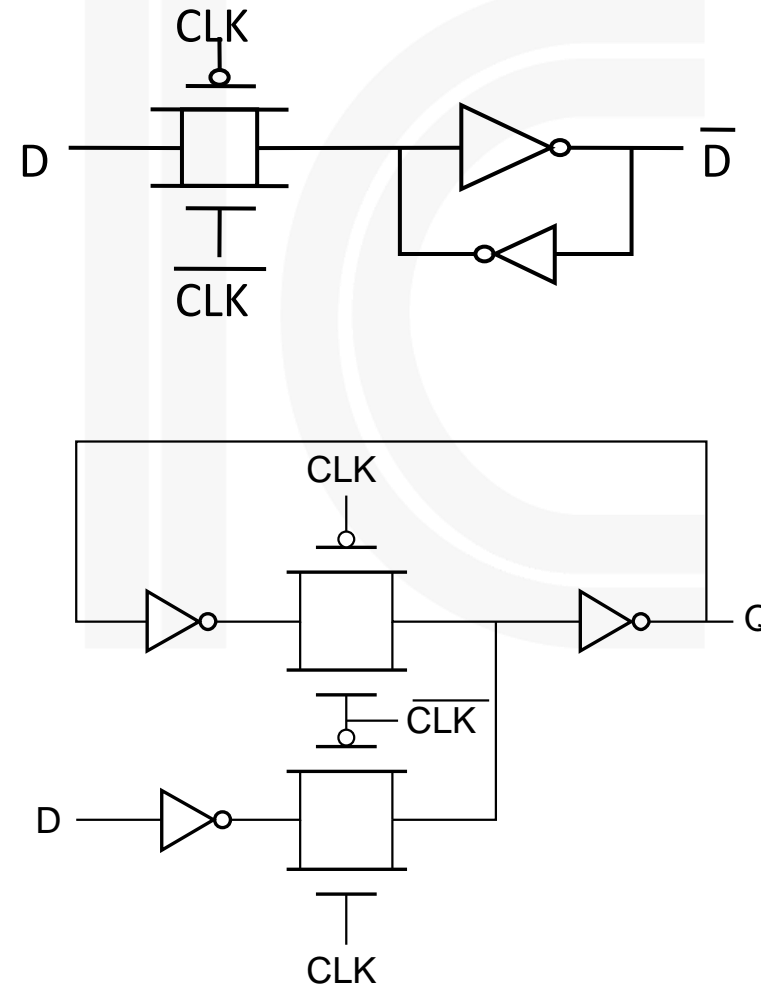- **A static latch can be made by using a feedback inverter.**
 - The TG (with the driver before it) must overcome the feedback inverter to write into the latch.
- **But it is usually more robust to create a mux-based non-ratioed latch.**
 - At the expense of size.





Making a Flip Flop

  - Conceptually, we can create an *edge triggered flip-flop* by combining two *opposite polarity latches*:




Master-Slave (Edge-Triggered) Register

 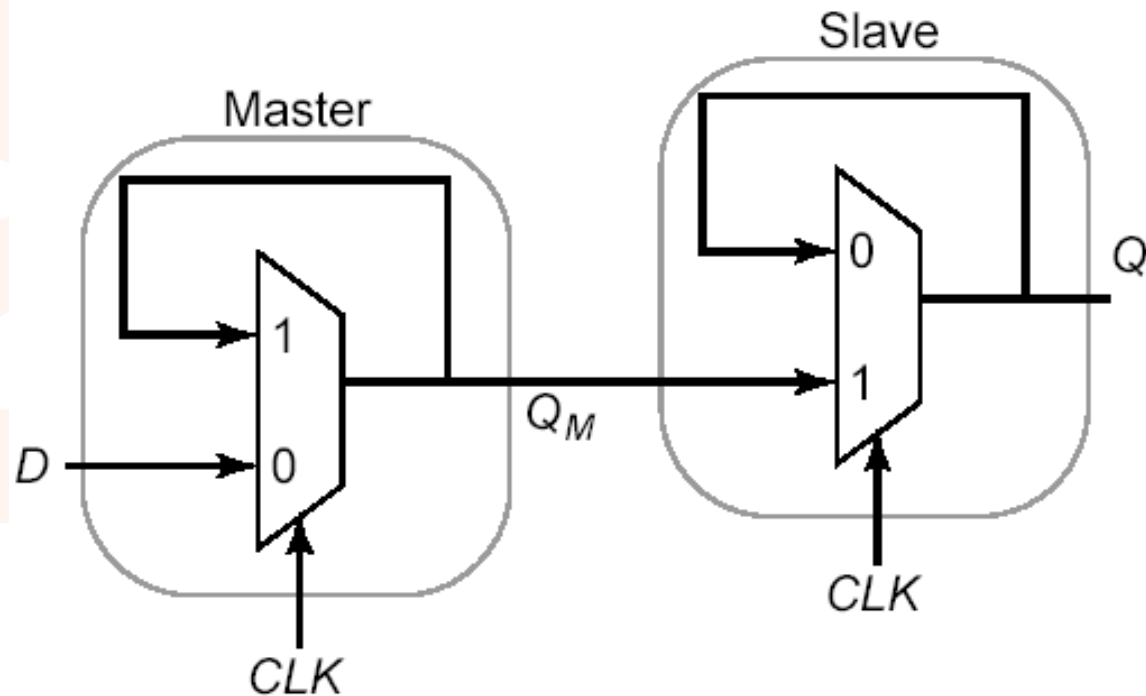- Two opposite latches trigger on edge
- Also called **master-slave** latch pair



Master-Slave Register


- Multiplexer-based latch pair

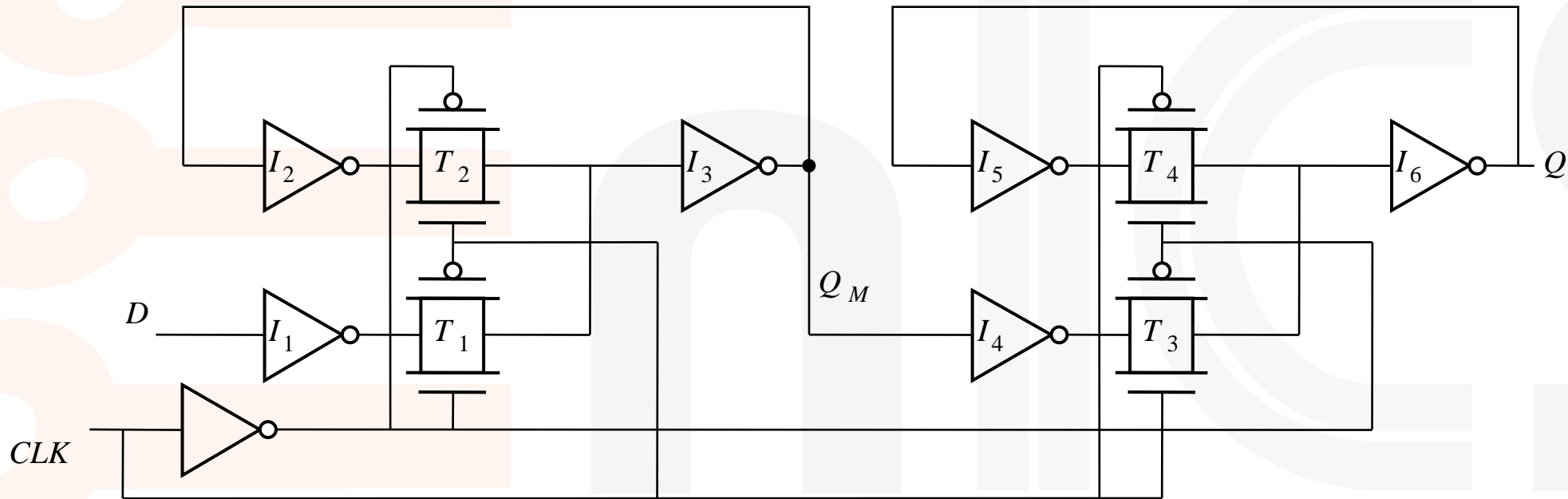


- How many *transistors* make up this flip-flop?
- What is its *clock load*?

Resettable Flip Flops

Asynchronous Set/Reset Flip-Flop


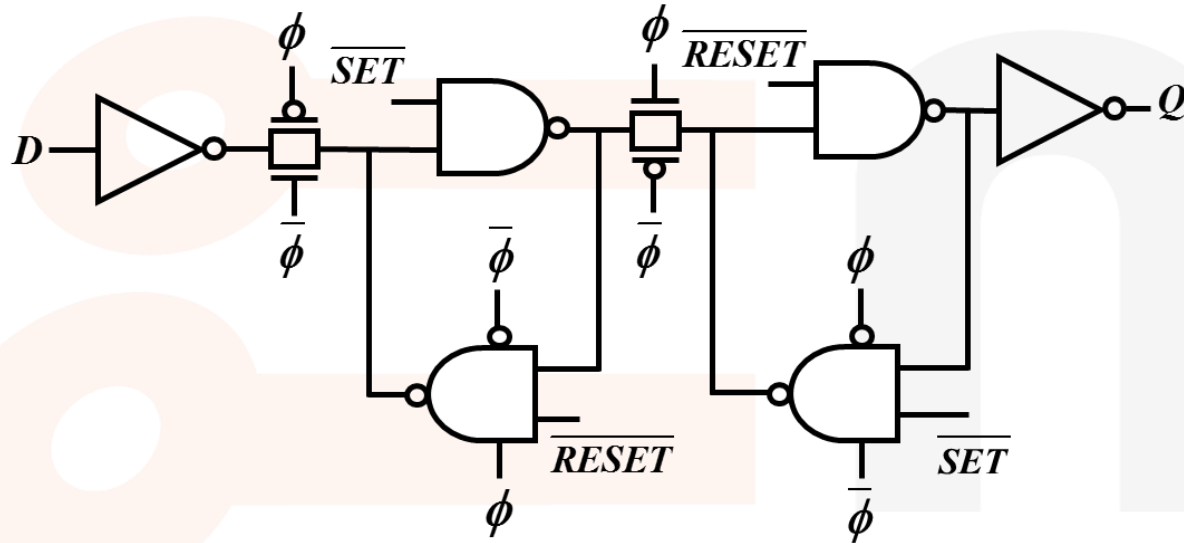


Synchronous Reset Flip-Flop

 

Timing Parameters of Sequential Elements

Timing Definitions

 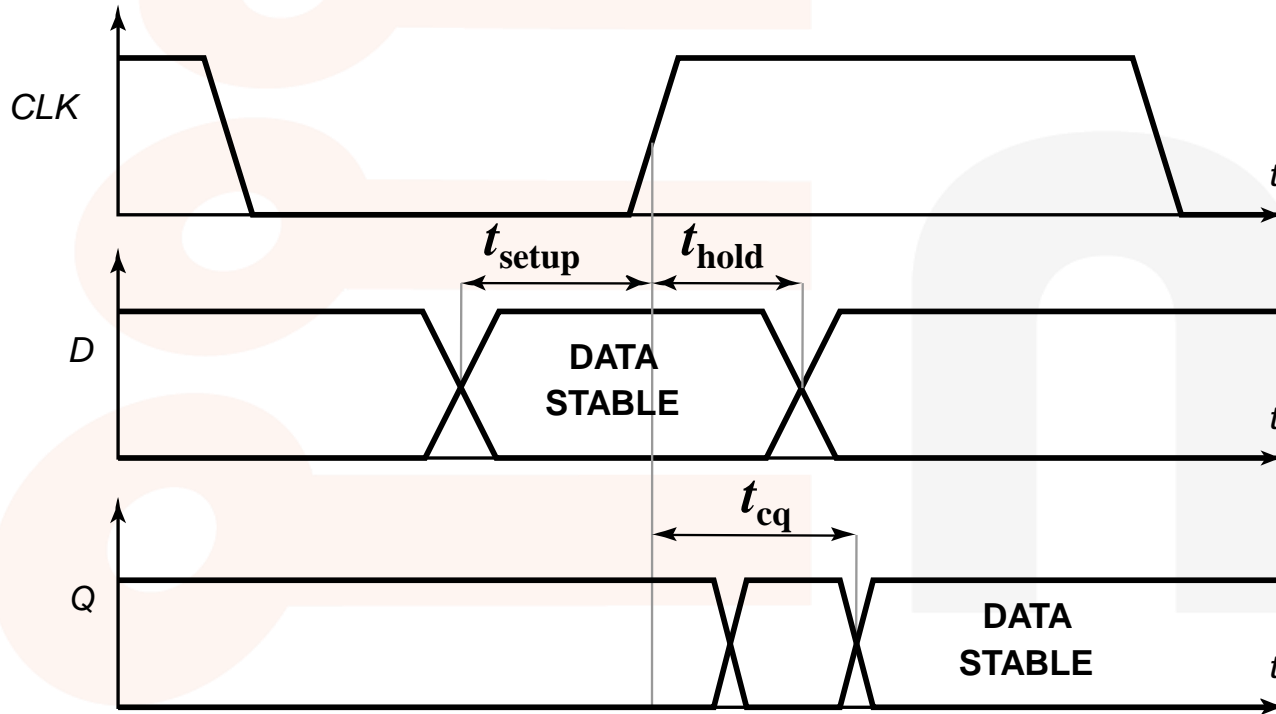



t_{cq} – propagation delay

t_{setup} – setup time

t_{hold} – hold time


Clk-Q Delay - t_{cq}

  - t_{cq} is the time from the clock edge until the data appears at the output.
- The t_{cq} for rising and falling outputs is different.





Mux based FF – t_{cq} Calculation

 - During low clock edge, data traverses slave and “waits” for the clock at pass gate input.
- When clock rises, data has to go through pass gate and inverter.



$$t_{cq} = T_3 + I_6$$

Timing Definitions

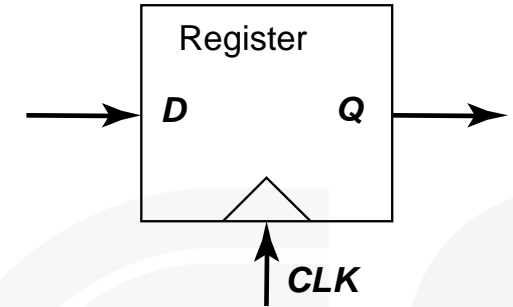 


t_{cq} – propagation delay

t_{setup} – setup time

t_{hold} – hold time


Setup Time - t_{setup}

 - **Setup time** is the time the data has to arrive *before the clock* to ensure correct sampling.



Mux based FF – t_{setup} Calculation

 
- Before clock edge, data should have propagated to the latching pass gate, or else data will be restored to the previous state.




$$t_{\text{setup}} = I_1 + T_1 + I_3 + I_2 = T + 3I$$

Timing Analysis - Setup Time

 
- To obtain the setup time of the register while using SPICE, we progressively skew the input with respect to the clock edge until the circuit fails.




 
(a) $T_{\text{setup}} = 0.21 \text{ nsec}$



 (b) $T_{\text{setup}} = 0.20 \text{ nsec}$



Timing Definitions

 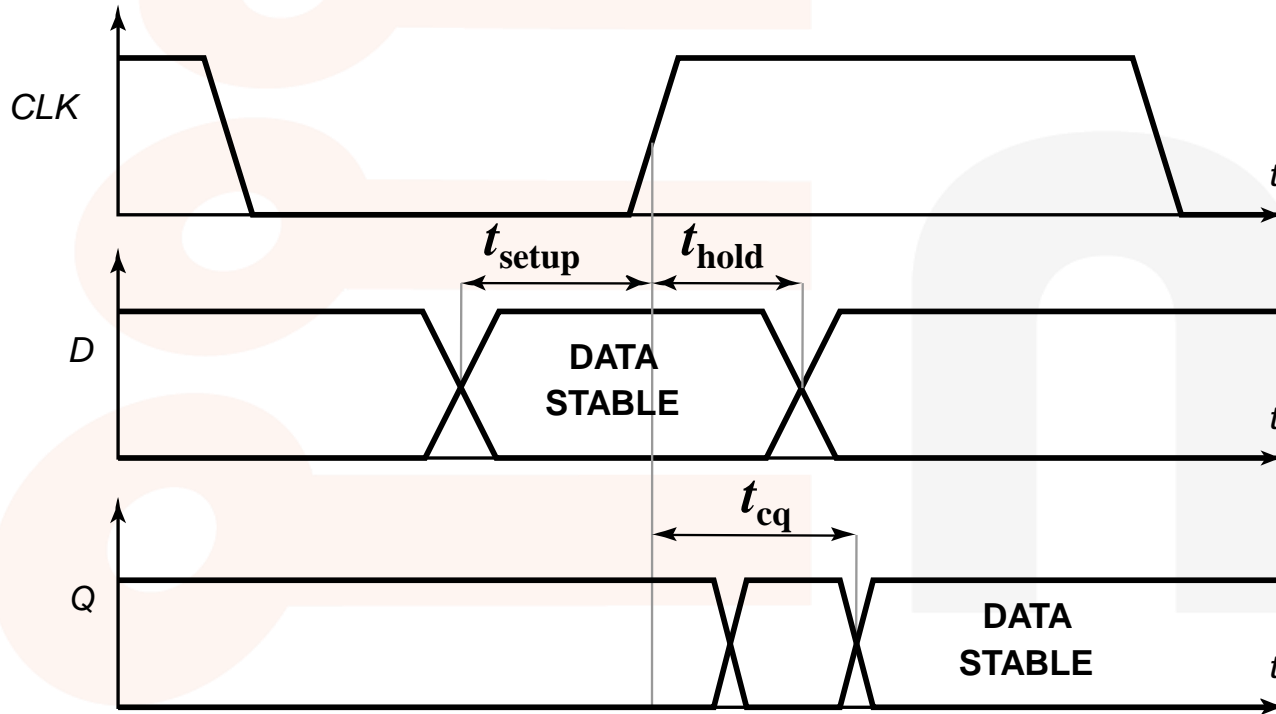


t_{cq} – propagation delay

t_{setup} – setup time

t_{hold} – hold time

Hold Time - t_{hold}

 
- Hold time is the time the data has to be stable *after the clock* to ensure correct sampling.



- Often (optimally), Hold Time is *negative*!


Mux based FF – t_{hold} Calculation

 - When the clock rises, T_1 closes, latching the data at the output of I_1 .
- Therefore, any changes made $t_{\text{pd}}(I_1)$ before the clock will not traverse.
- The hold time is $-t_{\text{pd}}(I_1)$




$$t_{\text{hold}} = -I_1$$

Characterizing Timing

 

Register

 


Latch

Other Flip Flop Implementations




Problem – Clock Overlap

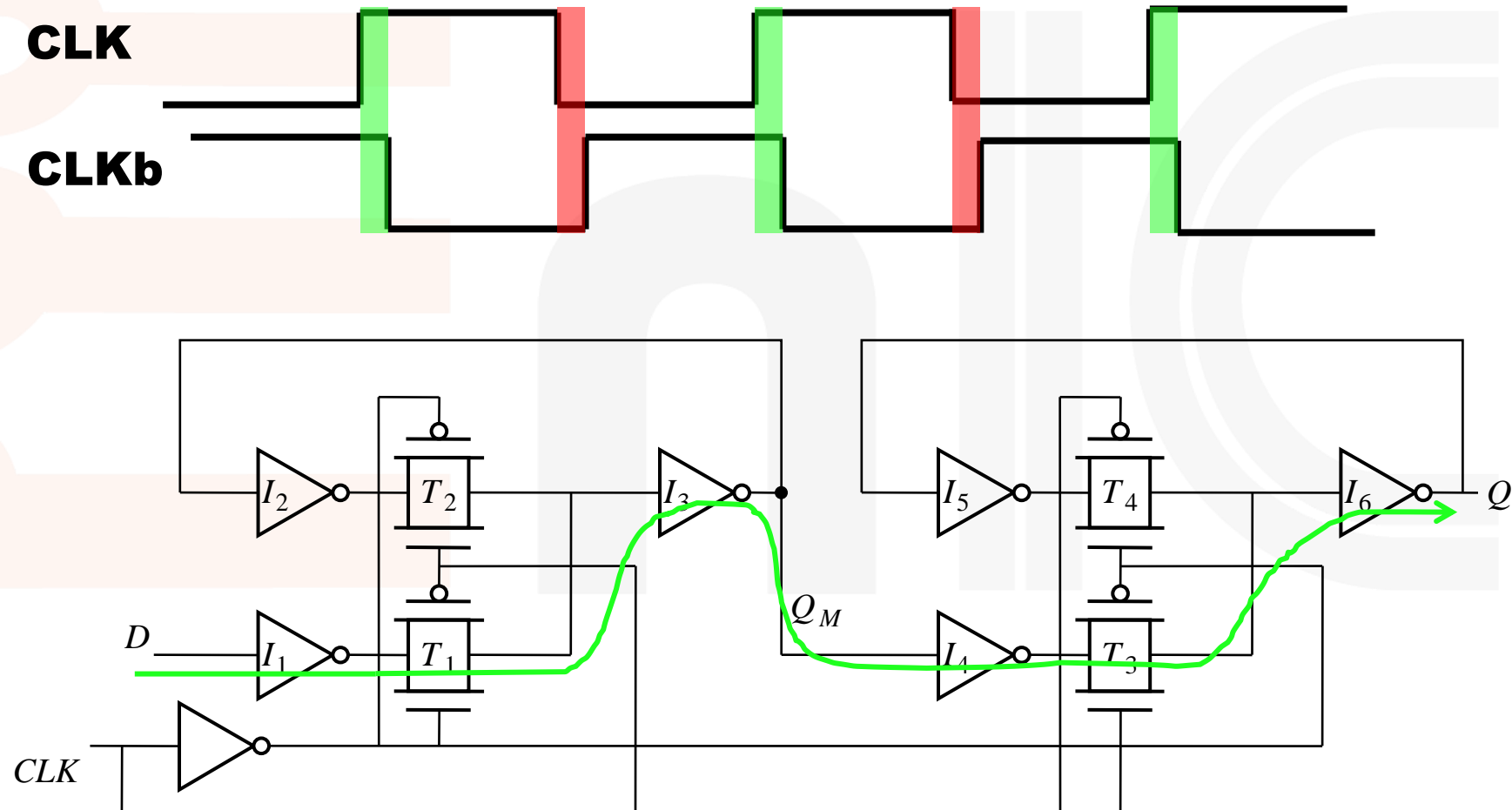


C²MOS – clocked CMOS


- Insensitive to clock overlap.

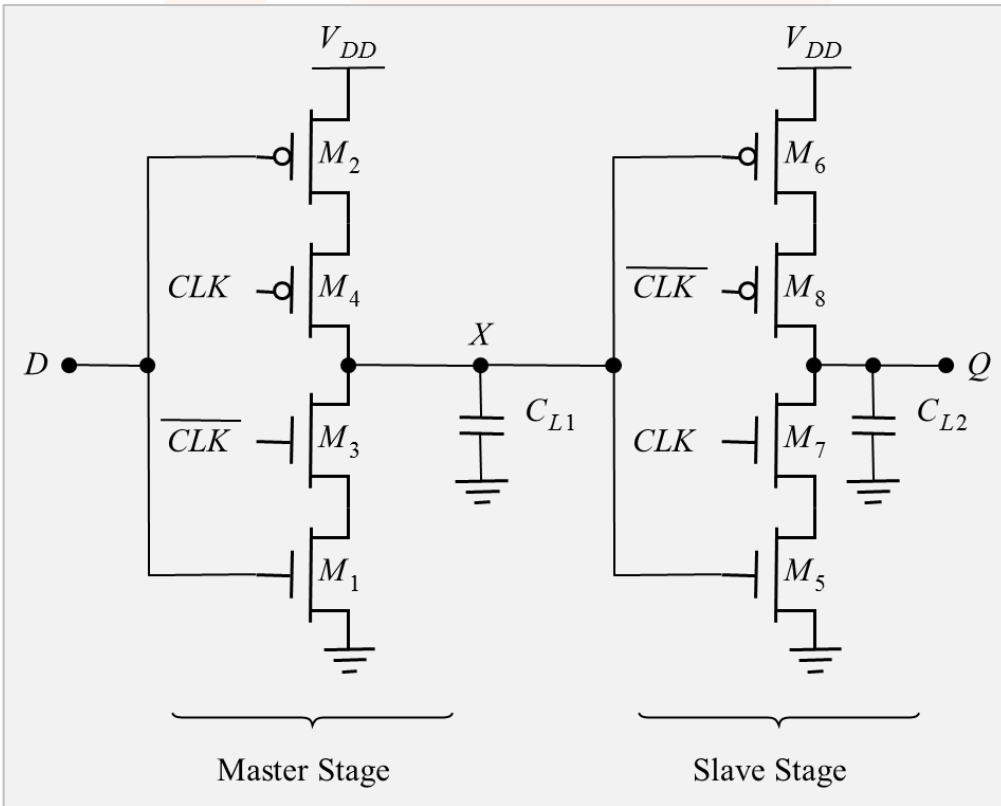

Low Phase Overlap

 


High Phase Overlap

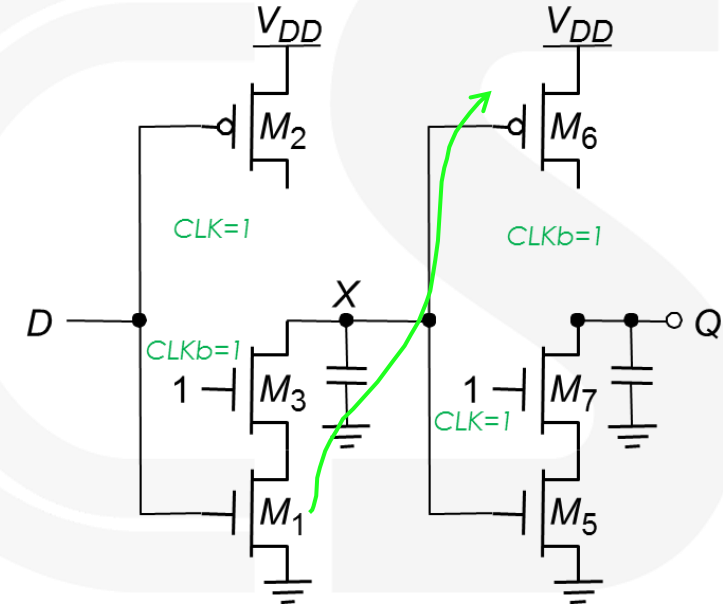


CLK


CLKb

 

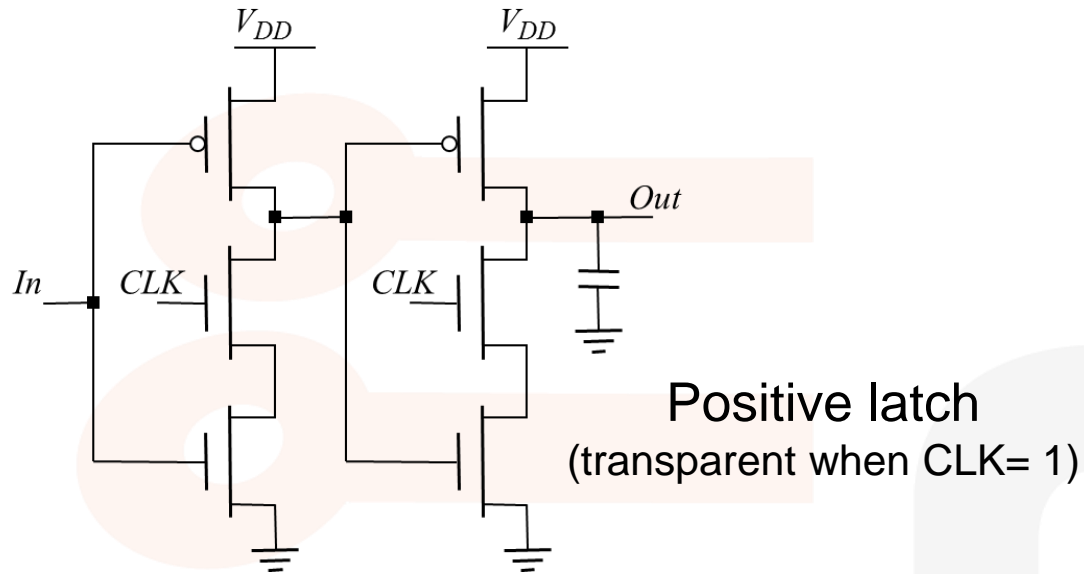TSPC – True Single-Phase Clocked Register




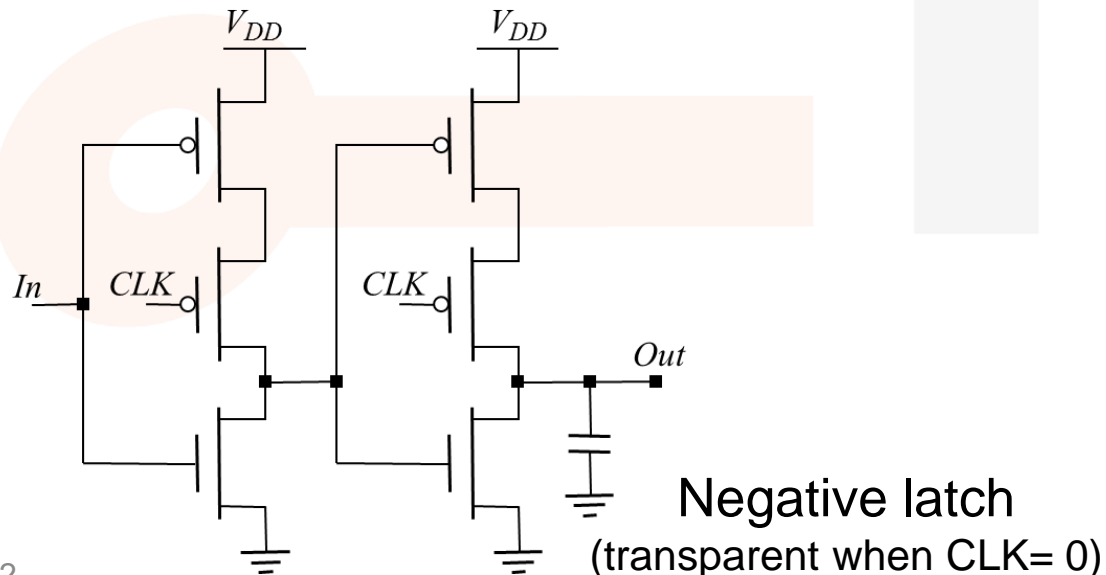Positive latch
(transparent when $CLK=1$)




Negative latch
(transparent when $CLK=0$)

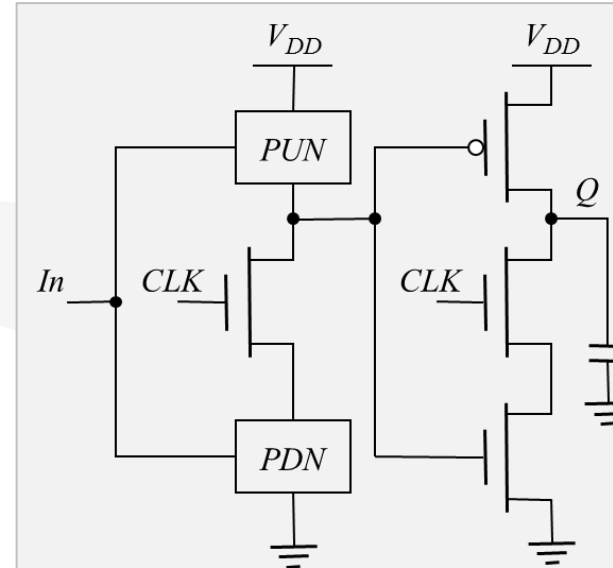
TSPC enables including logic inside the latch!



Example:
AND latch

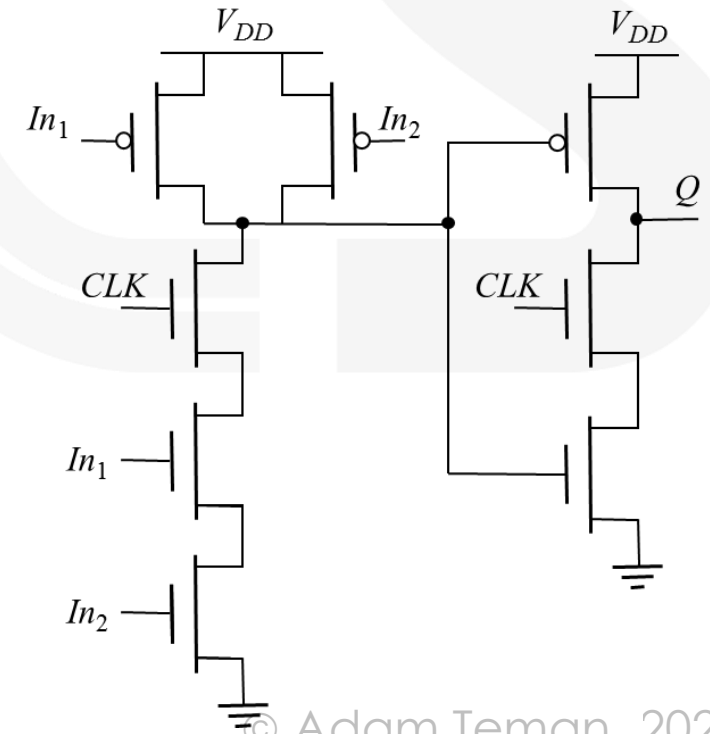


TSPC Flip Flop

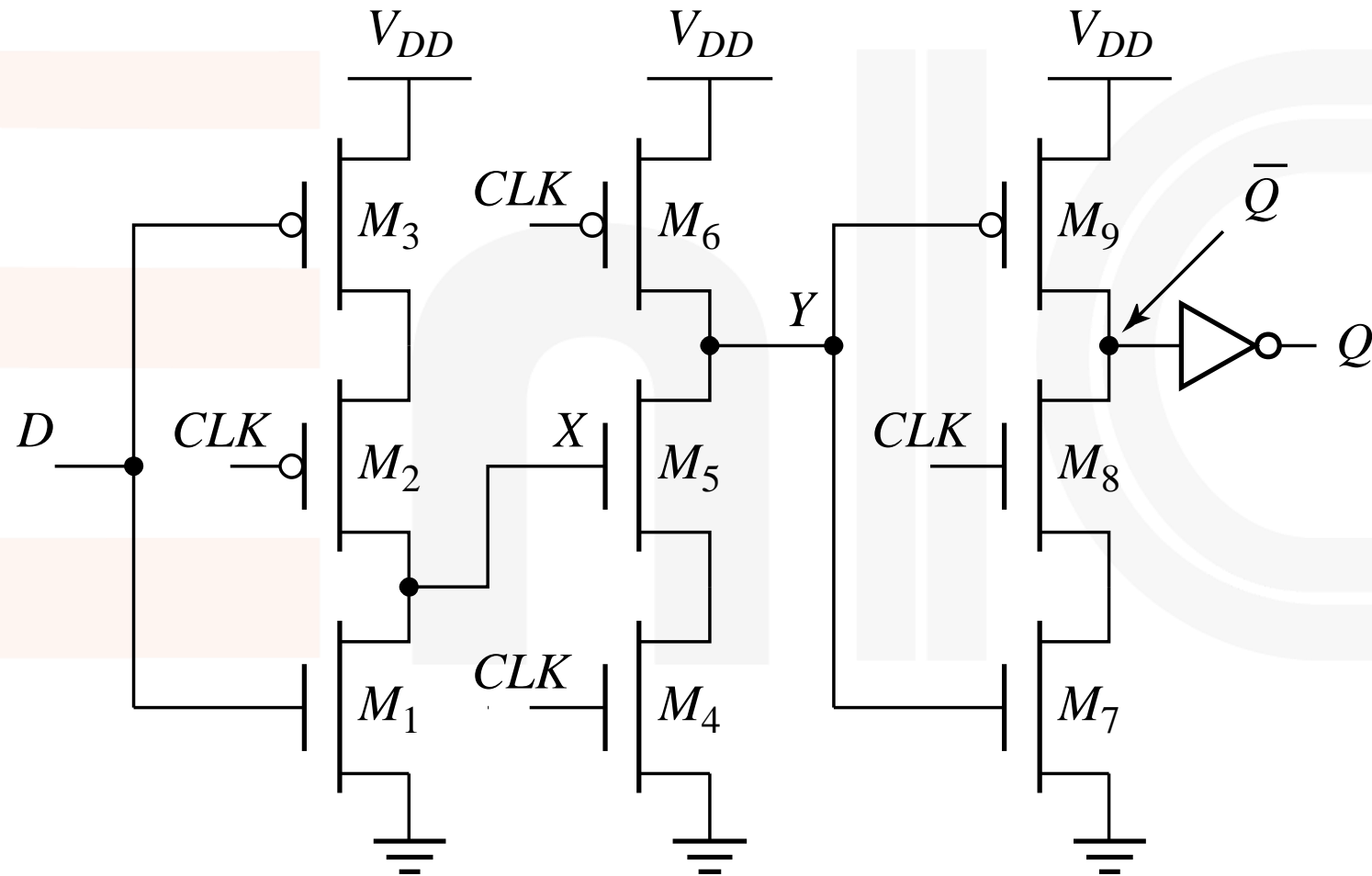


Pulse-Triggered Latches

 
- Instead of a full set of master-slave latches
- We can *emulate* an edge with a short clock pulse:



Pulse-Triggered Latch

 


 Design a clock pulse with a “clock chopper”



Basic Timing Constraints

Synchronous Timing

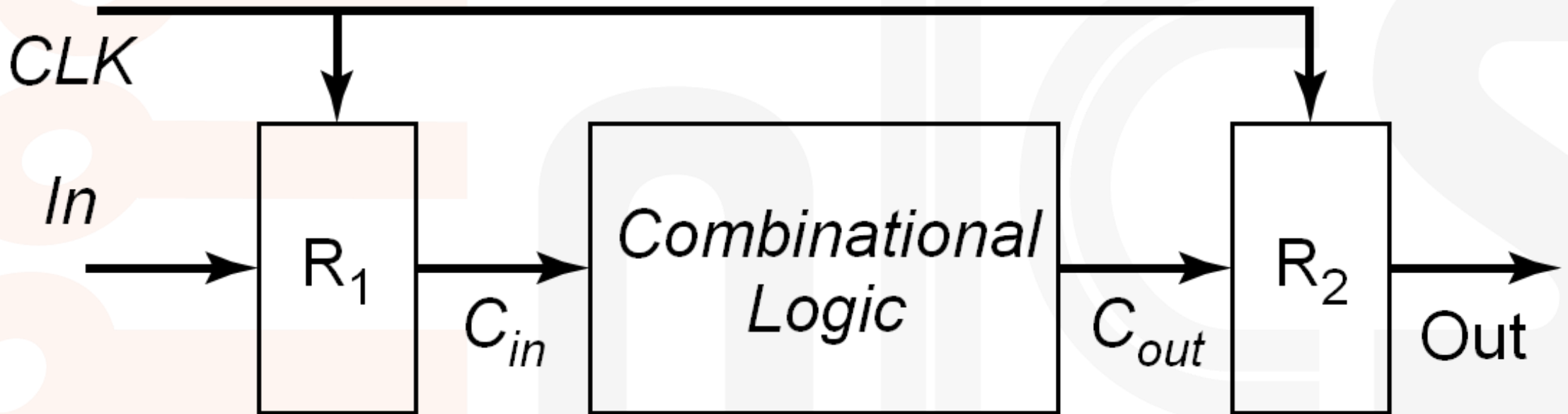


Timing Constraints


- There are two main problems that can arise in synchronous logic:
 - Max Delay: The data doesn't have enough time to pass from one register to the next before the next clock edge.
 - Min Delay: The data path is so short that it passes through several registers during the same clock cycle.
- Max delay violations are a result of a slow data path, including the registers' t_{setup} , therefore it is often called the “Setup” path.
- Min delay violations are a result of a short data path, causing the data to change before the t_{hold} has passed, therefore it is often called the “Hold” path.

Setup (Max) Constraint

- Let's see what makes up our clock cycle:
 - After the clock rises, it takes t_{cq} for the data to propagate to point A.
 - Then the data goes through the delay of the logic to get to point B.
 - The data has to arrive at point B, t_{setup} before the next clock.
- In general, our timing path is a race:
 - Between the **Data Arrival**, starting with the **launching clock** edge.
 - And the **Data Capture**, one clock period later.

 



Setup (Max) Constraint

 


$$T > t_{cq} + t_{logic} + t_{setup}$$

Hold (Min) Constraint

- Hold problems occur due to the logic changing before t_{hold} has passed.
- This is not a function of cycle time – it is relative to a single clock edge!
- Let's see how this can happen:
 - The clock rises and the data at **A** changes after t_{cq} .
 - The data at **B** changes t_{pd} (logic) later.
 - Since the data at **B** had to stay stable for t_{hold} after the clock (for the second register), the change at **B** has to be at least t_{hold} **after** the clock edge.

  

Hold (Min) Constraint

 

$$t_{cq} + t_{logic} > t_{hold}$$

Summary

- For **Setup** constraints, the clock period has to be longer than the data path delay:
 - This sets our maximum frequency.
 - If we have setup failures, we can always just **slow down the clock**.
- For **Hold** constraints, the data path delay has to be longer than the hold time:
 - This is **independent of clock period**.
 - If there is a hold failure, you can throw your chip away!

$$T > t_{cq} + t_{logic} + t_{setup}$$

$$t_{cq} + t_{logic} > t_{hold}$$

Clock Nonidealities

- **Clock skew**


- Spatial variation in temporally equivalent clock edges; deterministic + random, t_{skew}

- **Clock jitter**


- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term) $t_{Jit,S}$
- Long term $t_{Jit,L}$

- **Variation of the pulse width**


- Important for level sensitive clocking

 

Positive and Negative Skew

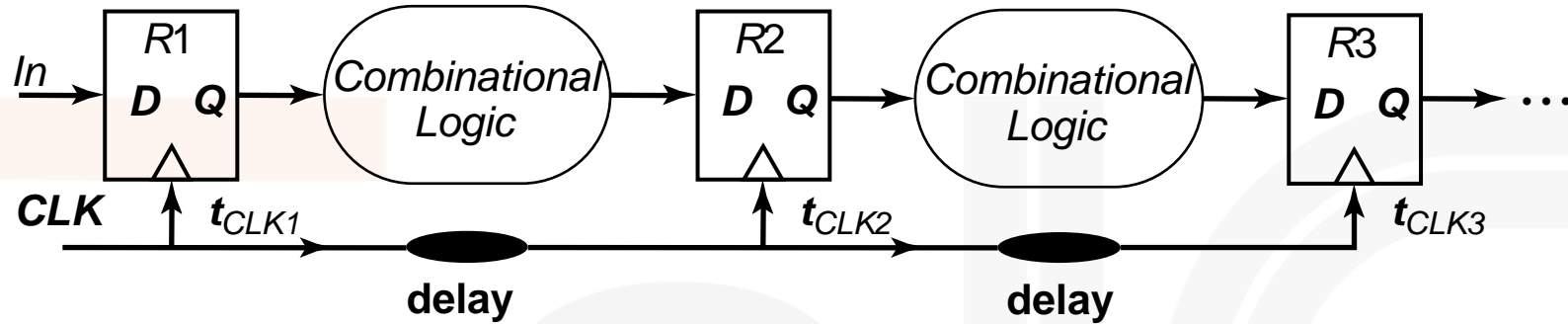

Positive skew

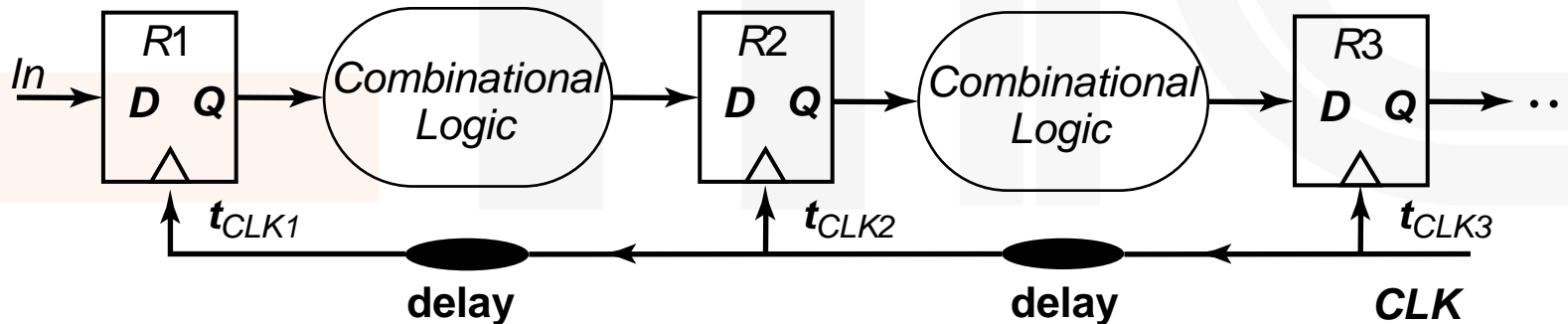

Negative skew

Setup (Max) Constraint

- The Launch path (still) consists of:

- $t_{cq} + t_{logic} + t_{setup}$
- But if **jitter** makes the launch clock **later**, we need to **add** it to the data path delay.

$$t_{launch} = t_{cq} + t_{logic} + t_{setup} + t_{jitter}$$

- The Capture path consists of:

- The clock period (T)
- **Positive skew** means the capture clock path is **longer**.
- If **jitter** makes the capture clock **earlier**, we need to **subtract** it.

$$t_{capture} = T + \delta_{skew} - t_{jitter}$$

- Our max constraint is:


- So we get:

$$t_{capture} \geq t_{launch}$$

$$T \geq t_{cq} + t_{logic} + t_{setup} + 2t_{jitter} - \delta_{skew}$$

Setup (Max) Constraint

 - Data has to arrive **before** next clock edge.



$$T + \delta_{\text{skew}} > t_{\text{cq}} + t_{\text{logic}} + t_{\text{setup}} + 2t_{\text{jitter}}$$

Hold (Min) Constraint

- The Launch path (still) consists of:

- $t_{cq} + t_{logic}$
- But if **jitter** makes the launch clock **later**, we need to **subtract** it from the data path delay.

$$t_{launch} = t_{cq} + t_{logic} - t_{jitter}$$

- The Capture path consists of:

- **Skew** that makes the clock edge arrive at the capture register **later** than at the launch register.
- Actually, since it is a single clock edge, jitter should effect the capture clock the same as the launch clock.
- But as a worst case, we will **add** it as spatial jitter.

$$t_{capture} = \delta_{skew} + t_{jitter} + t_{hold}$$

- Our min constraint is:


$$t_{launch} \geq t_{capture}$$

- So we get:

$$t_{cq} + t_{logic} \geq \delta_{skew} + t_{hold} + 2t_{jitter}$$

Hold (Min) Constraint

 - Data has to arrive **after** the same clock edge has arrived at capture reg.



$$t_{cq} + t_{logic} > t_{hold} + \delta_{skew} + 2t_{jitter}$$

Adding in Variation

- As previously discussed, variations in both fabrication and operating conditions occur and are taken into account through “corner” simulation.
- For global variation we have defined three primary simulation corners:
 - Typical Corner: our gates operate under **nominal** conditions and variation.
 - Slow Corner: our gates **slower** (i.e., high V_T , high temperature, low voltage).
 - Fast Corner: our gates **faster** (i.e., low V_T , low temperature, high voltage).
- To assume worst-case conditions:
 - Calculate **max-delay** with the **slowest** possible transitions → **Slow Corner**.
 - Calculate **min -delay** with the **fastest** possible transitions → **Fast Corner**.

The Computer Hall of Fame

- The machine that made IBM dominate the computer industry for 20 years

IBM System/360



Source: techradar.com

- Announced April 7th, 1964, the first “upgradable” and fully “compatible” computer.
- Thomas Watson “bet the business” on this machine with a \$5B investment that was to cannibalize all of IBM’s existing computers.
- Ranked as one of the all-time top 3 business accomplishments alongside Ford’s Model T and the Boeing 707.
- The machine that pioneered the 8-bit byte and the peripheral components made by third parties.



Source: computerhistory.org

Static Timing Analysis Example


STA Example

- We are given a synchronous network with:

$$t_{CQ} = 150\text{ps}, t_{\text{setup}} = 50\text{ps}, t_{\text{hold}} = 100\text{ps}, t_{\text{jitter}} = 0$$

- In addition:
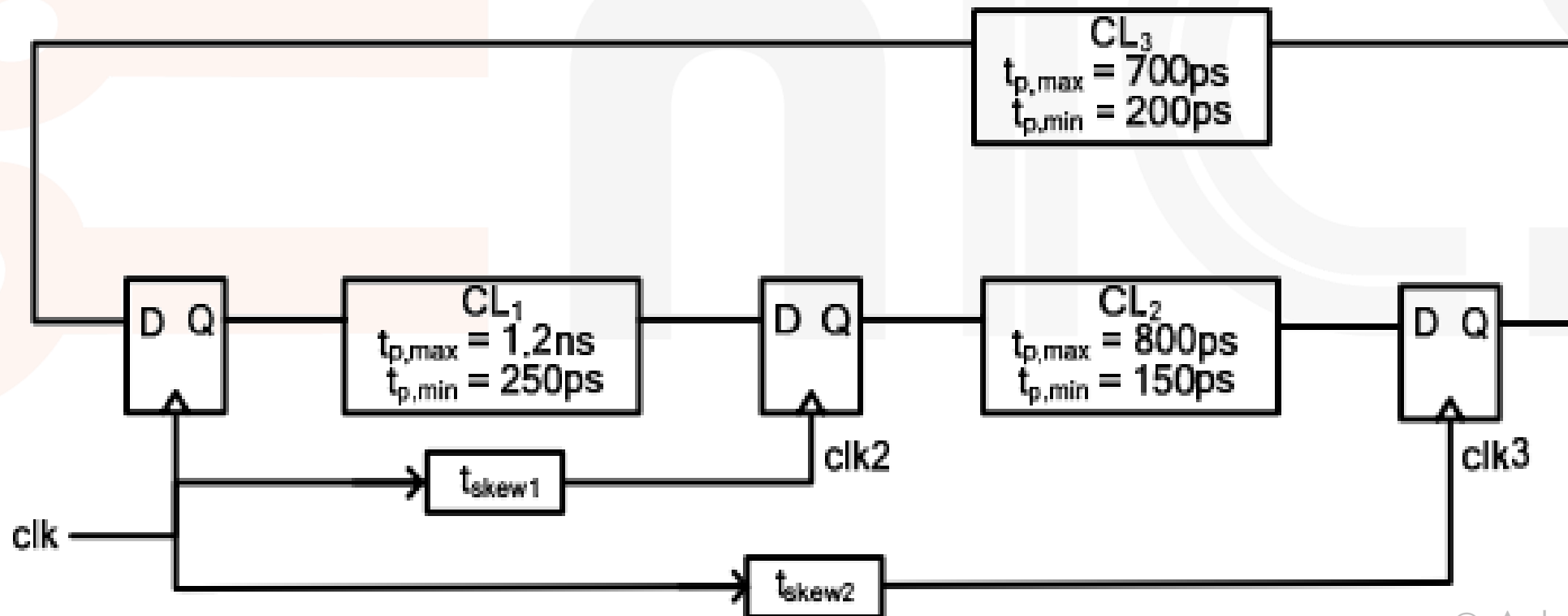
$$t_{\text{skew1}} = -100\text{ps}, t_{\text{skew2}} = 50\text{ps}$$



STA Example

- We'll find the setup constraints for each path:

Path 1: $T_1 + t_{\text{skew1}} > t_{\text{cq1}} + t_{\text{p,max}}(CL_1) + t_{\text{setup2}}$

$$T_1 > 150\text{p} + 1.2\text{n} + 50\text{p} + 100\text{p} = 1500\text{p} = 1.5\text{ns} \rightarrow 666\text{MHz}$$


Path 2: $T_2 + (t_{\text{skew2}} - t_{\text{skew1}}) > t_{\text{cq2}} + t_{\text{p,max}}(CL_2) + t_{\text{setup3}}$

$$T_2 > 150\text{p} + 800\text{p} + 50\text{p} - 150\text{p} = 850\text{p} \rightarrow 1.17\text{GHz}$$

Path 3: $T_3 + (0 - t_{\text{skew2}}) > t_{\text{cq3}} + t_{\text{p,max}}(CL_3) + t_{\text{setup1}}$

$$T_3 > 150\text{p} + 700\text{p} + 50\text{p} + 50\text{p} = 950\text{p} \rightarrow 1.05\text{GHz}$$

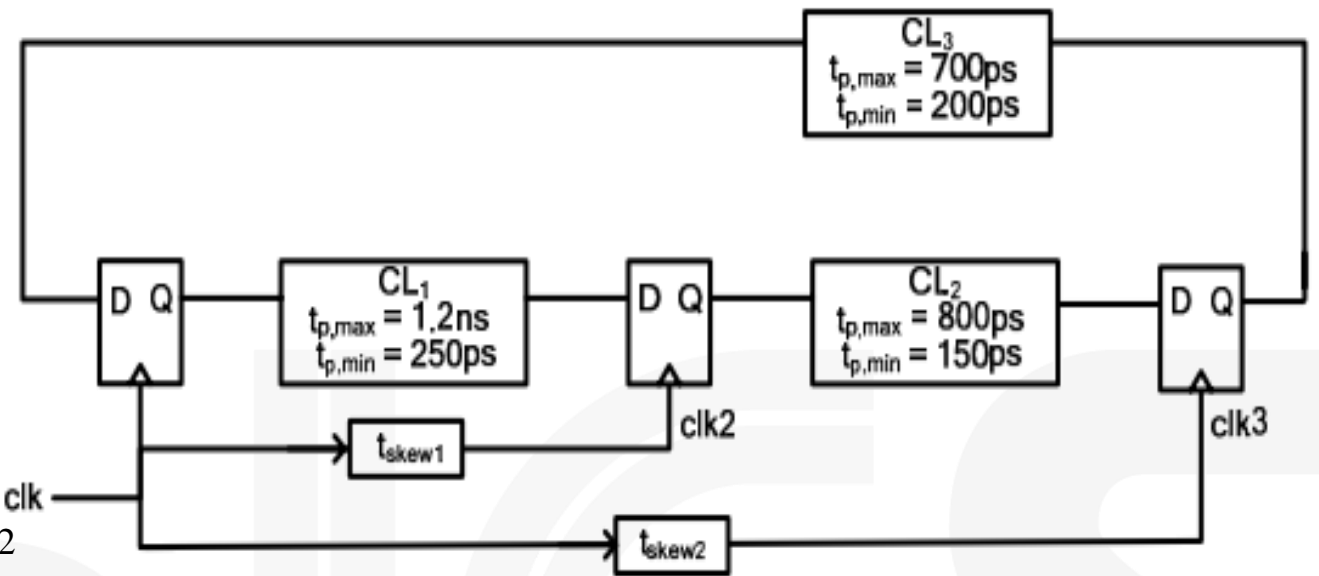- So the critical path is Path 1 and the maximum frequency is 666MHz.



STA Example

- Now, we'll find the hold constraints for t_{skew1} and t_{skew2} :

Path 1: $t_{skew1} + t_{hold2} < t_{cq1} + t_{p,min}(CL_1)$


$$t_{skew1} < 150p + 250p - 100p = 300p$$

Path 2: $(t_{skew2} - t_{skew1}) + t_{hold3} < t_{cq2} + t_{p,min}(CL_2)$

$$(t_{skew2} - t_{skew1}) < 150p + 150p - 100p = 200p$$

Path 3: $(0 - t_{skew2}) + t_{hold1} < t_{cq3} + t_{p,min}(CL_3)$
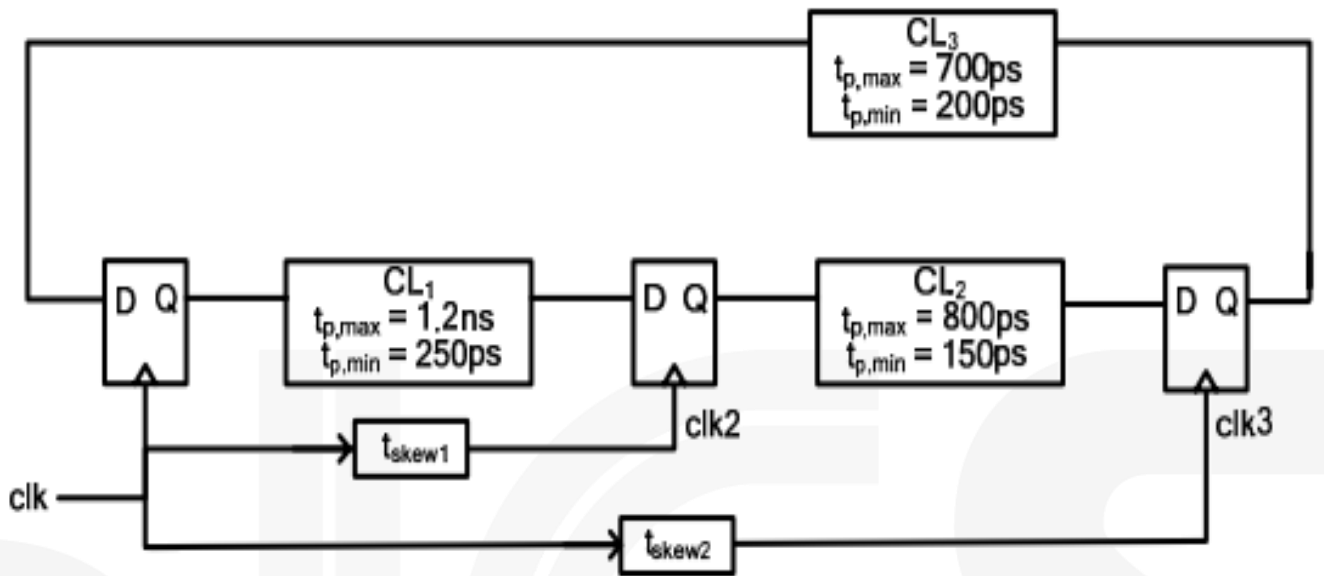
$$-t_{skew2} < 150p + 200p - 100p = 250p \rightarrow t_{skew2} > -250p$$



STA Example

- If we could set t_{skew1} and t_{skew2} , could we use them to maximize our frequency?
- If we could equally divide the delay of each path:


$$\begin{aligned}
 t_{\text{total}} &= 3 \cdot t_{\text{cq}} + t_{\text{p,max}} (CL_1 + CL_2 + CL_3) + 3 \cdot t_{\text{setup}} = \\
 &= 450\text{p} + 2.7\text{n} + 150\text{p} = 3.3\text{ns}
 \end{aligned}$$

- So to get the max frequency, set all delays to 1.1ns:

$$1.1\text{ns} + t_{\text{skew1}} = 150\text{p} + 1.2\text{n} + 50\text{p} \rightarrow t_{\text{skew1}} = 300\text{ps}$$

$$1.1\text{ns} + (t_{\text{skew2}} - t_{\text{skew1}}) = 150\text{p} + 800\text{p} + 50\text{p} \rightarrow t_{\text{skew2}} = 200\text{ps}$$
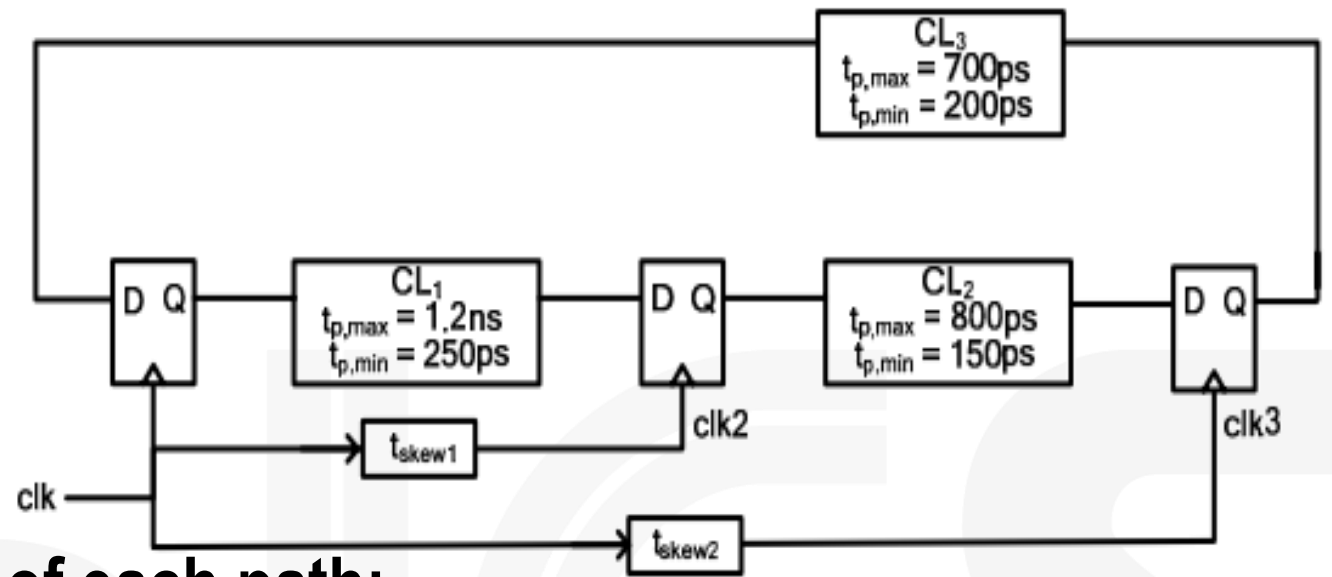
$$1.1\text{ns} + (0 - t_{\text{skew2}}) = 150\text{p} + 700\text{p} + 50\text{p} \rightarrow t_{\text{skew2}} = 200\text{ps}$$



Further Reading

- J. Rabaey, “*Digital Integrated Circuits*” 2003, Chapter 7
- Weste, Harris “CMOS VLSI Design” Chapter 7
- E. Alon, Berkeley *EE-141*, Lectures 23,24 (Fall 2010) http://bwrc.eecs.berkeley.edu/classes/icdesign/ee141_f10/
- Berkeley *CS-150*, Lecture 4 <http://inst.eecs.berkeley.edu/~cs150/>
- Oklobdzija, Stojanovic, Markovic, Nedovic, “*Digital System Clocking*”