

Digital Integrated Circuits

(83-313)

Lecture 8: SRAM

Prof. Adam Teman
2 May 2021

The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



Lecture Content

First Look at Memory



The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



The 6T SRAM Bitcell



The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



6T SRAM Operation



The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



6T SRAM Layout



The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



SRAM Stability
"Static Noise Margin"



The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University



SNM Calculation




The Alexander Kofkin
Faculty of Engineering
Bar-Ilan University




First Look at Memory


Why Memory?

 

Intel Pentium-M (2001) – 2MB L3 Cache

 


 Intel 10th Gen "Comet Lake" (2020) – 20MB L3 Cache



Cerebras Wafer Scale Engine 2 (2021) –
16GB On-Chip Memory


Memory Hierarchy of a Personal Computer

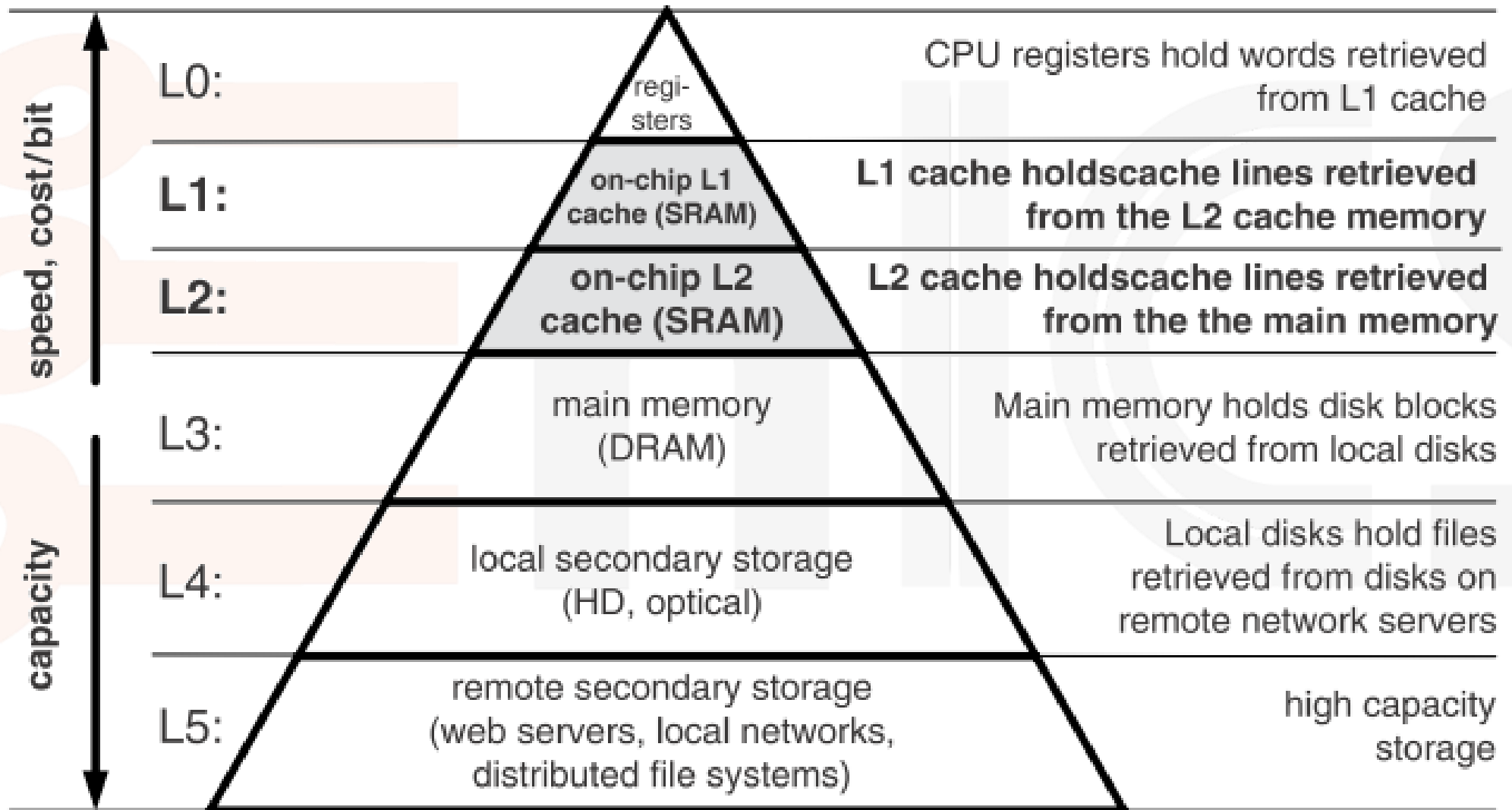

Source: Pavlov, Sachdev, 2008

© Adam Teman, 2021

Semiconductor Memory Classification

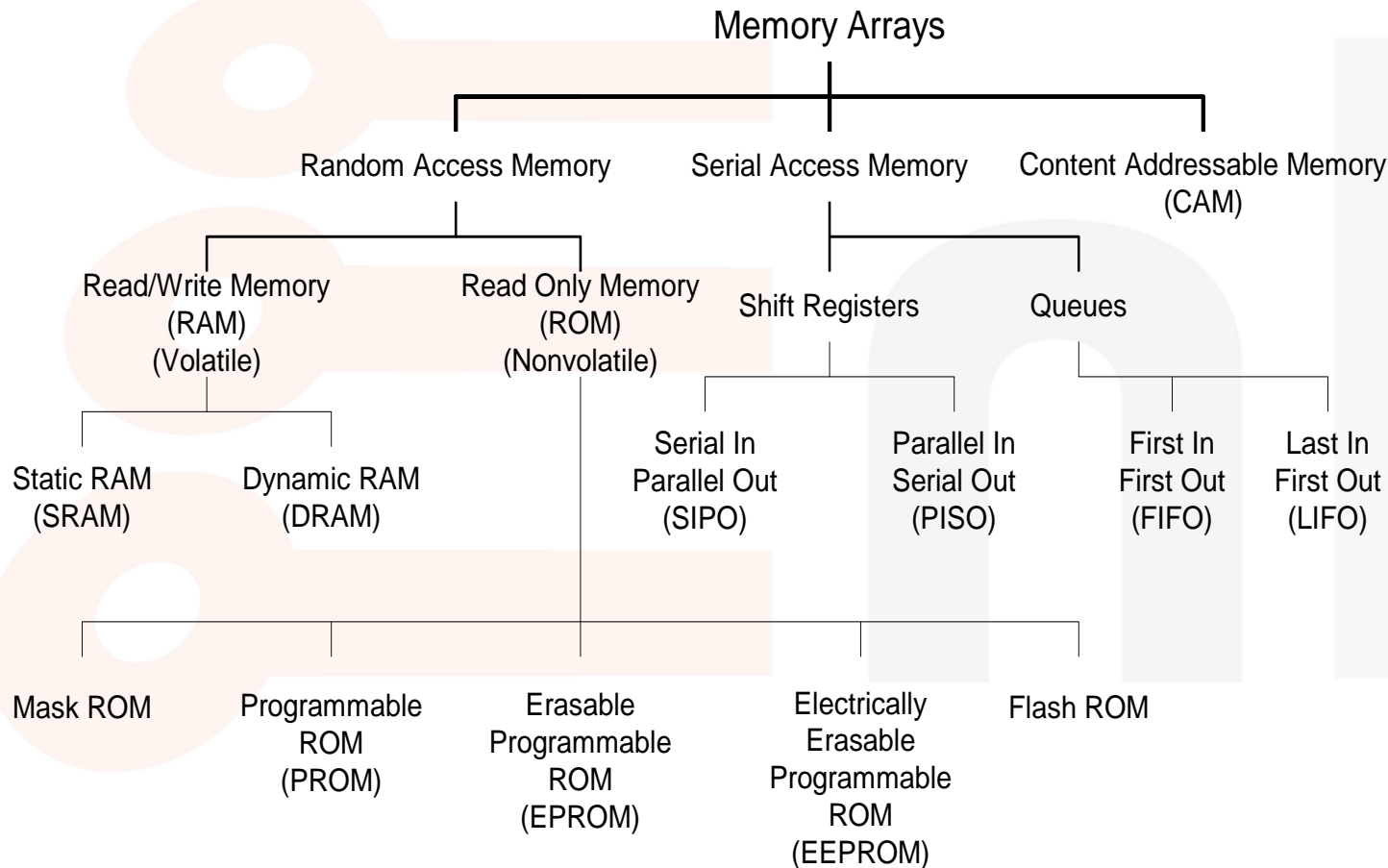

- **Size:**

- Bits, Bytes, Words

- **Timing Parameters:**

- Read access, write access, cycle time

- **Function:**

- Read Only (ROM) – non-volatile
- Read-Write (RWM) – volatile
- NVRWM – Non-volatile Read Write

- **Access Pattern:**

- Random Access, FIFO, LIFO, Shift Register, CAM

- **I/O Architecture:**


- Single Port, Multi-port

- **Application:**

- Embedded, External, Secondary



Random Access Chip Architecture

- **Conceptual: linear array**
 - Each box holds some data
 - But this leads to a long and skinny shape
- **Let's say we want to make a 1MB memory:**
 - $1\text{MB} = 2^{20}$ words X 8 bits = 2^{23} bits, each word in a separate row
 - A decoder would reduce the number of access pins from 2^{20} access pins to 20 address lines.
 - We'd fit the pitch of the decoder to the word cells, so we'd have *Word Lines* with no area overhead.
 - The output lines (= *bit lines*) would be extremely long, as would the delay of the huge decoder.
 - The array's height is about 128,000 times larger than its width ($2^{20}/2^3$).

 


Square Ratio

- Instead, let's make the array square:
 - $1\text{MB} = 2^{23} \text{ bits} = 2^{12} \text{ rows} \times 2^{11} \text{ columns}$.
 - There are 4000 rows, so we need a 12-bit row address decoder (to select a single row)
 - There are 2000 columns, representing 256 8-bit words.
 - We need to select only one of the 256 words through a column address decoder (or multiplexer).
 - We call the row lines "**Word Lines**" and the column lines "**Bit Lines**".

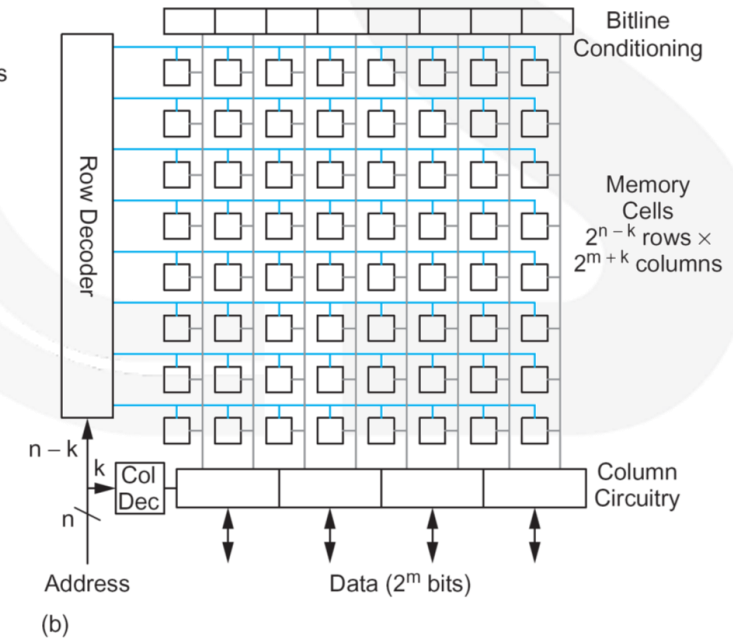 


Special Considerations

- The “**core**” of the memory array is huge.
It can sometimes take up most of the chip area.
 - For this reason, we will try to make the “**bitcell**” as small as possible.
 - A standard Flip Flop uses at least 10 transistors per bit (usually more than 20). This is very area consuming.
- We will trade-off area for other circuit properties:
 - Noise Margins
 - Logic Swing
 - Speed
 - Design Rules
- This requires special peripheral circuitry.

 

Memory Architecture

 

Memory Size: W Words of C bits

$= W \times C$ bits

Address bus: A bits

$\rightarrow W = 2^A$

Number of Words in a Row: 2^M

Multiplexing Factor: M

Number of Rows: 2^{A-M}


Number of Columns: $C \times 2^M$

Row Decoder: $A-M \rightarrow 2^{A-M}$

Column Decoder: $M \rightarrow 2^M$

The 6T SRAM Bitcell

Basic Static Memory Element

 


Positive Feedback: Bi-Stability



Writing into a Cross-Coupled Pair

 - The write operation is ratioed
 - The access transistor must overcome the feedback.



How should we write a '1'

Option 1: nMOS Access Transistor

Passes a "weak '1'", bad at pulling up against the feedback

Option 3: Transmission Gate

Writes well, but how do we read?

Option 2: pMOS Access Transistor



Passes a "weak '0'", bad at pulling down against the feedback

Solution: Differential nMOS Write

Reading from a 6T SRAM Cell



6-transistor CMOS SRAM Cell

  


The Computer Hall of Fame

- The machine that introduced the GUI, the mouse, and Steve Jobs to the mainstream.

The Macintosh

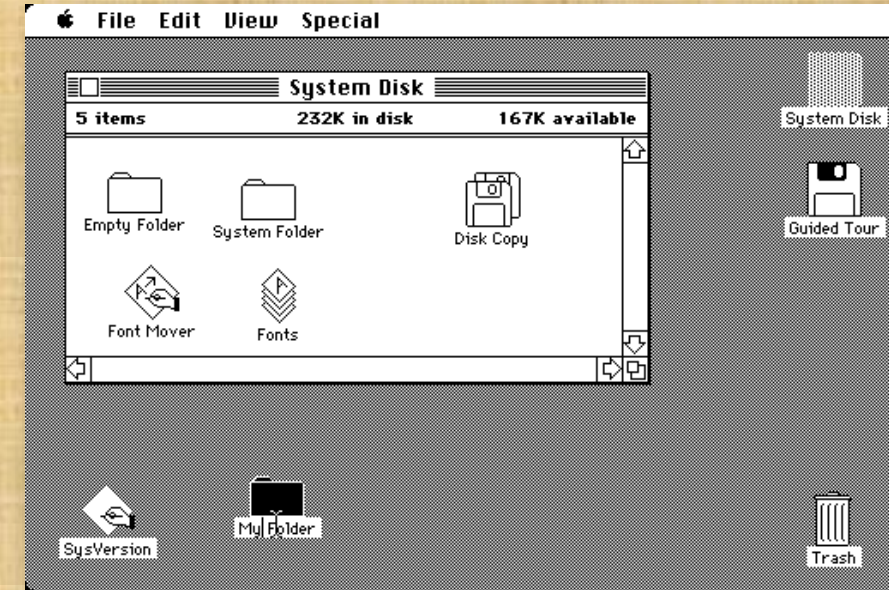- The personal computer that “was designed so easy to use that people could actually use it”.
- Developed based on a 3-day tour of Apple at Xerox PARC, where they saw the Xerox Alto.
- Introduced in 1984, sold for \$2500 with an 8MHz Motorola 6800 processor, 128kB RAM.
- Included MacPaint and MacWrite
- Despite initial success, sales declined and Steve Jobs was fired from Apple in 1985.



Source: macworld.co.uk




Source: macworld.co.uk




6T SRAM Operation



SRAM Operation: HOLD

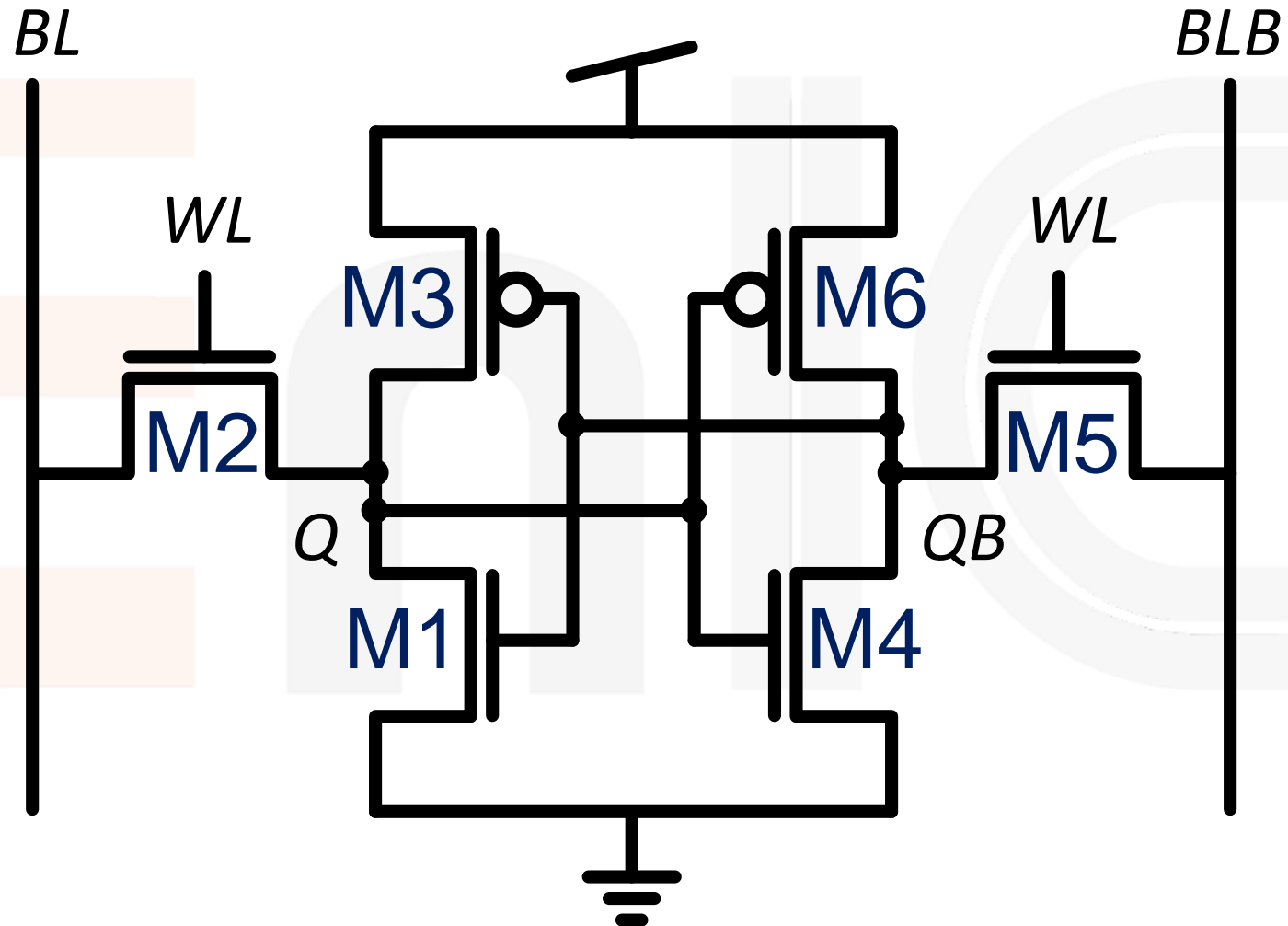

SRAM Operation: READ

 

SRAM Operation - Read

 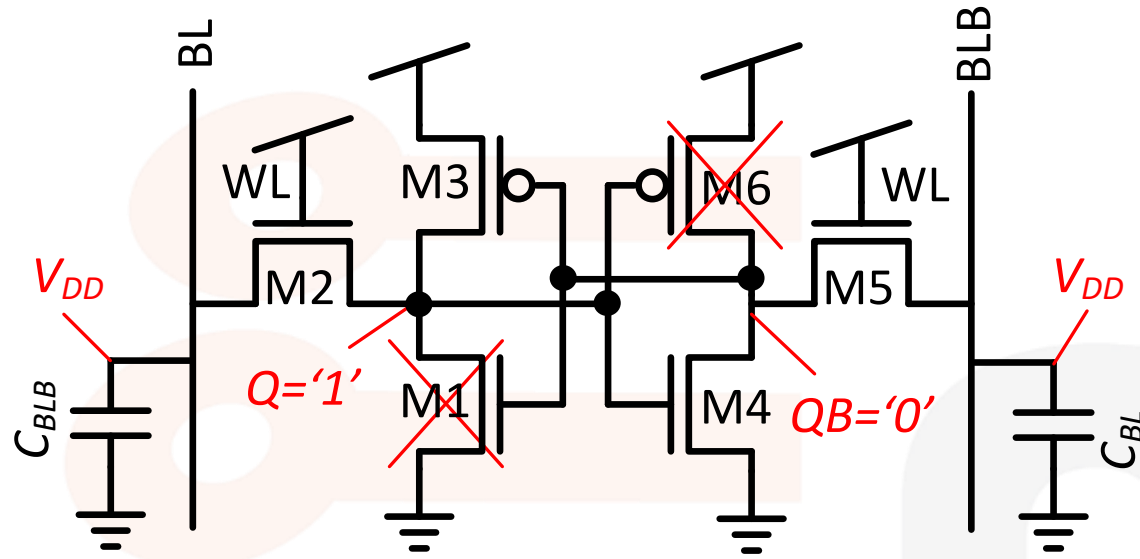


Cell Ratio:

$$CR \equiv \frac{W_4/L_4}{W_5/L_5}$$


$$k_{M5} \left[(V_{DD} - \Delta V - V_{T,n}) V_{DSat,n} - \frac{V_{DSat,n}^2}{2} \right] = k_{M4} \left[(V_{DD} - V_{T,n}) \Delta V - \frac{\Delta V^2}{2} \right]$$

$$\Delta V = \frac{V_{DSat,n} + CR(V_{DD} - V_{T,n}) - \sqrt{V_{DSat,n}^2 (1 + CR) + CR^2 (V_{DD} - V_{T,n})^2}}{CR}$$

Cell Ratio (Read Constraint)

 


$$CR \equiv \frac{W_4/L_4}{W_5/L_5}$$

 

So we need the pull down transistor to be much stronger than the access transistor...


SRAM Operation: WRITE

 

SRAM Operation - Write

Pull-Up Ratio


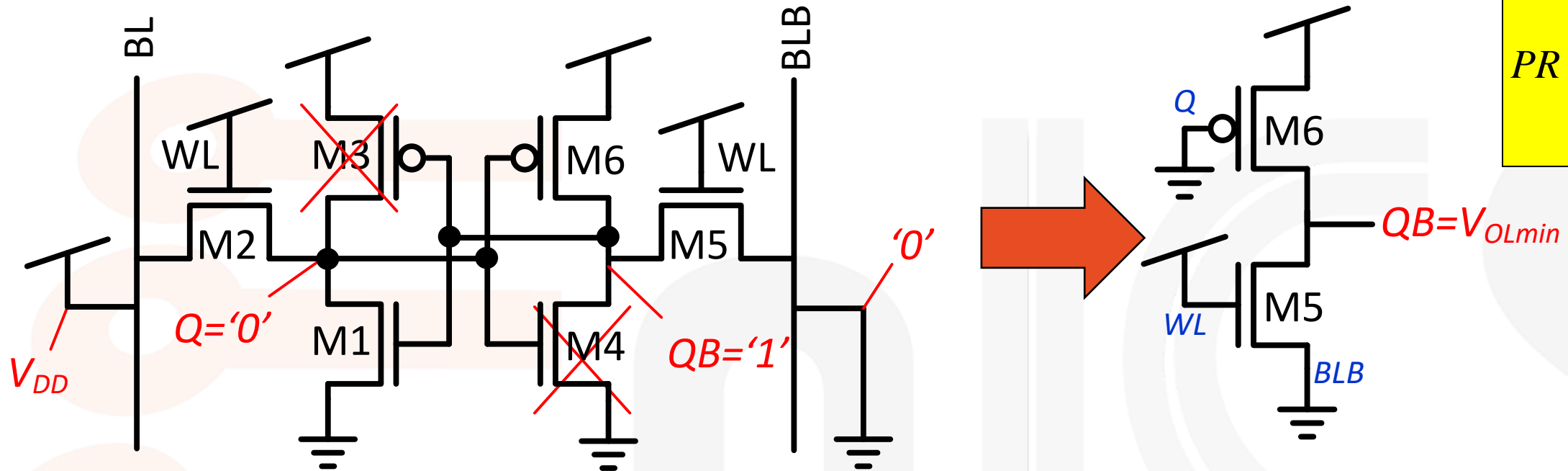
$$PR \equiv \frac{W_6 / L_6}{W_5 / L_5}$$



$$k_{M6} \left[\left(V_{DD} - |V_{T,p}| \right) V_{DSat,p} - \frac{V_{DSat,p}^2}{2} \right] = k_{M5} \left[\left(V_{DD} - V_{T,n} \right) V_{QB} - \frac{\Delta V_{QB}^2}{2} \right]$$

$$V_{QB} = V_{DD} - V_{T,n} - \sqrt{\left(V_{DD} - V_{T,n}\right)^2 - 2 \frac{\mu_p}{\mu_n} PR \left[\left(V_{DD} - |V_{T,p}|\right) V_{DSat,p} - \frac{V_{DSat,p}^2}{2} \right]}$$

Pull Up Ratio – Write Constraint

  


So we need the access transistor to be much stronger than the pull up transistor...

$$PR \equiv \frac{W_6/L_6}{W_5/L_5}$$

Summary – SRAM Sizing Constraints

Read Constraint

 

$$CR \equiv \frac{W_1/L_1}{W_2/L_2} = \frac{W_4/L_4}{W_5/L_5} = \frac{PDN}{access}$$




$$K_{PDN} > K_{access}$$




$$K_{PDN} > K_{access} > K_{PUN}$$

Write Constraint

 
 
$$PR \equiv \frac{W_3/L_3}{W_2/L_2} = \frac{W_6/L_6}{W_5/L_5} = \frac{PUN}{access}$$




$$K_{access} > K_{PUN}$$




4T Memory Cell

 - Achieve density by removing the PMOS pull-up.
- However, this results in static power dissipation.




Multi-Port SRAM

Dual Port SRAM

 




Two Port SRAM

 

6T SRAM Layout



SRAM Layout - Traditional

   - Share Horizontal Routing (**WL**).
- Share Vertical Routing (**BL**, **BLB**).
- Share Power and Ground.





SRAM Layout – Thin Cell

  - Avoid Bends in Polysilicon and Diffusion
- Orient all transistors in one direction.
- Minimize Bitline Capacitance.




65nm SRAM


- Industrial example from ST/Phillips

  


Commercial SRAMs

 

 0.092 μm^2 SRAM cell
for high density applications




 0.108 μm^2 SRAM cell
for low voltage applications




Intel Design Forum 2009


1 μm

 


130 nm [Tyagi00]

 


90 nm [Thompson02]

 

65 nm [Bai04]

 



45 nm [Mistry07]

 


32 nm [Natarajan08]

And very recent SRAMs

TSMC 7nm
SRAM

  


TSMC 5nm SRAM Test Chip

 

Technology	5nm HK-MG FinFET
HD Bit Cell Size	0.021 μm^2
SRAM Macro Configuration	144Kb (1024X144 MUX4)
SRAM Capacity	135Mb
Chip Size	10.00mm X 7.98mm = 79.8 mm ²

Source: ISSCC 2020

Samsung 3nm
GAA SRAM Test Chip

 


MBCFET SRAM
Vertical TEM Image

Source: ISSCC 2021


SRAM Stability

“Static Noise Margin”


Static Noise Margin - Hold

 

Static Noise Margin - Hold


 


 1. Plot both VTCs on the same graph
2. Find the maximum square that fits in the VTC.
3. The SNM is defined as the side of the maximum square.






Static Noise Margin - Read

  - **What happens during Read?**
 - We can't ignore the access transistors anymore...






Static Noise Margin - Read

 
 
 


Static Noise Margin - Write

  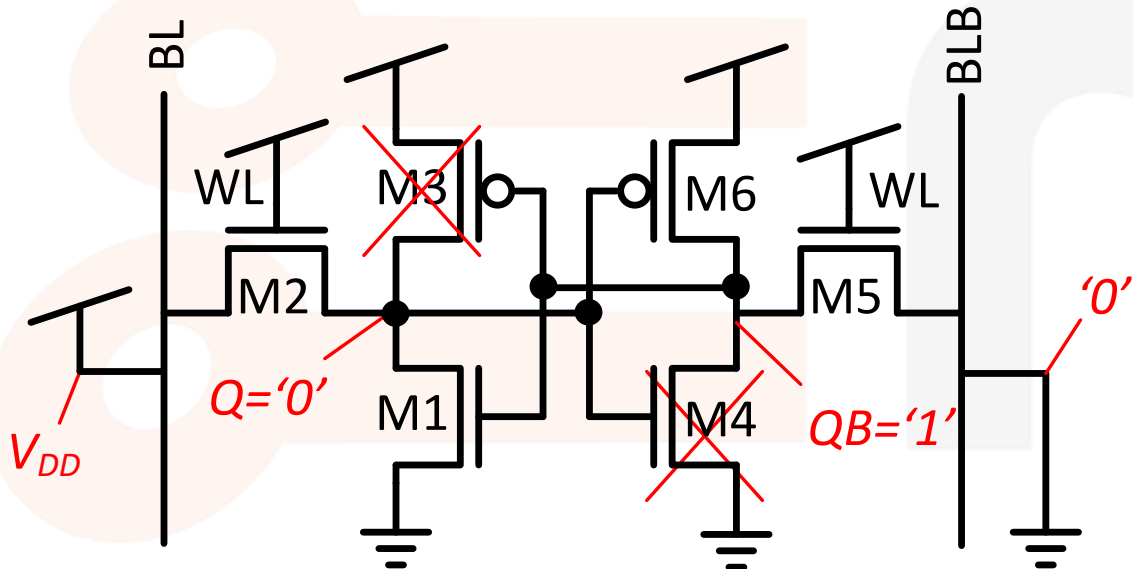- What happens during Write?
 - The two sides are now different.






Static Noise Margin - Write

   

Alternative Write SNM Definition

   - Write SNM depends on the cell's separatrix, therefore alternative definitions have been proposed.
- For example, add a DC Voltage (V_{BL}) to the 0 bitline and see how high it can be and still flip the cell.



Dynamic Stability



SNM Calculation

Simulating SNM

- **Problem:**

- How can we calculate *SNM* with *SPICE*?


- **Some options:**

- Insert *DC sources* at *Q* and *QB*
 - But where exactly do we connect them?
 - Draw *Butterfly Curves*
 - But how do we find the largest squares?

- **To run Monte Carlo Simulations we should have an easy way of calculation.**


Simulating SNM

 - **First let's define the graphical solution:**
 - The diagonals of all the squares are on lines parallel to $Q=QB$.
 - We need to find the distance between the points where these intersect the butterfly plot.
 - The largest of these distances is the diagonal of the maximum square in each lobe.
 - Multiply this by $\cos 45^\circ$ and we get the SNM.
- **Easy, right?**




Changing Coordinates

- What if we were to turn the graph?

 

Changing Coordinates

 - If we were to use new axes, we could just subtract the graphs.
 - This gives us the distances between the intersections with the $Q=QB$ parallels.
 - Now all we have to do is find the maximum of the subtraction.
 - (Don't forget to multiply by $\cos 45^\circ$)



Changing Coordinates

- The required transformation is:

$$x = \frac{1}{\sqrt{2}}u + \frac{1}{\sqrt{2}}v$$

$$y = -\frac{1}{\sqrt{2}}u + \frac{1}{\sqrt{2}}v$$

- Now let's define some function as F_1


- Substituting $y=F_1(x)$ gives:

$$\begin{aligned} v &= u + \sqrt{2}y = \\ &= u + \sqrt{2}F_1\left(\frac{1}{\sqrt{2}}u + \frac{1}{\sqrt{2}}v\right) \end{aligned}$$

Changing Coordinates

- What we did is turn some function (F_1) *45 degrees* counter clockwise.
- This can easily be implemented with the following circuit:

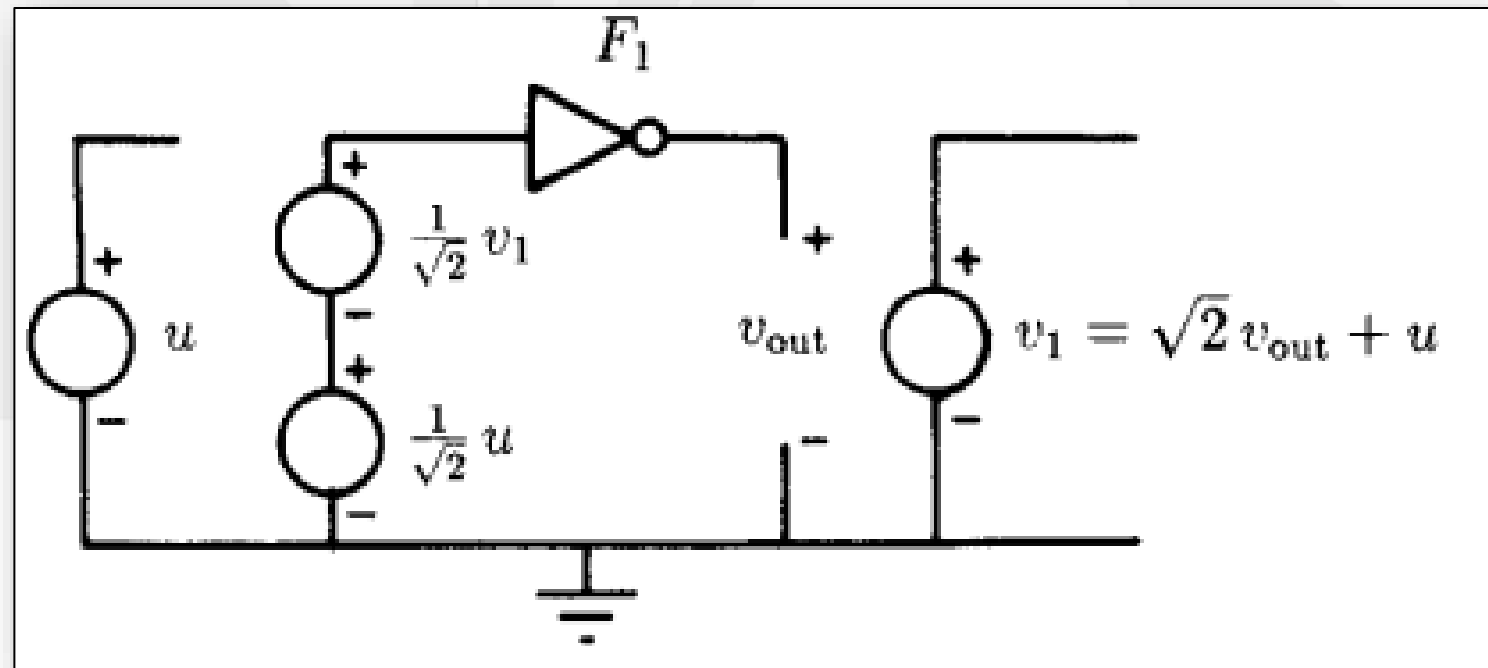- What is F_1 ?
 - It could be the *VTC* of $V_{in}=Q$, $V_{out}=QB\dots$




Changing Coordinates

- But what about the “mirrored” VTC?


- This needs to first be mirrored with respect to the v axis and then transformed to the (u, v) system.
- If we call the second VTC F_2 with $x=F_2(y)$ then the operation we need is:
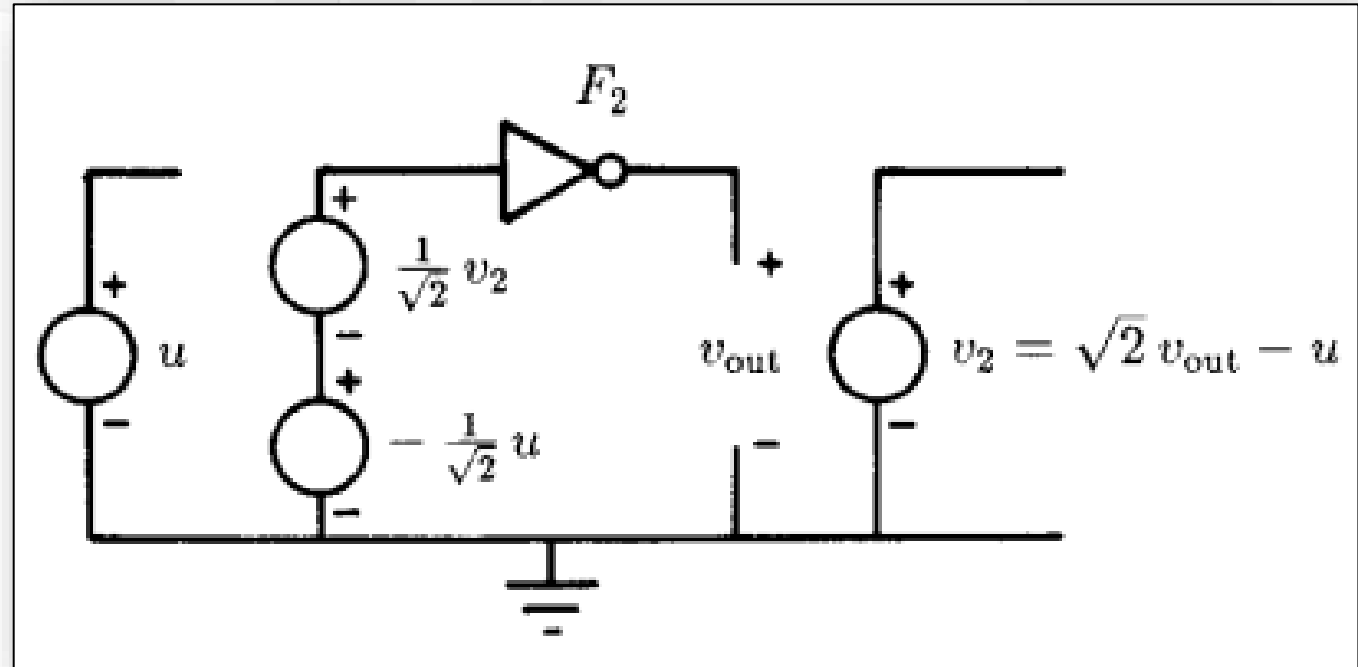
$$\begin{aligned} v &= -u + \sqrt{2}x \\ &= -u + \sqrt{2}F_2\left(\frac{v}{\sqrt{2}} - \frac{u}{\sqrt{2}}\right) \end{aligned}$$




Final SNM Calculation

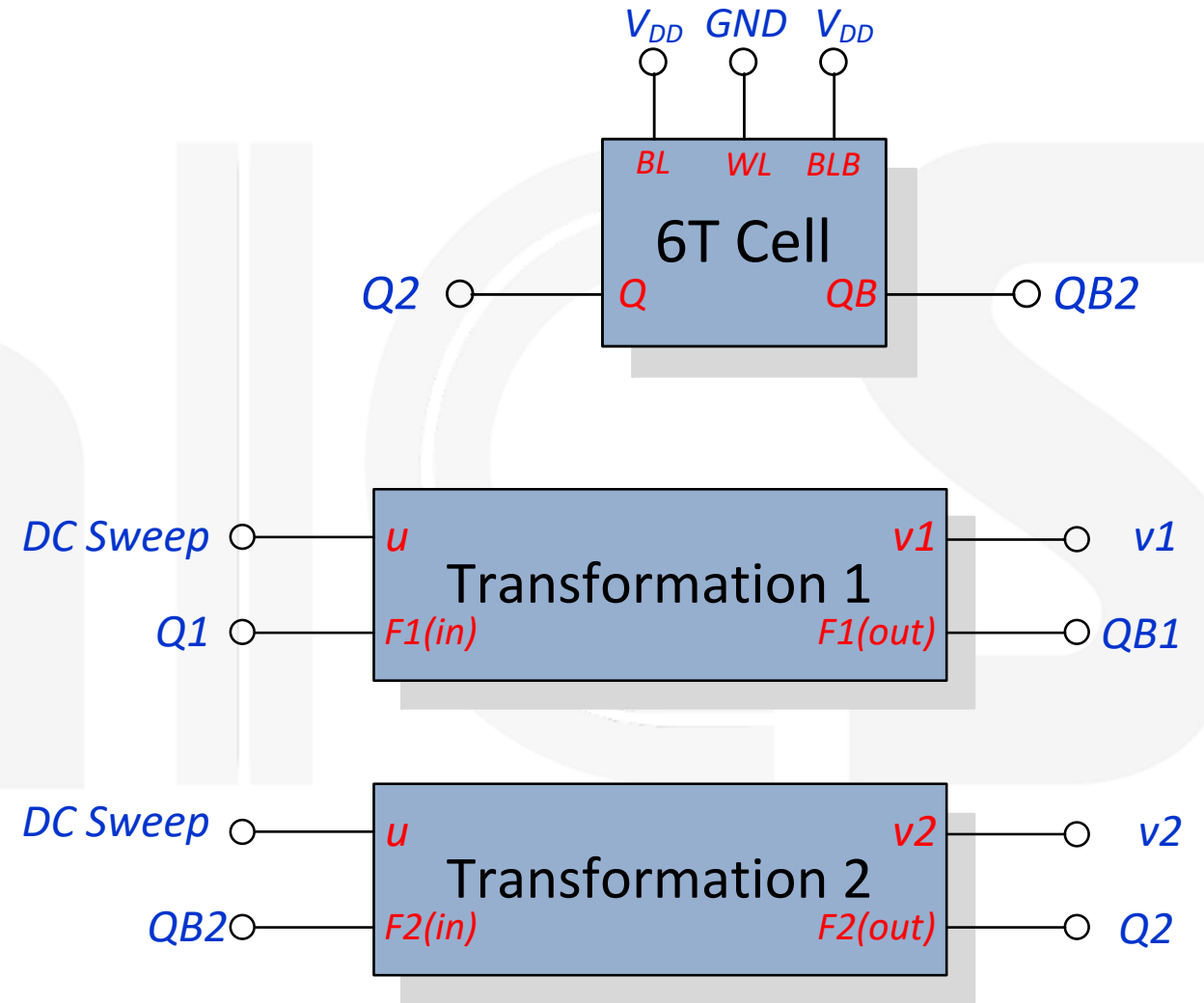- Now we need to:
 - Make a schematic of our SRAM cell with two pins: Q and QB .
 - Create a coordinate changing circuit for each of the transformations.




Final SNM Calculation

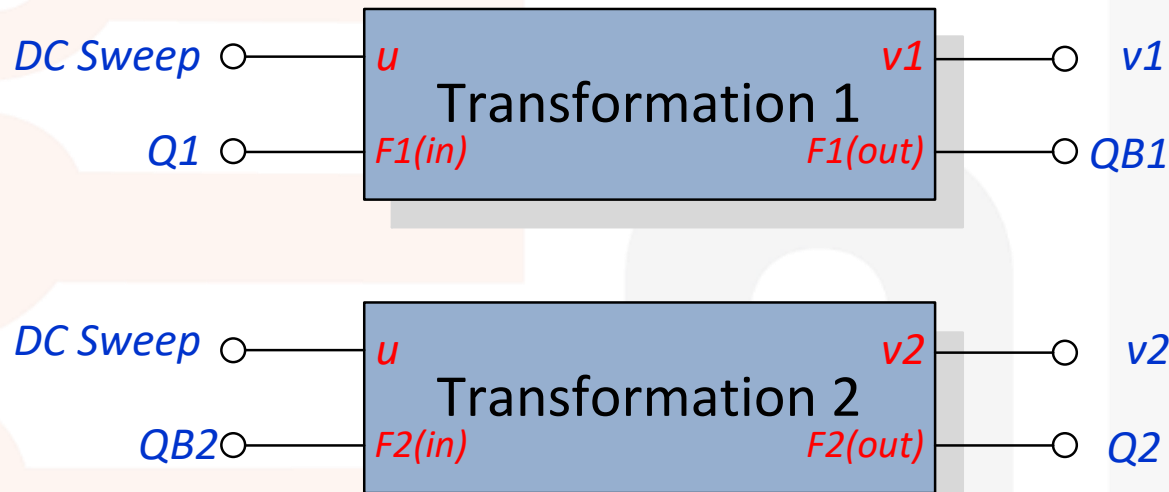- Now, connect F_1 to $Q \rightarrow QB$, and F_2 to $QB \rightarrow Q$.



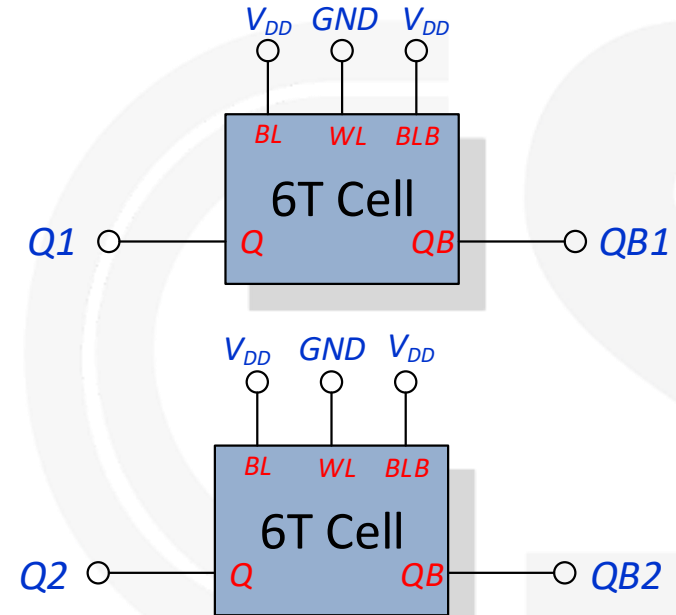- Run a *DC Sweep* on u from $-V_{DD}/\sqrt{2}$ to $V_{DD}/\sqrt{2}$
- This will present the butterfly curves turned 45 degrees.



Final SNM Calculation

- **Now just:**

- Subtract the bottom graph from the top one.
- Find the local maxima for each lobe.
- The smaller of the local maxima is the diagonal of the largest square.
- Multiply this by $\cos 45^\circ$ for the *SNM*

$$SNM = \frac{1}{\sqrt{2}} \cdot \min \left[\max (|v_1 - v_2|) \Big|_{-\sqrt{2} < u < 0}, \max (|v_1 - v_2|) \Big|_{0 < u < \sqrt{2}} \right]$$

Read/Write SNM

- **How about Read SNM:**


- Use the exact same setup.
- Connect *BL* and *BLB* to *VDD*.
- Connect *WL* to *VDD*.
- Run the same calculation.

- **And Write SNM.**


- Now connect one *BL* to *GND*.
- This is trickier, so you'll have to play around with the calculation.
- There are other options for WM calculation.

Testbench Setup – Read/Write

Read Testbench:

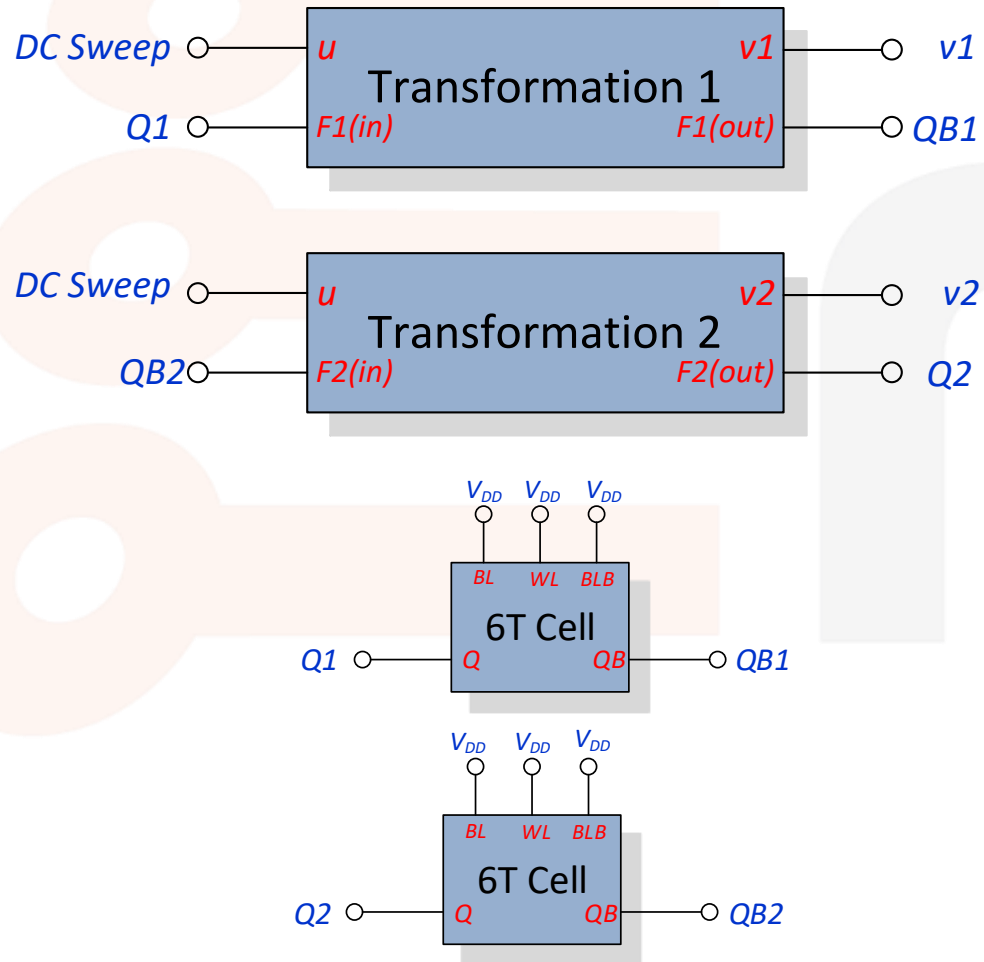

Write Testbench:

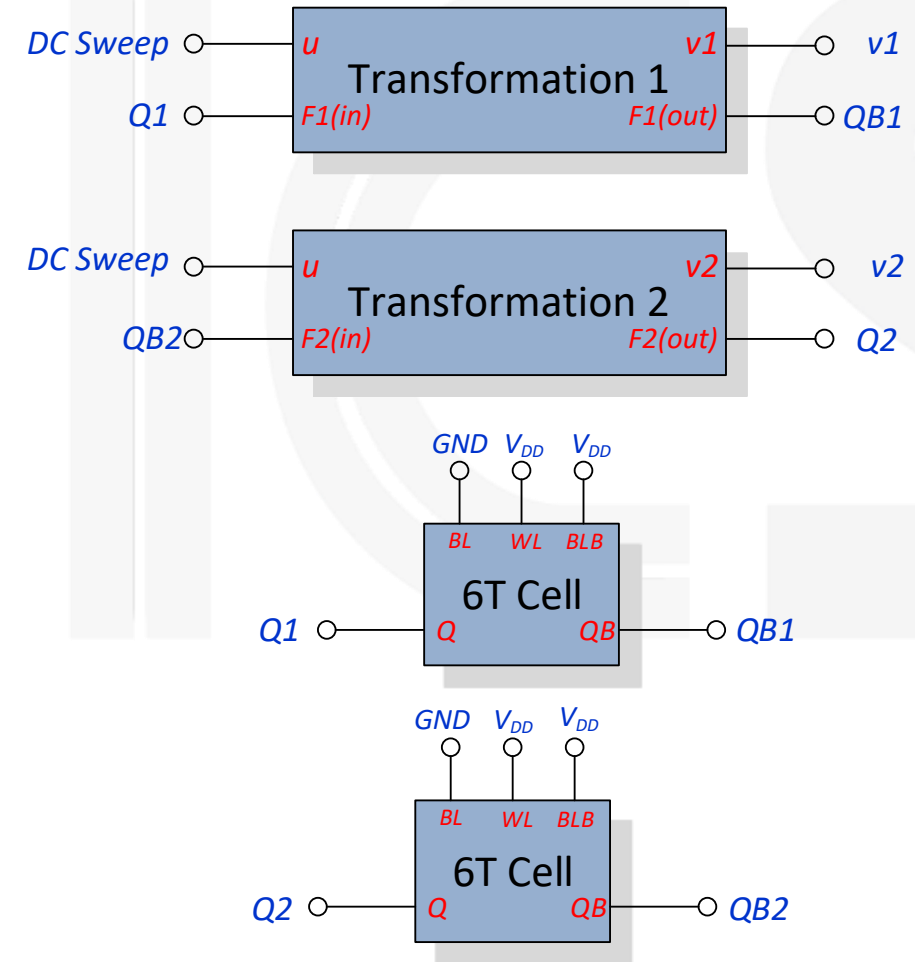

SRAM Stability under process variations



Metastability Convergence in Spectre

- **Node Sets**

- What solution does Virtuoso find with a standard OP?

- To fix this, make sure you use the “**Node Set**” option.

Node Sets vs. Initial Conditions

- **SPICE supports two types of conversion aids :**

- **Node Sets:**

- Help SPICE converge by providing it with an *initial guess*.
 - Used only for DC convergence!
Disregarded for Transient Analysis.

- **Initial Conditions:**

- Enforce a node voltage at time $t=0$.
 - Used only for Transient analysis!
Disregarded for DC convergence.

Additional simulation tips

- **Work with Design Hierarchy**
 - Create transformation functions and DUTs as symbols.
- **Create multiple tests in single ADE-XL view.**
- **Use variables/parameters to define initial conditions/node sets.**
- **Create supply voltages in separate symbol.**
- **Use buffers to smooth transitions and reduce cross cap.**

anics

Further Reading

- Rabaey, et al. “Digital Integrated Circuits” (2nd Edition)
- Elad Alon, Berkeley ee141 (online)
- Weste, Harris, “CMOS VLSI Design (4th Edition)”
- Seevinck, List, Lostroh, “Static Noise Margin Analysis of SRAM Cells”
IEEE Journal of Solid State Circuits, 1987
- Teman and Visotsky. "A fast modular method for true variation-aware separatrix tracing in nanoscaled SRAMs." IEEE TVLSI, 2014.