

Practice 10:

Ratioed Logic

Ratioed vs. Non-Ratioed

- ▶ Standard CMOS is a *non-Ratioed* logic family, because:
 - ▶ The logic function will be correctly implemented regardless of device sizing.
 - ▶ Device sizing will only affect the performance of the gate.
- ▶ A Ratioed gate is a circuit:
 - ▶ That will only function properly if a certain ratio is maintained between the drive strengths of its components.
 - ▶ If the required ratio is not met, the gate's output may be incorrect, the noise margins may become negative, or it may lose its regenerative property.

Why use ratioed circuits?

- ▶ Historically, before CMOS technology was available, it was hard to implement non-ratioed logic.
- ▶ Today, many techniques require ratioed circuits
 - ▶ Such as SRAM design.
- ▶ Pseudo-nMOS is a ratioed logic family that requires less transistors than CMOS and can optimize one transition.

Exercise 1: Pseudo nMOS

Exercise 1a


- ▶ For a pseudo-nMOS inverter with: $V_{Tn} = |V_{Tp}| = 0.4V$ $V_{DSAT} = V_{DD}$
 - ▶ A. Draw the gate's VTC and compute noise margins.

$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$

- ▶ Starting with $V_{in}=0$:

- ▶ M1 is cut-off
- ▶ M2 is in linear

$$V_{OH\max} = V_{DD} = 2.5V$$

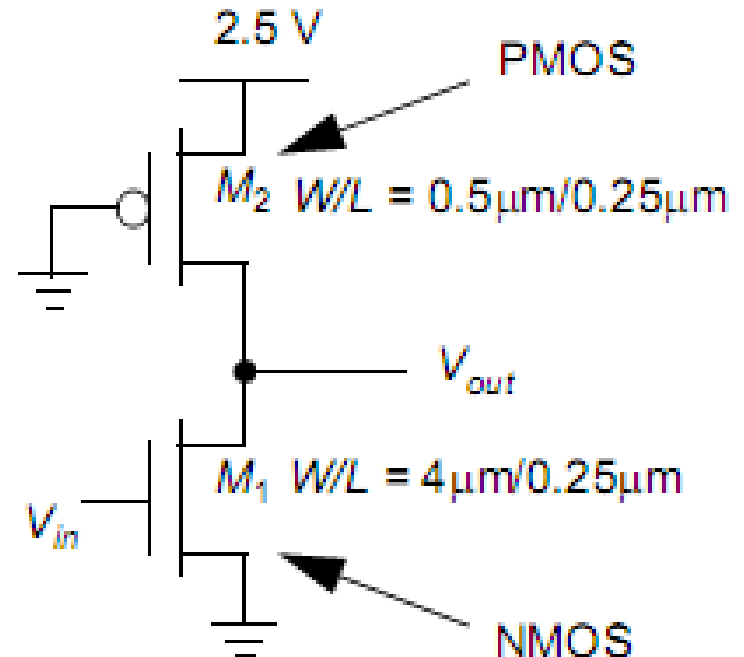


Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$

$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$

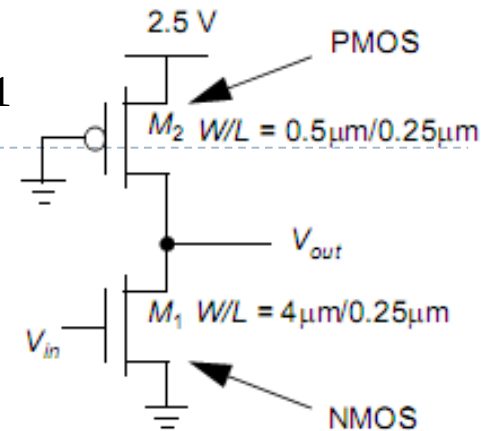- ▶ Raising V_{in} , $M1$ turns on in Saturation, while $M2$ is still linear:



$$I_{SDp} (lin) = I_{DSn} (sat)$$

$$k'_p \frac{W_p}{L_p} \left[(V_{SGp} - |V_{Tp}|) V_{SDp} - 0.5 V_{SDp}^2 \right] = k'_n \frac{W_n}{2L_n} (V_{GSn} - V_{Tn})^2 (1 + \lambda_n V_{DSn})$$

$$k_p \left[(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - 0.5(V_{DD} - V_{out})^2 \right] = r \cdot k_p (V_{in} - V_{Tn})^2$$

$$V_{out} = V_T + \sqrt{(V_{DD} - V_{in})^2 - r(V_T - V_{in})^2}$$

$$k_n = rk_p$$

$$\left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_{IL}} = -1 = \frac{d}{dV_{in}} \left[V_T + \sqrt{(V_{DD} - V_{in})^2 - r(V_T - V_{in})^2} \right]$$


$$V_{IL} = V_T + \frac{V_{DD} - V_T}{\sqrt{r(r+1)}}$$

Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$

$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$
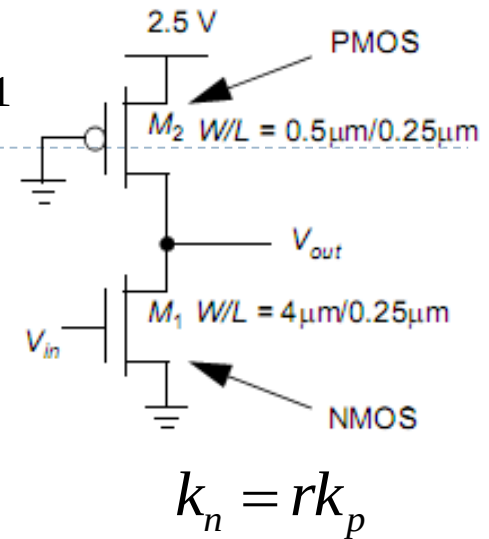
$$V_{IL} = V_T + \frac{V_{DD} - V_T}{\sqrt{r(r+1)}}$$



► Substituting values gives us:

$$k_p = 30\mu \cdot \frac{0.5\mu}{0.25\mu} = 60\mu \quad k_n = 115\mu \cdot \frac{4\mu}{0.25\mu} = 1840\mu \quad r = \frac{1840\mu}{60\mu} = 30.666$$

$$V_{IL} = V_T + \frac{V_{DD} - V_T}{\sqrt{r(r+1)}} = 0.4 + \frac{2.5 - 0.4}{\sqrt{971.11}} = 0.467V$$

$$V_{OH\min} = 0.4 + \sqrt{(2.5 - 0.467)^2 - 30.666(0.467 - 0.4)^2} = 2.4V$$

Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$

$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$


- As V_{in} rises, V_{out} drops, causing M_1 to enter linear and M_2 to saturate:

$$I_{SDp}(sat) = I_{DSn}(lin)$$

$$k'_p \frac{W_p}{2L_p} (V_{SGp} - |V_{Tp}|)^2 (1 + \lambda_p V_{SDp}) = k'_n \frac{W_n}{L_n} [(V_{GSn} - V_{Tn})V_{DSn} - 0.5V_{DSn}^2]$$

$$k_p (V_{DD} - |V_T|)^2 = r \cdot k_p [(V_{in} - V_T)V_{out} - 0.5V_{out}^2]$$


$$V_{out} = (V_{in} - V_T) - \sqrt{(V_{in} - V_T)^2 - \frac{1}{r}(V_{DD} - V_T)^2}$$

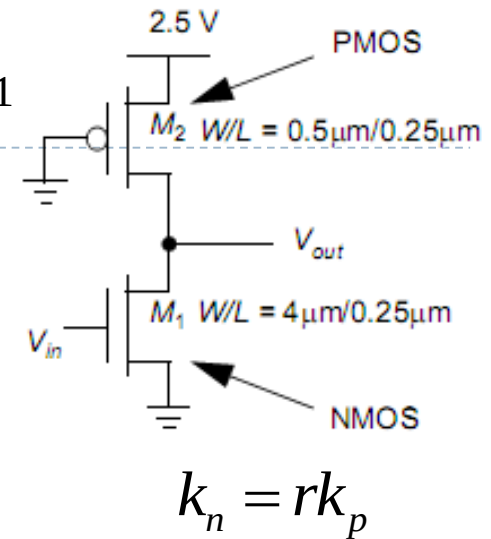

Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
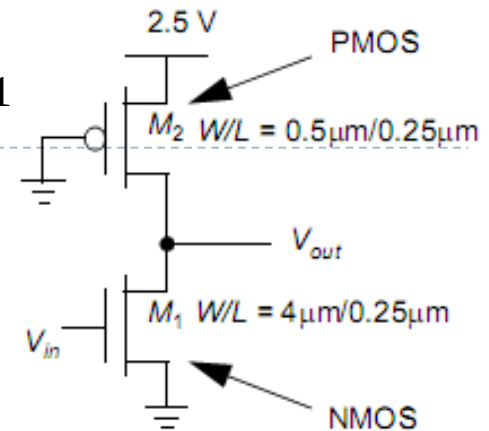
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$



$$V_{out} = (V_{in} - V_T) - \sqrt{(V_{in} - V_T)^2 - \frac{1}{r}(V_{DD} - V_T)^2}$$

► Differentiating, we find:

$$\left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_{IH}} = -1 = \frac{d}{dV_{in}} \left[(V_{in} - V_T) - \sqrt{(V_{in} - V_T)^2 - \frac{1}{r}(V_{DD} - V_T)^2} \right]$$

$$V_{IH} = V_T + \frac{2V_{DD} - V_T}{\sqrt{3r}} = 0.4 + \frac{5 - 0.4}{\sqrt{92}} = 0.88V$$

$$V_{OLmax} = (0.88 - 0.4) - \sqrt{(0.88 - 0.4)^2 - 0.0326(2.5 - 0.4)^2} = 0.18V$$

Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$


- ▶ Finally, we will find V_{OLmin} by setting

$$V_{in} = V_{DD} = 2.5V$$

- ▶ M1 is still in linear and M2 is still saturated
- ▶ The equation we found before is still relevant:

$$V_{out} = (V_{in} - V_T) - \sqrt{(V_{in} - V_T)^2 - \frac{1}{r}(V_{DD} - V_T)^2}$$

$$V_{OLmin} \big|_{V_{in}=V_{DD}} = (V_{DD} - V_T) \left[1 - \sqrt{1 - \frac{1}{r}} \right] = (2.5 - 0.4) \left(1 - \sqrt{0.9674} \right) = 0.0345V$$

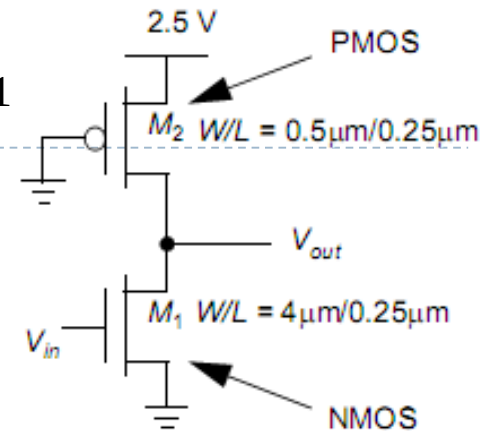


Exercise 1a

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$

- Now we can draw the VTC and find the Noise Margins

$$NM_H = V_{OH\min} - V_{IH} = 2.4 - 0.88 = 1.55V$$
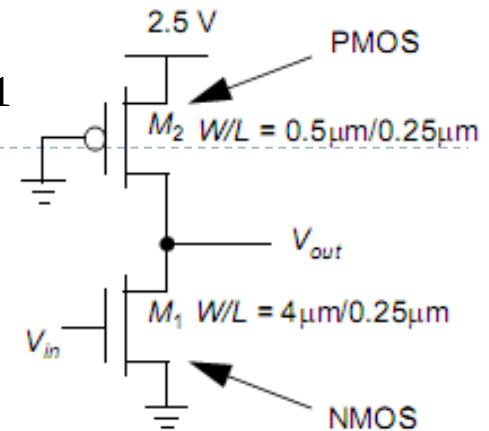
$$NM_L = V_{IL} - V_{OL\max} = 0.467 - 0.18 = 0.28V$$



$$V_{OH\max} = 2.5V$$

$$V_{IL} = 0.467V$$

$$V_{OH\min} = 2.4V$$

$$V_{IH} = 0.88V$$


$$V_{OL\max} = 0.18$$

$$V_{OL\min} = 0.0345V$$

Exercise 1b

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$

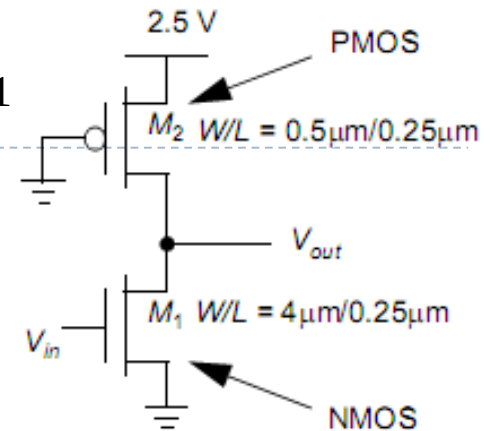- ▶ B. Find the power dissipation with high and low inputs. How is this different than CMOS?




$$I_{static} = \frac{1}{2} k_p (V_{DD} - V_{Tp})^2 (1 + \lambda (V_{DD} - V_{OLmin})) = 165\mu A$$

$$P_{AV} = I_{static} \cdot V_{DD} = 412.5\mu W$$

Exercise 1c

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
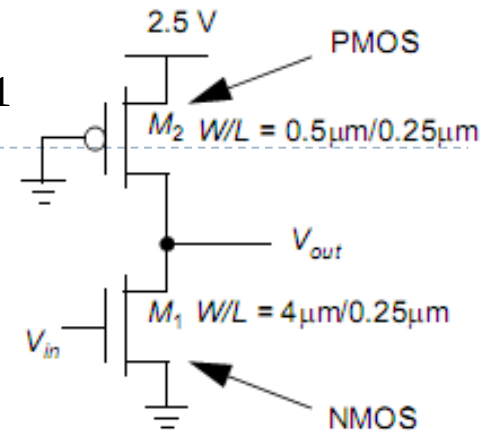
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$




- ▶ C. Find the high-to-low propagation delay of the gate, with an ideal step at the input.
 - ▶ Assume a 10pF load is connected.
 - ▶ Use the average current approximation, but differentiate between currents in different operating modes.
- ▶ At $t < 0$,
 - ▶ $V_{in} = 0$,
 - ▶ $V_{out} = V_{OHmax} = V_{DD}$
- ▶ At $t = 0$, $V_{in} \rightarrow V_{DD}$, and the output starts to discharge:
 - ▶ M1 – saturation
 - ▶ M2 – linear
- ▶ This continues until:
 - ▶ $V_{out} = V_{SGP} - V_T = V_{DD} - V_T$

Exercise 1c

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
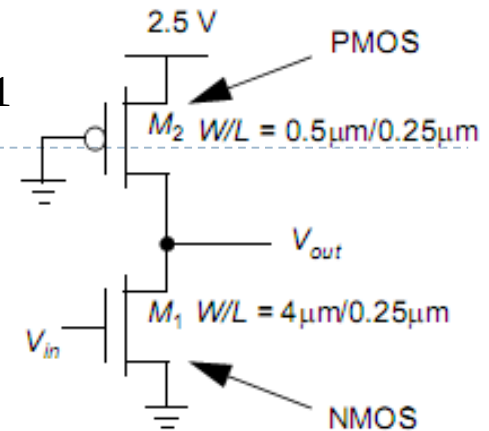
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$



► Therefore we will find the current at:

- $t=0 \rightarrow M1:sat, M2:lin$
- $t=t_1 (V_{out}=V_{DD}-V_T) \rightarrow M1:sat, M2:lin$
- $t=t_{pd} (V_{out}=V_{DD}/2) \rightarrow M1:lin, M2:lin$

► $t=0$

$$V_{GTn} = V_{DD} - V_T \quad V_{DSn} = V_{DD} \quad \Rightarrow SAT$$

$$I_{DSn} = \frac{k_n}{2} (V_{DD} - V_T)^2 (1 + \lambda V_{DD}) = 920\mu (2.1)^2 (1 + \lambda 2.5) = 5mA$$


$$V_{GTP} = V_{DD} - V_T \quad V_{DSP} = 0 \quad \Rightarrow LIN$$

$$I_{SDp} = 0$$

Exercise 1c

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
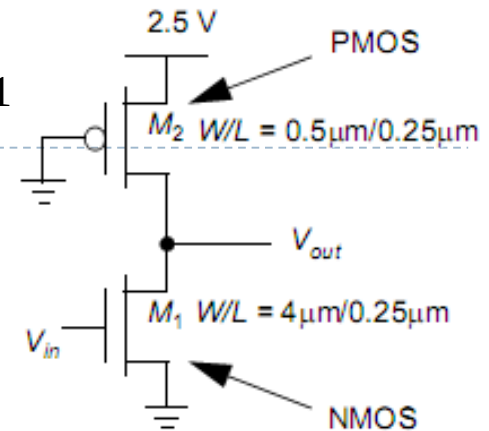
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$



► $t=t_1$

$$V_{GTn} = V_{DD} - V_T \quad V_{DSn} = V_{DD} - V_T \Rightarrow \text{pinch off}$$

$$I_{DSn} = \frac{k_n}{2} (V_{DD} - V_T)^2 (1 + \lambda (V_{DD} - V_T)) = 920\mu (2.1)^2 (1 + \lambda 2.1) = 4.9mA$$


$$V_{GTP} = V_{DD} - V_T \quad V_{DSP} = V_T \Rightarrow LIN$$

$$I_{SDP} = k_p \left[(V_{DD} - V_T) V_T - 0.5 V_T^2 \right] = 60\mu \left[(2.1) 0.4 - 0.5 \cdot 0.4^2 \right] = 45.6\mu A$$

Exercise 1c

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$
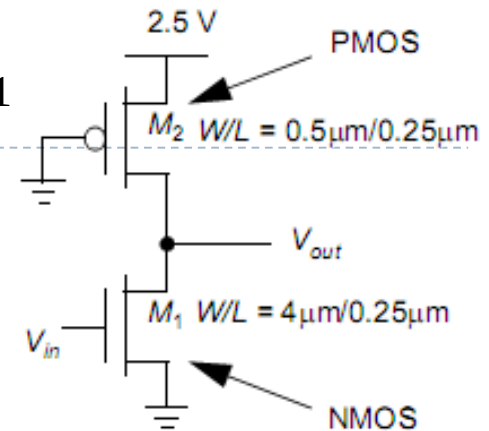
$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$



► $t = t_{pd}$

$$V_{GTn} = V_{DD} - V_T$$

$$V_{DSn} = V_{DD} / 2 \Rightarrow LIN$$

$$I_{DSn} = k_n \left[(V_{DD} - V_T) \frac{V_{DD}}{2} - 0.5 \left(\frac{V_{DD}}{2} \right)^2 \right] = 1840\mu \left[(2.1)1.25 - 0.5 \cdot 1.25^2 \right] = 3.4mA$$

$$V_{GTP} = V_{DD} - V_T$$

$$V_{DSP} = V_{DD} / 2 \Rightarrow LIN$$

$$I_{SDp} = k_p \left[(V_{DD} - V_T) \frac{V_{DD}}{2} - 0.5 \left(\frac{V_{DD}}{2} \right)^2 \right] = 60\mu \left[(2.1)1.25 - 0.5 \cdot 1.25^2 \right] = 110.6\mu A$$

Exercise 1c

$$V_{Tn} = |V_{Tp}| = 0.4V \quad V_{DSAT} = V_{DD}$$

$$k'_n = 115\mu \quad k'_p = 30\mu \quad \lambda_p = \lambda_n = 0.1$$

$$I_{t_0} = I_{n0} = 5mA \quad I_{t_1} = I_{n1} - I_{p1} = 4.9mA - 45.6\mu = 4.85mA$$

$$I_{tpd} = I_{tpd,n} - I_{tpd,p} = 3.4mA - 110.6\mu = 3.29mA$$

► Calculate t_1-0 :

$$(t_1 - 0) = C_L \frac{V_{DD} - (V_{DD} - V_T)}{0.5(I_{t_0} + I_{t_1})} = \frac{10p \cdot 0.4}{4.925mA} = 812ps$$

► Calculate $t_{pd}-t_1$:

$$(t_{pd} - t_1) = C_L \frac{(V_{DD} - V_T) - V_{DD}/2}{0.5(I_{t_1} + I_{t_{pd}})} = \frac{10p \cdot 0.85}{4.07mA} = 2ns$$

