

Practice 11:

Pass Transistor Logic

Using a MOSFET as a switch

Looking at an nMOS as a switch

Is a PTL switch an AND gate?

Exercise 1: PTL Switch


Exercise 1a

$$\mu_n C_{ox} = 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V;$$

$$\gamma = 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1$$

$$V_{DD} = 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF$$

 - ▶ A. Draw the VTC of the PTL switch shown here (with $V_G = V_{DD}$).



- ▶ Starting with $V_{in}=0$:
 - ▶ We can mark the source at V_{in} .

$$V_{GSn} = V_{DD} - V_{in} > V_T \Rightarrow ON$$

- ▶ Therefore, V_{out} will discharge down to 0.

Exercise 1a


$$\mu_n C_{ox} = 50 \mu; \mu_p C_{ox} = 20 \mu; |V_{T0}| = 1V;$$

$$\gamma = 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1$$

$$V_{DD} = 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF$$

- ▶ As we raise V_{in} :
 - ▶ We can mark the source at V_{out} .
 - ▶ As long as $V_{GSn} = V_{DD} - V_{out} > V_T$
 - ▶ The PTL is on and $V_{out} = V_{in}$.
- ▶ When V_{out} reaches $V_{DD} - V_T$
 - ▶ Now $V_{GSn} = V_{DD} - V_{out} = V_T$
 - ▶ The PTL is cut-off.
 - ▶ We continue to raise V_{in} , but:

$$V_{OH \max} = V_{DD} - V_T$$

 


Exercise 1a

$$\mu_n C_{ox} = 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V;$$

$$\gamma = 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1$$

$$V_{DD} = 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF$$

- ▶ So let's draw the VTC:
- ▶ We see that:
 - ▶ The PTL is non-inverting.
 - ▶ The PTL is non-digital.
 - ▶ The PTL has a “*Weak 1*”

 

Exercise 1b

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

► B. Calculate V_{OHmax} .

► We already saw that: $V_{OHmax} = V_{DD} - V_T$

► But we can't help noticing that:

$$V_{SB} = V_{out} - 0 = V_{out} > 0$$


► Therefore, the PTL is Reverse Biased with

$$V_T > V_{T0}$$

► We know that: $V_T = V_{T0} + \gamma \left(\sqrt{|-2\Phi_F + V_{out}|} - \sqrt{|-2\Phi_F|} \right)$

► And at $V_{out} = V_{OHmax}$ we get:

$$V_{OHmax} = V_{DD} - V_T = V_{DD} - \left[V_{T0} + \gamma \left(\sqrt{|-2\Phi_F + V_{OHmax}|} - \sqrt{|-2\Phi_F|} \right) \right]$$

 

Exercise 1b

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

$$V_{OH\max} = V_{DD} - V_{T0} - \gamma \left(\sqrt{|-2\Phi_F + V_{OH\max}|} - \sqrt{|-2\Phi_F|} \right)$$

► So now we can find $V_{OH\max}$.


$$\begin{aligned}V_{OH\max} &= V_{DD} - V_{T0} - \gamma \left(\sqrt{|-2\Phi_F + V_{OH\max}|} - \sqrt{|-2\Phi_F|} \right) \\ &= 5 - 1 - 0.5 \left(\sqrt{0.6 + V_{OH\max}} - \sqrt{0.6} \right)\end{aligned}$$

$$2V_{OH\max} - 8 - 0.77 = \sqrt{0.6 + V_{OH\max}}$$

$$4V_{OH\max}^2 - 35V_{OH\max} + 77 = 0.6 + V_{OH\max}$$

$$V_{OH\max} = 3.42V$$


$$V_T = V_{DD} - V_{OH\max} = 1.58V$$

 

Exercise 1c

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

 - ▶ C. Assuming $V_{out}(0)=0$, find the propagation delay for charging the output to $V_{DD}/2$:



- ▶ At $t=0$, V_{in} rises to V_{DD} , with V_{out} low:
 - ▶ The source is at V_{out} .

$$V_{GSn} = V_{DD} - V_{out} = V_{DD}$$

$$V_{DSn} = V_{DD} - V_{out} = V_{DD}$$

$$V_{BSn} = 0 - V_{out} = 0 \Rightarrow V_T = V_{T0}$$

- ▶ Therefore the PTL is in saturation with:

$$I_{DS}(0) = \frac{k_n}{2} (V_{DD} - V_{T0})^2 (1 + \lambda V_{DD}) = \frac{50\mu}{2} \frac{4\mu}{2\mu} (5 - 1)^2 (1 + 0.1 \cdot 5) = 1.2mA$$

Exercise 1c

$$\mu_n C_{ox} = 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V;$$

$$\gamma = 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1$$

$$V_{DD} = 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF$$


- ▶ At $V_{DD}/2$ we will first find V_T :

$$V_T(V_{out} = 2.5V) = 1 + 0.5(\sqrt{0.6 + 2.5} - \sqrt{0.6}) = 1.49V$$

- ▶ At this point: $V_{GSn} = V_{DSn} = V_{DD} - V_{out} = V_{DD}/2$

- ▶ So the transistor is still saturated with:

$$\begin{aligned} I_{DS}\left(\frac{V_{DD}}{2}\right) &= \frac{k_n}{2} \left(\frac{V_{DD}}{2} - V_T\right)^2 \left(1 + \lambda \frac{V_{DD}}{2}\right) \\ &= \frac{50\mu}{2} \frac{4\mu}{2\mu} (2.5 - 1.49)^2 (1 + 0.1 \cdot 2.5) = 64\mu A \end{aligned}$$

 

Exercise 1c

$$\mu_n C_{ox} = 50 \mu; \mu_p C_{ox} = 20 \mu; |V_{T0}| = 1V;$$


$$\gamma = 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1$$

$$V_{DD} = 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF$$

- Therefore the average current is:

$$I_{Avg} = \frac{1.2m + 64\mu}{2} = 632\mu A$$


$$t_{pLH} = C_L \frac{V_{DD}/2 - 0}{I_{Avg}} = 50f \cdot \frac{2.5}{632\mu} = 198p \text{ sec}$$

 

Exercise 1d

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

 - ▶ The input now changes from 1 to 0.
- ▶ D. Calculate the time it takes the PTL to discharge the output past $V_{DD}/2$.



- ▶ The most important aspect here is that the **Source and Drain change sides!**

$$V_{GSn} = V_{DD} - V_{in} = V_{DD}$$

Exercise 1d


$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

- In this case:

$$V_{SBn} = 0 \Rightarrow V_T = V_{T0}$$

$$V_{GTn} = V_{DD} - V_{T0}$$

$$V_{DSn} = V_{out} - V_{in} = V_{out}$$

 


- So the PTL is in linear throughout the transition, because:

$$V_{DS} = V_{out} \leq V_{OH\max} < V_{DD} - V_{T0} = V_{GTn}$$

Exercise 1d

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF\end{aligned}$$

► So at $t=0$

 

$$I_{DS}(V_{out} = V_{OH\max}) = k_n \left[(V_{DD} - V_{T0}) V_{OH\max} - \frac{1}{2} V_{OH\max}^2 \right] = 783\mu A$$

$$I_{DS}(V_{out} = 2.5V) = k_n \left[(V_{DD} - V_{T0}) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2} \right)^2 \right] = 687\mu A$$

$$I_{Avg} = \frac{783\mu + 687\mu}{2} = 735\mu A$$

$$t_{pHL} = C_L \frac{V_{OH\max} - V_{DD}/2}{I_{Avg}} = 50f \cdot \frac{3.42 - 2.5}{735\mu} = 62p\text{sec}$$


Exercise 1e

- ▶ Looking at the VTC, we see that the PTL gate is not digital.
 - ▶ No regenerative property
 - ▶ No distinguished 1 and 0
 - ▶ Non-positive Noise margins
- ▶ Therefore to make it digital, we can cascade a CMOS inverter after it with.

- ▶ E. Find the static power dissipated when a CMOS inverter with

$$(W/L)_p = 2.5(W/L)_n = 10\mu/2\mu;$$

is connected to the output of the PTL gate.

 

Exercise 1e

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF \\ INV : (W/L)_p &= 2.5(W/L)_n = 10\mu/2\mu;\end{aligned}$$


▶ When $V_{in}=0$, $V_{out}(PTL)=0$, therefore:

▶ The nMOS of the inverter is cut-off.

▶ $V_{out}(INV) = V_{OHmax}(INV) = V_{DD}$

▶ No static current exists.

▶ $P_{static} = 0$

 


Exercise 1e

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF \\ INV : (W/L)_p &= 2.5(W/L)_n = 10\mu/2\mu;\end{aligned}$$

► However, when

- $V_{in} = V_{DD}$
- $V_{out}(PTL) = V_{OHmax}$

$$\begin{aligned}V_{SGp} &= V_{DD} - V_{out}(PTL) \\ &= V_{DD} - (V_{DD} - V_{Tn}|_{V_{SB}>0}) > V_{Tp0}\end{aligned}$$

 


- So both the pMOS and the nMOS of the inverter are conducting!

Exercise 1e

$$\begin{aligned}\mu_n C_{ox} &= 50\mu; \mu_p C_{ox} = 20\mu; |V_{T0}| = 1V; \\ \gamma &= 0.5V^{1/2}; \Phi_F = -0.3V; \lambda = 0.1 \\ V_{DD} &= 5V; (W/L)_n = 4\mu/2\mu; C_L = 50fF \\ INV : (W/L)_p &= 2.5(W/L)_n = 10\mu/2\mu;\end{aligned}$$

- ▶ We can calculate the static current in two ways:

 - ▶ 1. Find the *linear* current through the nMOS.
- ▶ 2. Find the *saturation* current through the pMOS.




- ▶ In both cases, we need to first find $V_{out}(INV)$
- ▶ But to shorten things, let's just neglect the *channel length modulation* and find the saturation current of the pMOS:

$$I_{static} = I_{SDp} = \frac{k_p}{2} \left((V_{DD} - V_{OH_{max}}) - |V_{Tp}| \right)^2 = \frac{1}{2} \cdot 20\mu \cdot \frac{10\mu}{2\mu} (5 - 3.42 - 1)^2 = 17\mu A$$

$$P_{static} = I_{static} \cdot V_{DD} = 84\mu W$$

Exercise 1f

- ▶ F. How can we solve the “weak I” problem?
 - ▶ Method I: Bleed Transistor

 

Exercise 1f

- ▶ F. How can we solve the “weak 1” problem?
 - ▶ Method 2: Pass Gate

