

Practice 2: Digital Systems

Boolean Algebra:

A few important identities:

1. $A \cdot \bar{A} = 0$ $A \cdot A = A = A + A$
2. $A + \bar{A} = 1 = 1 + x$
3. $A + \bar{A}B = A + B$ $\bar{A} + AB = \bar{A} + B$
4. $\overline{AB} = \bar{A} + \bar{B}$ $\overline{A + B} = \bar{A} \cdot \bar{B}$

Example 1: Function Minimization

Minimize the following expression:

$$(\bar{A} + ABC\bar{C}) + (A + \bar{A}\bar{B}C)\left(\overline{A(\bar{A} + \bar{B} + C)}\right)$$

Solution:

$$\begin{aligned} & (\bar{A} + ABC\bar{C}) + (A + \bar{A}\bar{B}C)\left(\overline{A(\bar{A} + \bar{B} + C)}\right) = \\ & \quad \overline{A(\bar{A} + \bar{B} + C)} = \bar{A} + \overline{\bar{A} + \bar{B} + C} = \bar{A} + ABC = \bar{A} + BC \\ & (\bar{A} + BC) + (A + \bar{B}C)(\bar{A} + BC) = \\ & (\bar{A} + BC)(1 + (A + \bar{B}C)) = \bar{A} + BC \end{aligned}$$

Example 2: Complementary Functions

Find the complementary expression for:

$$f = A + BC + \bar{A}\bar{B}$$

Solution:

$$\begin{aligned}\bar{f} &= \overline{A + BC + \bar{A}\bar{B}} = (\text{DeMorgan}) = \\ &= \bar{A} \cdot \overline{BC} \cdot \overline{\bar{A}\bar{B}} = \bar{A} \cdot (\bar{B} + \bar{C}) \cdot (A + B) = \\ &\quad \bar{A} \cdot (A + B) = \bar{A}B \\ &= \bar{A}B \cdot (\bar{B} + \bar{C}) = \\ &\quad B \cdot (\bar{B} + \bar{C}) = B\bar{C} \\ &= \bar{A}B\bar{C}\end{aligned}$$

Example 3: Universality


Implement the following function with NAND and NOT gates:

$$f = ABC + \bar{A}\bar{C} + D$$

Solution:

An important step in implementation of digital circuits is finding the *inverting* representation of the function. To do this we will apply a *double inverting* operator:

$$\begin{aligned}\bar{\bar{f}} &= \overline{\overline{ABC + \bar{A}\bar{C} + D}} = (\text{DeMorgan}) = \\ &= \overline{\bar{A}BC \cdot \bar{\bar{A}}\bar{\bar{C}} \cdot \bar{D}}\end{aligned}$$

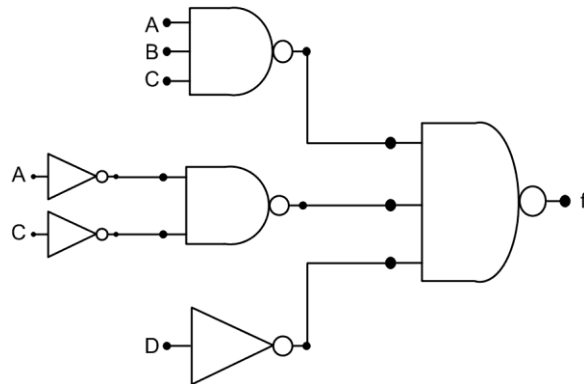

Example 4: Multiplexers

A Multiplexer is a complex gate that receives 2^N inputs, N selectors and propagates one output. Muxes are one of the most important and useful gates in digital design. In this example, we will implement a standard logic function using the universality of multiplexers:

Implement the following function using 4:1 multiplexers:

$$f(A, B, C, D) = \sum(0, 1, 5, 7, 13, 14)$$

Solution:

1. First, we'll draw the Karnaugh Map of the function:
2. A 4:1 Multiplexer receives 2 selectors, so we can make two-variable circles to define the output of each state of the mux. We will choose AB as the selectors for the first mux:

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	1	1	0
11	0	1	0	0
10	0	0	1	0

3. As we can see, we have arrived at four partial expressions:

$$f(\bar{A}\bar{B}) = \bar{C}$$

$$f(\bar{A}B) = D$$


$$f(AB) = C \oplus D$$

$$f(A\bar{B}) = 0$$

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	1	1	0
11	0	1	0	0
10	0	0	1	0

$\bar{A}\bar{B}$ $\bar{A}B$ AB $A\bar{B}$

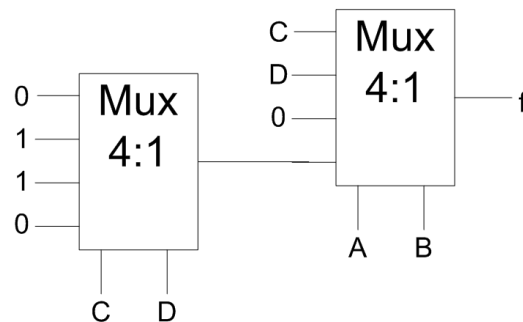4. We can implement this function with two 4:1 muxes:



Bonus Question (if we have time)

- A. Create a leading zeros detector for a four bit vector.
- B. Use the answer to A to create a leading zeros detector for a 16-bit vector.

Bonus 2:

Using 3 Shift Registers and an n-bit adder, design a circuit that receives incrementing integers and outputs their squared value. (1, 4, 9, 16...)