


# Practice 3: Terminology and Design Metrics

## Voltage Transfer Characteristic:

The VTC of a digital logic gate shows its DC reaction to varying inputs by plotting  $V_{out}/V_{in}$ .

The VTC teaches us a lot about the quality of the gate through the following parameters:

 1. Regenerative Property
2. Nominal Voltage Levels ( $V_{OHmax}$  and  $V_{OLmin}$ )
3. Switching Threshold ( $V_M$ )
4. Gain
5. Transition width and Noise Margins



## Exercise 1:

Find the properties of the following inverter VTC:

### Solution:

1. We'll find  $V_{OHmax}$ ,  $V_{OLmin}$  at the end points of the graph, where  $V_{in}=0V$  and  $V_{in}=5V$ :

$$V_{OHmax}=4.8V, V_{OLmin}=0.2V$$

2. To find  $V_M$  we'll find the intersection between the VTC and  $V_{in}=V_{out}$

$$V_M=2.25V$$

3. Next we'll find the points where the VTC slope (gain) is -1.

The input voltages at these points are  $V_{IH}$  and  $V_{IL}$ .

$$V_{IL}=1.45V, V_{IH}=2.9V$$

4. We can now find  $V_{OHmin}$  and  $V_{OLmax}$  – the outputs of  $V_{IL}$  and  $V_{IH}$ :

$$V_{OHmin} = f(V_{IL}) = 4.5V$$


$$V_{OLmax} = f(V_{IH}) = 1V$$

5. Accordingly, we can calculate the *Transition Width* and the *Noise Margins*:

$$TransitionWidth = V_{IH} - V_{IL} = 2.9 - 1.45 = 1.45V$$

$$NM_H = V_{OHmin} - V_{IH} = 4.5 - 2.9 = 1.6V$$
 
$$NM_L = V_{IL} - V_{OLmax} = 1.45 - 1 = 0.45V$$



6. The gain of the gate can be expressed as the slope between the points of  $V_{IL}$  and  $V_{IH}$ .

$$g = \frac{4.5 - 1}{1.45 - 2.9} = -2.4$$

7. The larger the gain (more negative) the better. Large the Noise Margins and a small Transition Width are desirable.

## Exercise 2:

An amplifier, operating from a 5V supply, limits 1.5V from the upper supply rail (at 5V) and 0.5V from the lower rail (at 0V). It has a relatively constant gain of -10V/V in the transition region, which is centered at  $V_M = 2.5V$ .

- Use a three-segment VTC approximation to find  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$ ,  $V_{IH}$ ,  $NM_L$  and  $NM_H$ .
- How wide is the transition region? If it is doubled in width do to manufacturing error, what do the noise margins become?
- If you had a choice of relocating the center of the transition region, where would you put it?

## Solution

1. From the description:

$$V_{OL} = V_{OL\min} = V_{OL\max} = 0 + 0.5 = 0.5V,$$

$$V_{OH} = V_{OH\max} = V_{OH\min} = 5 - 1.5 = 3.5V$$

2. The three-segment VTC approximation is shown here.

3. Knowing the gain and substituting  $V_M = 2.5$ , we get:

$$V_{out} = -10V_{in} + 27.5$$

4. Now we can find  $V_{IL}$  and  $V_{IH}$ :

$$3.5 = -10V_{IH} + 27.5 \Rightarrow V_{IH} = 2.7V$$

$$0.5 = -10V_{IL} + 27.5 \Rightarrow V_{IL} = 2.4V$$

5. To find the transition width:  $\Delta V = V_{IH} - V_{IL} = 0.3V$

6. We can now calculate the noise margins:


$$NM_H = V_{OH} - V_{IH} = 3.5 - 2.7 = 0.8V \quad NM_L = V_{IL} - V_{OL} = 2.4 - 0.5 = 1.9V$$

7. If the transition region doubles to  $\Delta V = 0.6V$ , the noise margins are reduced by 0.3V:

$$NM'_H = NM_H - 0.15 = 0.65V \quad NM'_L = NM_L - 0.15 = 1.75V$$

 8. We'd want to make the inverter symmetrical with equal high and low noise margins, so we'd move  $V_M$  to the midpoint between  $V_{OL}$  and  $V_{OH}$ :

$$V'_M = V_{OL} + \frac{V_{OL} + V_{OH}}{2} = 0.5 + \frac{3.5 - 0.5}{2} = 2V$$




### Dynamic Properties:

Propagation Delay ( $t_p$  or  $t_{pd}$ ) of a gate is the time it takes for a 50% change in the input to cause a 50% change in the output.

Rise Time ( $t_r$ ) and Fall Time ( $t_f$ ) are the time it takes a signal to change from 10% to 90%.

 $t_{pd}$  describes the two-sided functionality of a *gate*, while  $t_r/t_f$  describe the one-sided functionality of a *signal*.



### Exercise 3:

Find the propagation delay and rise time of a simple RC Circuit with a step signal input.

#### ***Solution:***

- As we saw during practice 1:


$$V_{in} = V_R + V_{out} = i_c R + V_{out} = RC \dot{V}_{out} + V_{out}$$

$$V_h = K e^{-t/\tau} \quad \tau \triangleq RC \quad V_p = V_{in}$$

$$V_{out}(t) = K e^{-t/\tau} + V_{in}$$

$$V_{out}(0) = 0 = K e^{-0/\tau} + V_{in} \Rightarrow K = -V_{in}$$
 
$$V_{out}(t) = \left(1 - e^{-t/\tau}\right) V_{in}$$



- Since we assumed a zero-time step input at the input, the propagation delay is the time it takes the output to reach 50% of  $V_{in}$ :

$$V_{out}(t_{pd}) = 0.5V_{in} = \left(1 - e^{-t_{pd}/\tau}\right) V_{in}$$

$$e^{-t_{pd}/\tau} = \frac{0.5V_{in}}{V_{in}} \Rightarrow t_{pd} = -\tau \cdot \ln 0.5 = 0.69\tau$$

- To find the rise time, we need to find when the voltage reaches  $0.1V_{in}$  and  $0.9V_{in}$ :

$$V_{out}(t_{10\%}) = 0.1V_{in} \Rightarrow t_{10\%} = -\tau \ln 0.9 = 0.1\tau$$

$$V_{out}(t_{90\%}) = 0.9V_{in} \Rightarrow t_{90\%} = -\tau \ln 0.1 = 2.3\tau$$

$$t_r = t_{90\%} - t_{10\%} = 2.2\tau$$

## Power Dissipation:

The power dissipation of a digital circuit is composed of:

1. **Dynamic Power**: The power consumed during a switching (active) action. This power is generally used to charge/discharge a capacitance that represents the logic level.
2. **Static Power**: The power consumed by the circuit during its steady state, while it keeps its previous logic level. This is usually considered leakage power.

## Exercise 4:

Find the power dissipation of a simple RC network connected to a step input toggling at a frequency of  $f$  (assume  $1/f \gg 3\tau$ ).

## ***Solution***

1. We will first measure the energy needed to fully charge the capacitor:

$$E_{switch} = \int_0^\infty i_{in}(t)v_{in}(t)dt = V_{in} \int_0^\infty C \frac{dv_{out}}{dt} dt = CV_{in} \int_0^{V_{in}} dV_{out} = CV_{in}^2$$

2. Power (or average power) is the amount of energy dissipated per second. With a frequency of  $f$ , we have  $f$  switching operations per second, so we get:

$$P_{dynamic} = fE_{switch} = fCV_{in}^2$$

3. Considering an ideal capacitor, no current exists in steady state, so:

$$P_{static} = 0$$

4. Altogether we get:

$$P_{total} = P_{dynamic} + P_{static} = fCV_{in}^2$$