
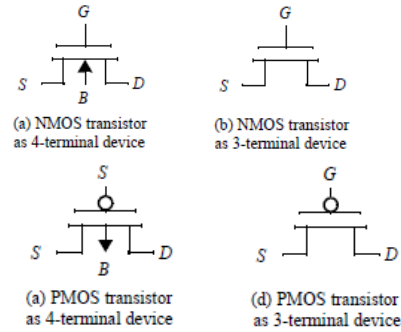


Practice 4: Semiconductors

The MOS Transistor:

 

Regions of Operation:

$I_{DS} = 0$	$V_{GS} < V_T$	Cut-Off
$k'_n \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$	$V_{GS} > V_T, V_{DS} < V_{GS} - V_T$	Linear/Ohmic
$k'_n \frac{W}{2L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$	$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$	Saturation
$I_{DS} = k'_n \frac{W}{L} \left((V_{GS} - V_{TH}) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$	$V_{GS} > V_T, V_{DS} > V_{DSAT}$	Velocity Saturation

When discussing pMOS transistors:

1. Everything that was positive is now negative, for example we need $V_{GS} < 0$ to turn the transistor on.
2. To make it more intuitive, we can look at the voltages upside down, in other words, use V_{SG}, V_{SD}, I_{SD} , etc.
3. In any case, the threshold voltage of a pMOS is negative ($V_{Tp} < 0$). To use our “upside down” voltages, we need to use the absolute value of V_{Tp} , so we get:

$I_{SD} = 0$	$V_{SG} < V_{Tp} $	Cut-Off
$k'_p \frac{W}{L} \left[(V_{SG} - V_{Tp}) V_{SD} - \frac{V_{SD}^2}{2} \right]$	$V_{SG} > V_{Tp} , V_{SD} < V_{SG} - V_{Tp} $	Linear/Ohmic
$k'_p \frac{W}{2L} (V_{SG} - V_{Tp})^2 (1 + \lambda V_{SD})$	$V_{SG} > V_{Tp} , V_{SD} > V_{SG} - V_{Tp} $	Saturation
$I_{SD} = k'_p \frac{W}{L} \left((V_{SG} - V_{Tp}) V_{DSAT} - \frac{ V_{DSAT} ^2}{2} \right)$	$V_{SG} > V_{Tp} , V_{SD} > V_{DSAT} $	Velocity Saturation

Exercise 1:

Consider a process technology for which:

$$L_{\min} = 0.4\mu m \quad t_{ox} = 8nm \quad \mu_n = 450 \frac{cm^2}{V \cdot s} \quad V_T = 0.7V \quad \lambda \approx 0 \quad \epsilon_{ox} = 3.45 \cdot 10^{-11}$$

- Find C_{ox} and k_n'
- For a MOSFET with $\frac{W}{L} = \frac{8\mu m}{0.8\mu m}$, calculate the values of V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a DC current of $I_{DS} = 100\mu A$.
- For the device in (b), find the value of V_{GS} required to cause the device to operate as a 1000Ω resistor for very small V_{DS} .

Solution

$$a. \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \cdot 10^{-11}}{8 \cdot 10^{-9}} = 4.32 \cdot 10^{-3} \frac{F}{m^2} = 4.32 \frac{fF}{\mu m^2}$$

$$k_n' = \mu_n C_{ox} = 450 \frac{cm^2}{V \cdot s} \cdot 4.32 \frac{fF}{\mu m^2} = 1.94 \cdot 10^{-6} \frac{F}{V \cdot s} = 194 \frac{\mu A}{V^2}$$

$$b. \quad \text{For operation in the saturation region: } I_{DS} = \frac{k_n'}{2} \cdot \frac{W}{L} (V_{GS} - V_T)^2$$

$$\text{so for a current of } 100\mu A, \text{ we get: } 100 = 0.5 \cdot 194 \cdot \frac{8}{0.8} (V_{GS} - 0.7)^2$$

$$V_{GS} - 0.7 = 0.32V \longrightarrow V_{GS} = 1.02V \quad \text{and} \quad V_{DSmin} = V_{GS} - V_T = 0.32V$$

- c. For the MOSFET in the Ohmic/Linear/Triode region with a very small V_{DS} (so $V_{DS}^2 \rightarrow 0$):

$$I_{DS} = k_n' \frac{W}{L} (V_{GS} - V_T) V_{DS} \quad \text{To find the drain to source resistance: } R_{DS} = \frac{V_{DS}}{I_{DS}} = \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_T)}$$


$$\text{Thus: } 1000 = \frac{1}{194 \cdot 10^{-6} \cdot 10 (V_{GS} - 0.7)} \longrightarrow V_{GS} - 0.7 = 0.52V \longrightarrow V_{GS} = 1.22V$$

Exercise 2:

Two serially connected NMOS transistors are connected to the same gate voltage, as shown. The following parameters are given:

$$K = K_1 = K_2 = 20 \mu A / V^2 \quad V_{T1} = V_{T2} = V_T = 1V \quad V_{DD} = 3V$$

 - Prove that if N_1 is cut off, M_2 is cut off as well.
- Prove that N_1 can never be saturated.
- Find the state of the transistors as we raise V_G from 0 to 5V.
- The threshold of M_1 was doubled ($V_{T1}=2V$). Can both transistors be saturated at the same time?
- Show that the given configuration is equivalent to one transistor with $K_{eq}=0.5K$ when M_1 is ohmic and M_2 is saturated.



Solution

- We know that N_1 is cut off, so: $V_{GS1} = V_G < V_T$
Looking at N_2 we see that $V_{GS2} = V_G - V_{out} < V_G < V_T \rightarrow$ Cut-off!
- Let's assume that N_1 is saturated, so: $V_{DS1} > V_{GS1} - V_T \Leftrightarrow V_{out} > V_G - V_T$
Now we'll see what state N_2 is in: $V_{GS2} = V_G - V_{out} < V_G - (V_G - V_T) = V_T$
So $V_{GS2} < V_T$ meaning that N_2 is cut off. That contradicts the conduction of N_1 , so we proved that N_1 can't be saturated!
- For a $V_G < V_T$ we know both transistors are cut off.
When $V_G = V_T$, N_1 turns on and we know it can't be saturated, so it's ohmic.
Now $V_{GS2} - V_T = V_G - V_{out} - V_T \big|_{V_G \approx V_T} = -V_{out} < V_{DS2}$ so N_2 is saturated!
If V_G and V_{out} get high enough, N_2 will go into ohmic conduction. Let's see if and when it happens. We'll see what happens on the border of saturation: $V_{DS2} = V_{GS2} - V_T$
 $V_{DD} - V_{out} = (V_G - V_{out}) - V_T \Rightarrow V_G = V_{DD} + V_T$ (note: this is higher than the supply)
Let's summarize it in a table:

V_G	N_1	N_2
$0 < V_G < V_T$	Cut-off	Cut-off
$V_T < V_G < V_{DD} + V_T$	Linear	Saturation
$V_G > V_{DD} + V_T$	Linear	Linear

- Our condition for M_2 to be saturated still stands: $V_G < V_{DD} + V_{T2}$
Now let's assume M_1 is saturated and we'll equate the current of the transistors:

$$I_{DS1} = \frac{K_1}{2} (V_G - (2 \cdot V_T))^2 = I_{DS2} = \frac{K_2}{2} (V_G - V_{out} - V_T)^2$$

This is true when $2V_T = V_{out} + V_T \Rightarrow V_{out} = V_T$

We'll check that this holds for saturation of M_1 and M_2 . For M_1 , we need:

$$V_{DS1} = V_{out} = V_T > V_{GS1} - V_{T1} = V_G - 2V_T \Rightarrow V_G < 3V_T$$

Combining the two conditions, we have saturation when: $3V_T < V_G < V_{DD} + V_T$

E. We'll equate the current through the two transistors:

$$I_{DS2} = \frac{K_2}{2} (V_G - V_{out} - V_T)^2 = I_{DS1} = K \left((V_G - V_T)V_{out} - \frac{V_{out}^2}{2} \right)$$

$$V_{out}^2 - 2V_{GT}V_{out} + 0.5V_{GT}^2 = 0 \quad V_{GT} \equiv V_G - V_T$$

$$V_{out} = V_{GT} \left(1 \pm \frac{1}{\sqrt{2}} \right)$$

Exercise 3:

The threshold voltage of a pMOS transistor was measured at standard conditions (no body biasing) to be $|V_{TH}| = 0.4V$. Calculate the threshold voltage with a reverse body biasing of 2.5V.

The body effect coefficient is -0.4 and the Fermi potential is 0.3V.

Solution

Calculation of V_{TH} is done with the following equation:

$$V_{TH} = V_{T0} + \gamma \left(\left(\sqrt{-2\Phi_F + V_{SB}} \right) - \left(\sqrt{-2\Phi_F} \right) \right)$$

With:

	nMOS	pMOS
Φ_F	-	+
γ	+	-
V_{SB}	+	-

We were given a reverse body biasing of 2.5V, so $V_{SB} = -2.5V$. Accordingly:

$$V_{TH} = -0.4 - 0.4 \left(\left(\sqrt{-0.6 - 2.5} \right) - \left(\sqrt{-0.6} \right) \right) = -0.4 - 0.4 \cdot 0.98 = -0.79V$$

This is twice the standard threshold voltage of the transistor!