

Practice 5:

The CMOS Inverter

Voltage Transfer Characteristic


Exercise 1 – VTC Extraction

- ▶ Given the Following Parameters:

$$V_{Tn} = 1V \quad V_{Tp} = -1.5V$$


$$k_n = 100 \frac{\mu A}{V^2} \quad k_p = 50 \frac{\mu A}{V^2}$$

- ▶ Draw the inverter's VTC and find the nominal voltage levels.

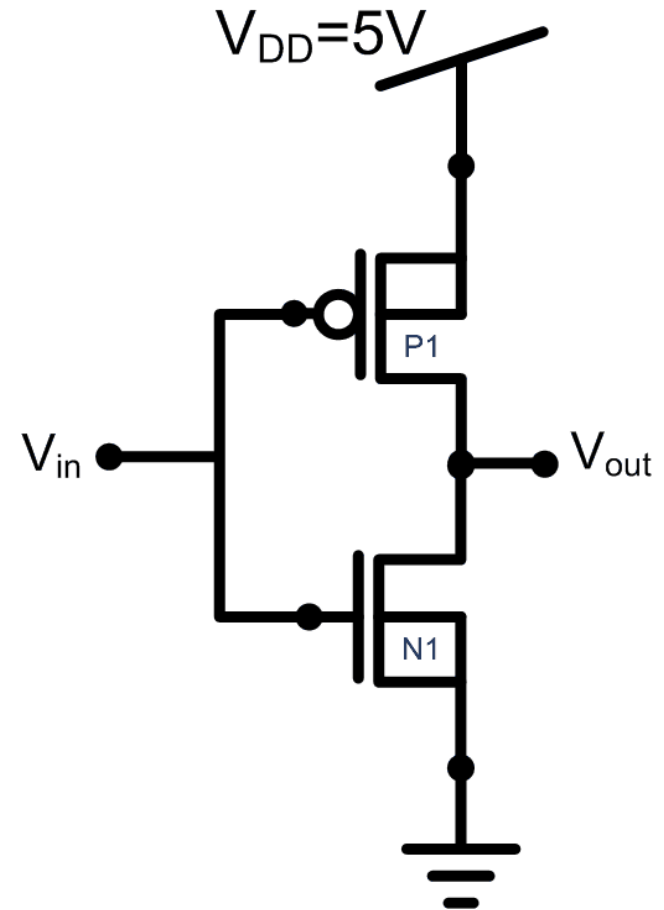

Exercise 1 – VTC Extraction

- ▶ Guessing the Operating Regions:

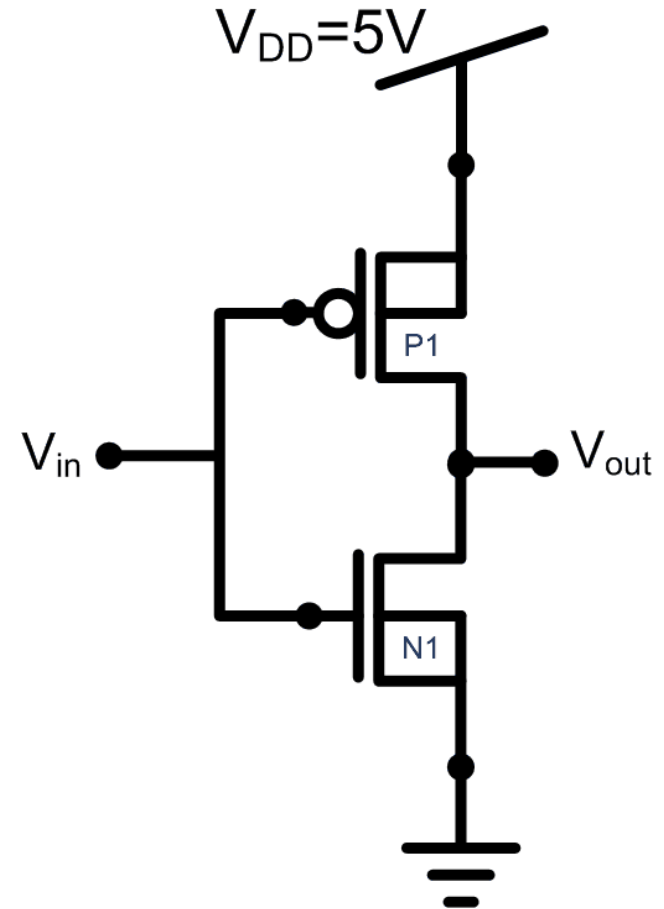

Exercise 1 – VTC Extraction


► Find V_{OHmax} :

► Find V_{IL} and V_{OHmin} :

$$I_{Dp} = k_p \left[\left(V_{SGp} - |V_{Tp}| \right) V_{SDp} - \frac{V_{SDp}^2}{2} \right]$$

$$= k_p \left[\left(V_{DD} - V_{in} - |V_{Tp}| \right) (V_{DD} - V_{out}) - \frac{(V_{DD} - V_{out})^2}{2} \right]$$

$$I_{Dn} = \frac{k_n}{2} (V_{GSn} - V_{Tn})^2 (1 + \lambda V_{DS}) \approx \frac{k_n}{2} (V_{in} - V_{Tn})^2$$

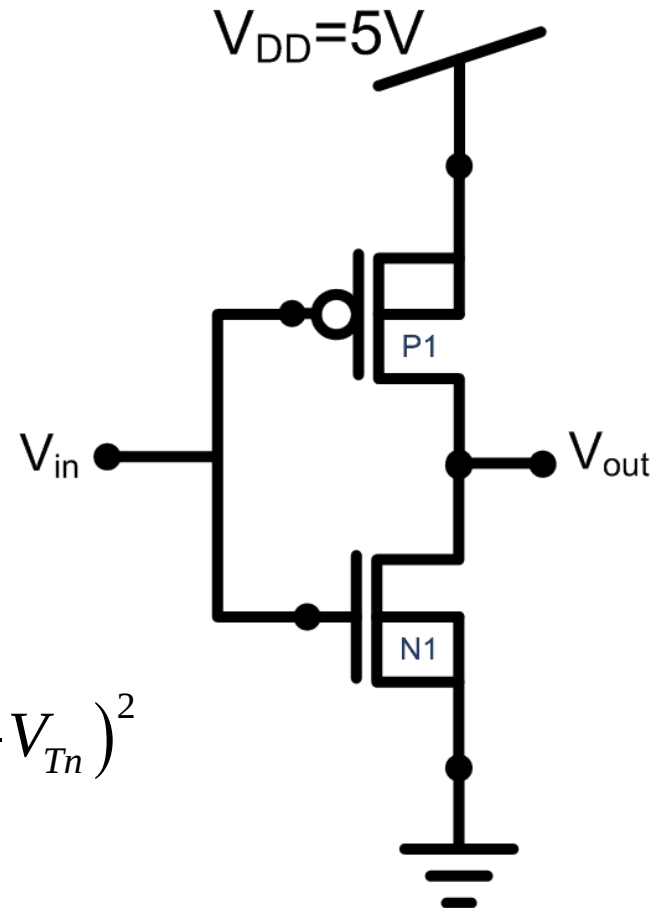

Exercise 1 – VTC Extraction

$$I_{Dp} = I_{Dn} = 50 \left[(3.5 - V_{in})(5 - V_{out}) - \frac{(5 - V_{out})^2}{2} \right] = 50(V_{in} - 1)^2$$


$$5 - 5V_{in} + 1.5V_{out} + V_{in}V_{out} - 0.5V_{out}^2 = V_{in}^2 - 2V_{in} + 1 \quad V_{DD} = 5V$$

► Differentiate by dV:

$$-5 + 1.5 \frac{dV_{out}}{dV_{in}} + V_{out} + V_{in} \frac{dV_{out}}{dV_{in}} - V_{out} \frac{dV_{out}}{dV_{in}} = 2V_{in} - 2$$

$$\frac{dV_{out}}{dV_{in}} = -1$$

$$V_{in} = \frac{2V_{out} - 4.5}{3}$$

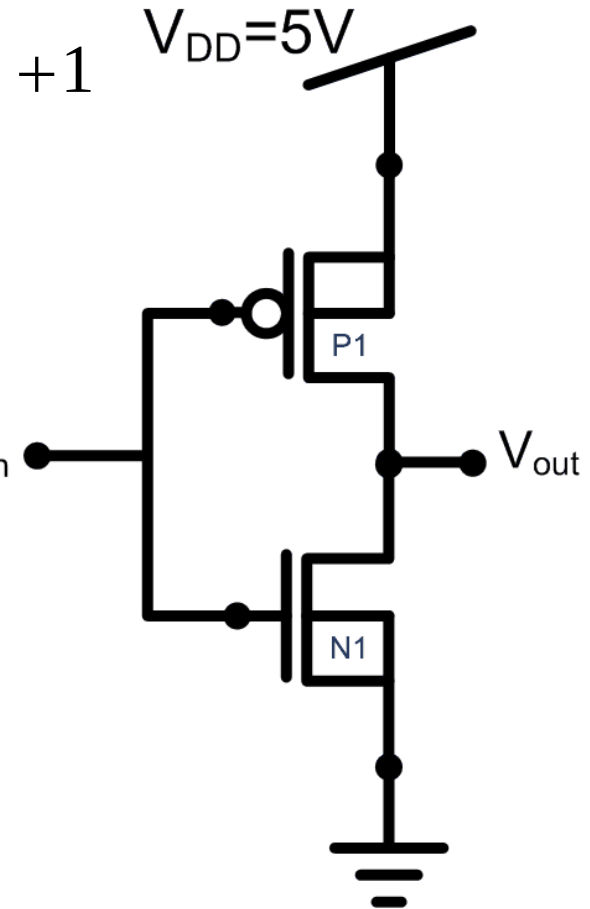

Exercise 1 – VTC Extraction

$$5 - 5V_{in} + 1.5V_{out} + V_{in}V_{out} - 0.5V_{out}^2 = V_{in}^2 - 2V_{in} + 1$$

$$V_{in} = \frac{2V_{out} - 4.5}{3}$$


$$5 - 5\frac{2V_{out} - 4.5}{3} + 1.5V_{out} + \frac{2V_{out} - 4.5}{3}V_{out} - 0.5V_{out}^2 = \left(\frac{2V_{out} - 4.5}{3} - 1\right)^2$$

$$12.5 - \frac{10}{3}V_{out} + \frac{1}{6}V_{out}^2 = \frac{4}{9}V_{out}^2 - \frac{10}{3}V_{out} + 6.25$$

$$V_{out}^2 = 22.5$$

$$V_{OH \min} = 4.7V$$

$$V_{IL} = 1.66V$$

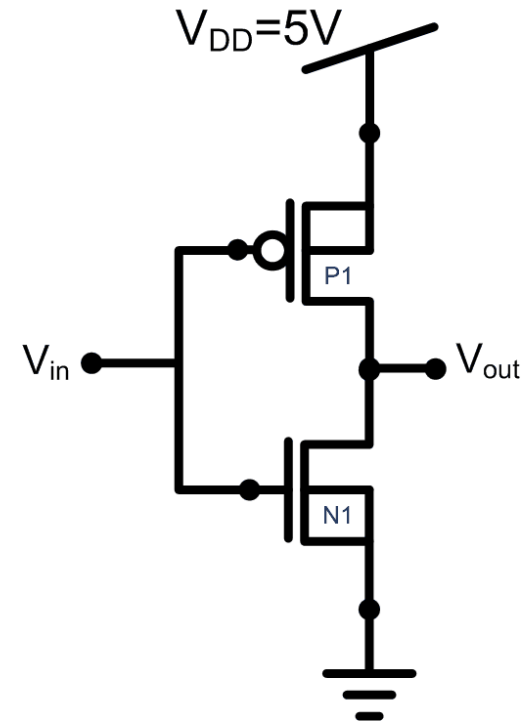

Exercise 1 – VTC Extraction


- Find V_{OLmax} and V_{IH} :

$$I_{Dn} = k_n \left[(V_{GSn} - V_{Tn}) V_{DSn} - \frac{V_{DSn}^2}{2} \right] = k_n \left[(V_{in} - V_{Tn}) V_{out} - \frac{V_{out}^2}{2} \right]$$

$$I_{Dp} = \frac{k_p}{2} (V_{SGp} - |V_{Tp}|)^2 (1 + \lambda V_{SDp}) \approx \frac{k_p}{2} (V_{DD} - V_{in} - |V_{Tp}|)^2$$

$$I_{Dn} = I_{Dp} = 100 \left[(V_{in} - 1) V_{out} - \frac{V_{out}^2}{2} \right] = 25 (5 - V_{in} - 1.5)^2$$

$$4 (V_{in} V_{out} - V_{out}^2 - 0.5 V_{out}^2) = 12.25 - 7 V_{in} + V_{in}^2$$

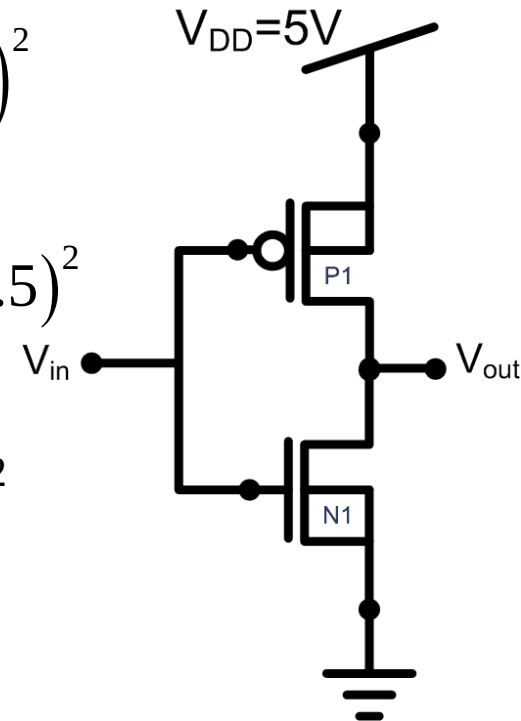

Exercise 1 – VTC Extraction

$$4(V_{in}V_{out} - V_{out} - 0.5V_{out}^2) = 12.25 - 7V_{in} + V_{in}^2$$

$$\frac{dV_{out}}{dV_{in}} = -1 \quad 4\left(V_{out} + V_{in} \frac{dV_{out}}{dV_{in}} - \frac{dV_{out}}{dV_{in}} - V_{out} \frac{dV_{out}}{dV_{in}}\right) = 2V_{in} - 7$$


$$V_{in} = \frac{8V_{out} + 11}{6}$$

$$4\left(\frac{8V_{out} + 11}{6}V_{out} - V_{out} - 0.5V_{out}^2\right) = \left(3.5 - \frac{8V_{out} + 11}{6}\right)^2$$

$$\frac{14}{9}V_{out}^2 + \frac{70}{9}V_{out} - \frac{25}{9} = 0$$


$$V_{OL\max} = 0.33$$

$$V_{IH} = 2.27$$

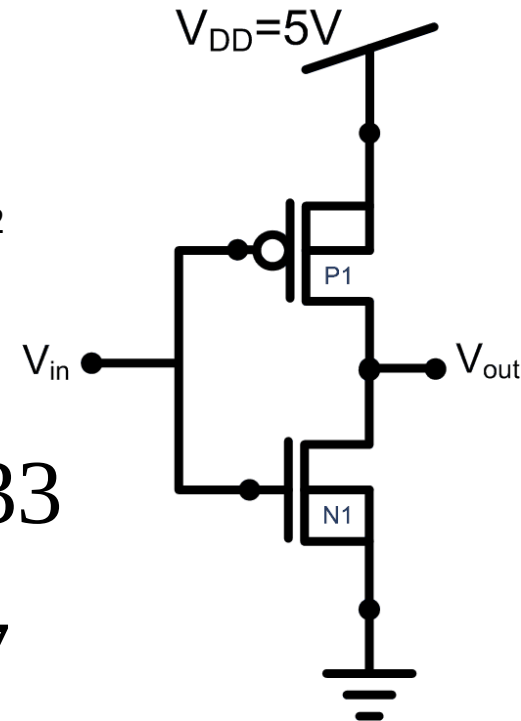

Exercise 1 – VTC Extraction

- ▶ Find V_{OLmin} :
- ▶ Draw the VTC:

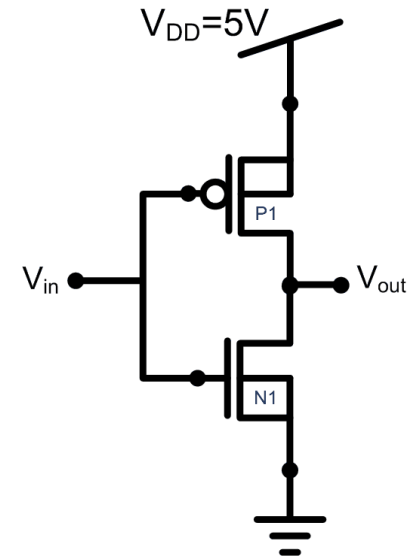

$$V_{OHmin} = 4.7V$$

$$V_{OLmax} = 0.33$$

$$V_{IL} = 1.66V$$

$$V_{IH} = 2.27$$

Exercise 2 – Propagation Delay


- ▶ Given a CMOS inverter made up of *long channel* devices with the following parameters: $\frac{(W/L)_p}{(W/L)_n} = 3.4$ $L_{\min} = 0.25\mu\text{m}$ $(W/L)_{\min} = 1.5$

$V_{DD} = 2.5\text{V}$	$V_{T0} [\text{V}]$	$\gamma [\sqrt{\text{V}}]$	$k' [\frac{\mu\text{A}}{\text{V}^2}]$	$\lambda [\text{V}^{-1}]$
nMOS	0.43	0.4	115	0.06
pMOS	-0.4	-0.4	-30	-0.1

- ▶ Find the inverter's propagation delay when driving a 50fF load.

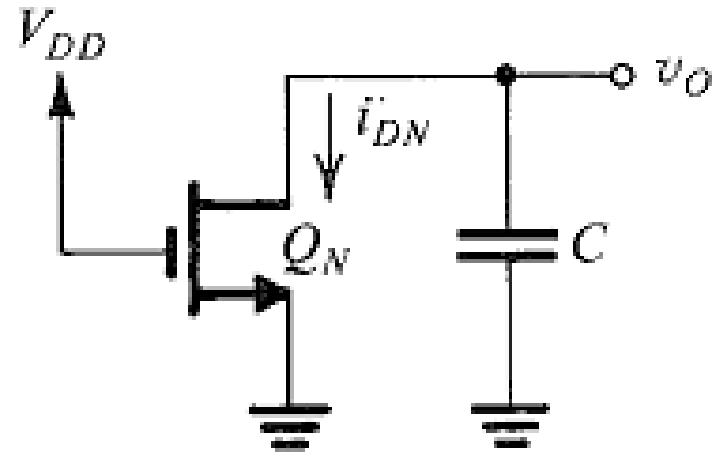Exercise 2 – Propagation Delay

- ▶ At $t < 0, V_{in} = 0 \rightarrow V_{out} = V_{DD} = 2.5V$
- ▶ At $t = 0, V_{in} = 2.5V$:
 - ▶ $V_{SGp} = 0 \rightarrow$ cut-off
 - ▶ $V_{GSn} = V_{DD} \rightarrow$ on
 - ▶ $V_{DSn} = V_{DD} \rightarrow$ saturation



$$I_{Dn} = \frac{k_n}{2} (V_{GSn} - V_{Tn})^2 (1 + \lambda V_{DS}) \approx \frac{k_n}{2} (V_{in} - V_{Tn})^2$$

Exercise 2 – Propagation Delay

- ▶ The nMOS is saturated until $V_{DS} < V_{GS} - V_T = V_{DD} - V_T$.

$$t_1 = \frac{C\Delta V}{I} = \frac{C_L \cdot V_T}{\frac{k_n}{2}(V_{DD} - V_{Tn})^2} = \frac{50 \cdot 10^{-15} \cdot 0.43}{\frac{115\mu}{2} \cdot 1.5(2.07)^2} = 0.058 \text{ nsec}$$

- ▶ Now the transistor enters linear...

Exercise 2 – Propagation Delay


► The cap current is: $I_C = C \frac{dV_{out}}{dt}$

► Which equals:

$$I_{DS} = k_n \left[(V_{DD} - V_T) V_{out} - \frac{V_{out}^2}{2} \right]$$

► So we get:
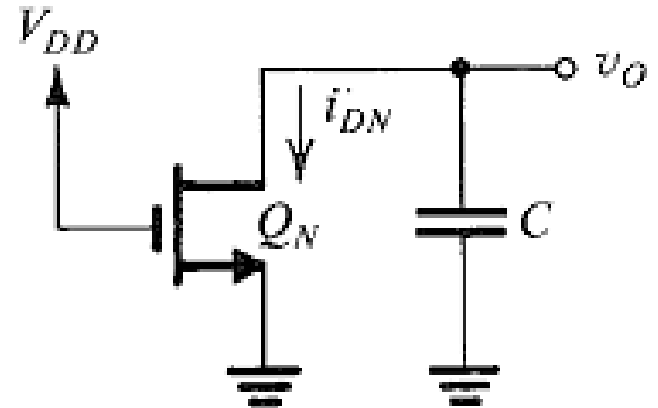
$$\frac{k_n}{C} dt = \frac{1}{(V_{DD} - V_T)} \cdot \frac{dV_{out}}{\frac{1}{2(V_{DD} - V_T) V_{out}^2 - V_{out}}}$$



$$\int \frac{dx}{ax^2 - x} = \ln \left(1 - \frac{1}{ax} \right)$$

Exercise 2 – Propagation Delay

- ▶ We need to integrate until $V_{DD}/2$:

$$\frac{k_n}{C_L} t_2 = \frac{1}{(V_{DD} - V_T)} \int_{V_{DD} - V_T}^{V_{DD}/2} \frac{dV_{out}}{\frac{1}{2(V_{DD} - V_T)V_{out}^2 - V_{out}}}$$
$$t_2 = \frac{C_L}{k_n(V_{DD} - V_T)} \ln\left(\frac{3V_{DD} - 4V_T}{V_{DD}}\right) = \frac{50 \cdot 10^{-15}}{115 \mu \cdot 1.5 \cdot 2.07} \ln\left(\frac{7.5 - 1.72}{2.5}\right) = 0.117 \text{ nsec}$$

- ▶ The total delay is:

$$t_{pHL} = 0.058 \text{ n} + 0.117 \text{ n} = 175 \text{ psec}$$