

Practice 6:

CMOS Digital Logic


The MOSFET as a Switch

The MOSFET as a Switch


- ▶ We can look at the MOSFET as a Switch, passing the data between the diffusions when it's on, and blocking the data when it's off:
 - ▶ An nMOS is on when it's gate is high:
 - ▶ A pMOS is on when it's gate is low:

ANDing and ORing

 - ▶ It is important to recognize the functionality of a *serial* and *parallel* connection of switches:
 - ▶ Connecting switches serially, creates an *AND* function:



 - ▶ Connecting switches in parallel, creates an *OR* function.



Strong and Weak Levels

- ▶ MOSFETs are imperfect switches for various reasons. One of them is the fact that each type of device is only *good* at passing one kind of signal:
 - ▶ nMOS is *good* at passing a '0':
 - ▶ But *bad* at passing a '1':
 - ▶ We like to say that the nMOS passes a “*weak 1*”

Pull Up and Pull Down Networks

- ▶ Since the nMOS is *good* at passing a '0', and the pMOS is *good* at passing a '1', we will:
 - ▶ Use nMOS devices to *pull down* the output.
 - ▶ Use pMOS devices to *pull up* the output.
- ▶ Therefore:
 - ▶ *Non-inverted* inputs to the nMOS create an *inverted output*.
 - ▶ *Inverted* inputs to the pMOS create a *non-inverted output*.
- ▶ This is what we got from the DeMorgan identities!


Creating a NAND Gate

- ▶ We now can use these principles to create a NAND gate:
 - ▶ The pull-down network of the NAND gate provides a '0' when both inputs are high.
 - ▶ The pull-up network provides a '1' for all other cases.
 - ▶ These two conditions are *complementary* so connecting them to the same output doesn't create a *contention*.
 - ▶ Instead, it creates a complete function.

A	B	PDN	PUN	NAND
0	0	Z	1	1
0	1	Z	1	1
1	0	Z	1	1
1	1	0	Z	0

 Example: Constructing a CMOS Gate

- ▶ Given a Pull Down Network:
 - ▶ A) Find the logic function of the given circuit:





$$f(A, B, C, D) = \overline{A + B(C + D)}$$

  Example: Constructing a CMOS Gate

- ▶ Given a Pull Down Network:
 - ▶ B) Construct the PUN of the function

$$\begin{aligned}f &= \overline{A + B(C + D)} \\&= \bar{A} \cdot \overline{B(C + D)} = \bar{A} \cdot (\bar{B} + \overline{C + D}) \\&= \bar{A} \cdot (\bar{B} + \bar{C}\bar{D})\end{aligned}$$



Transistor Sizing

On Resistance of a MOS Switch

- ▶ According to our unified current model, the current of a transistor is proportional to the transconductance (K):

$$I_{DS} = K \left(V_{GT} V_{DS,eff} - 0.5 V_{DS,eff}^2 \right) (1 + \lambda V_{DS})$$

$$K = \mu C_{ox} \frac{W}{L}$$

- ▶ Therefore the current *increases* with W and *decreases* with L .
- ▶ This is equivalent to saying *resistance* increases with L and *decreases* with W .

Transistor Connection Equivalence

- ▶ Connecting two transistors with the same width in series is equivalent to increasing their lengths:
$$\frac{W}{L_1} + \frac{W}{L_2} \Leftrightarrow \frac{W}{(L_1 + L_2)}$$
- ▶ Connecting two transistors with the same length in parallel is similar to increasing their widths.
$$\frac{W_1}{L} \parallel \frac{W_2}{L} \Leftrightarrow \frac{(W_1 + W_2)}{L}$$

Transistor Connection Equivalence

► In general, since: $R_{eq} \propto 1/K \propto L/W$

► When connecting transistors in series:


$$R_{series} = R_{eq1} + R_{eq2} + \dots \propto \frac{1}{k_1} + \frac{1}{k_2} + \dots$$

► When connecting transistors in parallel:

$$R_{parallel} = \frac{1}{R_{eq1}} + \frac{1}{R_{eq2}} + \dots \propto k_1 + k_2 + \dots$$

 Example: Equivalent Transconductance

- What is the equivalent transconductance of the following network?




$$\frac{W_{\min}}{L_{\min}} \parallel \frac{W_{\min}}{L_{\min}} = \frac{2W_{\min}}{L_{\min}}$$

$$\frac{2W_{\min}}{L_{\min}} + \frac{W_{\min}}{L_{\min}} = \frac{2W_{\min}}{L_{\min}} + \frac{2W_{\min}}{2L_{\min}} = \frac{2W_{\min}}{3L_{\min}} \propto \frac{2}{3} K_{\min}$$

 
Example: Worst Case Path

- ▶ However, we can only set the size according to the *Worst Case Path* so we will look for serially connected networks:
- ▶ Then we will size the devices to be equivalent to one minimally sized nMOS:




 Example: Sizing a CMOS Gate

- ▶ Now we can go back to sizing our complex CMOS Gate.
- ▶ In class we saw that $\beta_{opt}=2$.



- ▶ Method 1: Find all Serial Networks

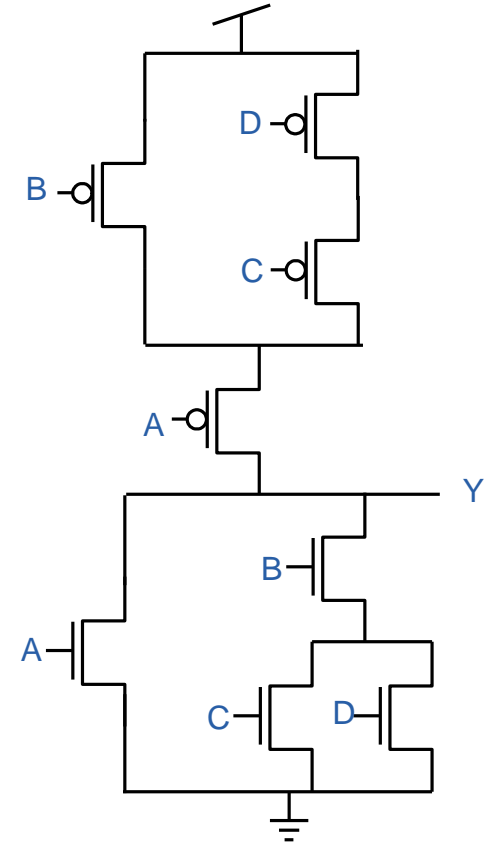

Example: Sizing a CMOS Gate

► Method 2: Find all Serial Networks

► For the PUN, we find the worst case path.


► Then to size the remaining devices we will use the equation:

$$\frac{1}{\frac{W_{peq}}{L_{peq}}} = \frac{1}{\frac{W_{pA}}{L_{pA}}} + \frac{1}{\frac{W_{pA}}{L_{pA}}}$$

$$W_{peq} = 2W_{\min}$$
$$L_i = L_{\min}$$

$$\frac{1}{2W_{\min}} = \frac{1}{W_{pA}} + \frac{1}{W_{pB}} = \frac{1}{6W_{\min}} + \frac{1}{W_{pB}}$$

$$W_{pB} = 3W_{\min}$$

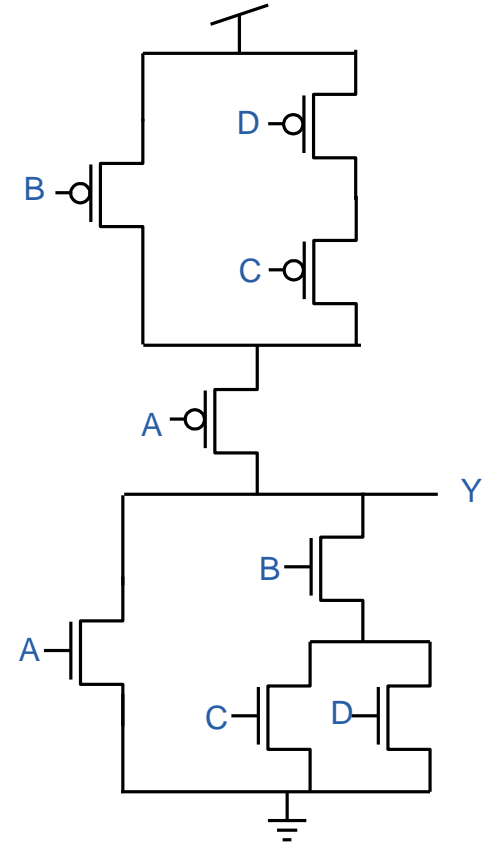

Exercise: Constructing a Complex Gate

- ▶ **Given the equation:** $f = ((\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F})\bar{G}$
- ▶ A) Build a CMOS gate that realizes the equation
- ▶ B) Size the gate with $(W/L)_n = 2$ $(W/L)_p = 6$
- ▶ C) What are the best and worst case patterns for PUN and PDN resistance?

Exercise: Constructing a Complex Gate

- ▶ A) First we'll find the appropriate PDN for the given function.

$$\begin{aligned} f &= \overline{\overline{\left(\left(\bar{A} + \bar{B}\right)\left(\bar{C} + \bar{D} + \bar{E}\right) + \bar{F}\right)}\bar{G}} = \overline{\left(\bar{A} + \bar{B}\right)\left(\bar{C} + \bar{D} + \bar{E}\right) + \bar{F} + G} = \\ &= \overline{\left(\bar{A} + \bar{B}\right)\left(\bar{C} + \bar{D} + \bar{E}\right) \cdot F + G} = \overline{\left(\bar{A} + \bar{B} + \bar{C} + \bar{D} + \bar{E}\right) \cdot F + G} = \\ &= \overline{\left(\left(A \cdot B\right) + \left(C \cdot D \cdot E\right)\right) \cdot F + G} \end{aligned}$$



Exercise: Constructing a Complex Gate

- Now we can draw our logic gate.

$$f = \underbrace{\left((\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F} \right) \bar{G}}_{PUN} = \overline{\underbrace{\left((A \cdot B) + (C \cdot D \cdot E) \right) \cdot F + G}_{PDN}}$$

  Exercise: Constructing a Complex Gate

- ▶ B) Next we will size the PDN according to $(W/L)_n = 2$
- ▶ Finally, we will size the PUN according to $(W/L)_p = 6$



Exercise: Constructing a Complex Gate

► C) Best case patterns:

- High to Low Transition
- Low to High Transition

► Worst Case Patterns:

- High to Low Transition
- Low to High Transition

